

# Computer Architecture

Dr. Esti Stein

(Partly taken from Dr. Alon Schclar slides)

Based on slides by:

**Prof. Myung-Eui Lee**

Korea University of Technology & Education  
Department of Information & Communication

Taken from: **M.**

**Mano/Computer Design and  
Architecture 3<sup>rd</sup> Ed.**

# Microoperations Types

## Data transfer only

1. Register Transfer microoperations transfer binary information from one register to another
2. Arithmetic microoperations perform arithmetic operation on numeric data stored in registers.
3. Logic microoperations perform bit manipulation operations on non numeric data stored in registers.
4. Shift microoperations perform shift operations data stored in registers.

## Changes data during transfer

# Arithmetic Microoperations

Basic: addition, subtraction, increment, decrement & shift

Multiplication and division are not basic

# Arithmetic Microoperations

There are two identical operations

**TABLE 4-3** Arithmetic Microoperations

| Symbolic designation                   | Description  |
|--|--|
| $R3 \leftarrow R1 + R2$                | Contents of $R1$ plus $R2$ transferred to $R3$     |
| $R3 \leftarrow R1 - R2$                | Contents of $R1$ minus $R2$ transferred to $R3$    |
| $R2 \leftarrow \overline{R2}$          | Complement the contents of $R2$ (1's complement)   |
| $R2 \leftarrow \overline{R2} + 1$      | 2's complement the contents of $R2$ (negate)       |
| $R3 \leftarrow R1 + \overline{R2} + 1$ | $R1$ plus the 2's complement of $R2$ (subtraction) |
| $R1 \leftarrow R1 + 1$                 | Increment the contents of $R1$ by one              |
| $R1 \leftarrow R1 - 1$                 | Decrement the contents of $R1$ by one              |


# Binary Adder-Subtractor

•  $M = 0$  : Adder

$$B \oplus M + C_0 = B \oplus 0 + 0 = B \Rightarrow S = A + B$$

•  $M = 1$  : Subtractor
 
$$B \oplus M + C_0 \rightarrow B \oplus 1 + 1 = B' + 1 = -B \Rightarrow S = A - B$$



# Binary Incrementer

Sequential circuit using a binary counter

Truth Table

| J | K | CLK | Q                     |
|---|---|-----|-----------------------|
| 0 | 0 | ↑   | $Q_0$ (no change)     |
| 1 | 0 | ↑   | 1                     |
| 0 | 1 | ↑   | 0                     |
| 1 | 1 | ↑   | $\bar{Q}_0$ (toggles) |

Combinational circuit using half adders


 
 


Figure 2-10 4-bit synchronous binary counter.

# Arithmetic Circuit

TABLE 4-4 Arithmetic Circuit Function Table


| Select |       |          | Input<br>$Y$   | Output<br>$D = A + Y + C_{in}$ | Microoperation       |
|--------|-------|----------|----------------|--------------------------------|----------------------|
| $S_1$  | $S_0$ | $C_{in}$ |                |                                |                      |
| 0      | 0     | 0        | $B$            | $D = A + B$                    | Add                  |
| 0      | 0     | 1        | $B$            | $D = A + B + 1$                | Add with carry       |
| 0      | 1     | 0        | $\overline{B}$ | $D = A + \overline{B}$         | Subtract with borrow |
| 0      | 1     | 1        | $\overline{B}$ | $D = A + \overline{B} + 1$     | Subtract             |
| 1      | 0     | 0        | 0              | $D = A$                        | Transfer $A$         |
| 1      | 0     | 1        | 0              | $D = A + 1$                    | Increment $A$        |
| 1      | 1     | 0        | 1              | $D = A - 1$                    | Decrement $A$        |
| 1      | 1     | 1        | 1              | $D = A$                        | Transfer $A$         |

 

# Arithmetic Circuit

TABLE 4-4 Arithmetic Circuit Function Table

| Select |       |          | Input<br>$Y$   | Output<br>$D = A + Y + C_{in}$ | Microoperation       |
|--------|-------|----------|----------------|--------------------------------|----------------------|
| $S_1$  | $S_0$ | $C_{in}$ |                |                                |                      |
| 0      | 0     | 0        | $B$            | $D = A + B$                    | Add                  |
| 0      | 0     | 1        | $B$            | $D = A + B + 1$                | Add with carry       |
| 0      | 1     | 0        | $\overline{B}$ | $D = A + \overline{B}$         | Subtract with borrow |
| 0      | 1     | 1        | $\overline{B}$ | $D = A + \overline{B} + 1$     | Subtract             |
| 1      | 0     | 0        | 0              | $D = A$                        | Transfer $A$         |
| 1      | 0     | 1        | 0              | $D = A + 1$                    | Increment $A$        |
| 1      | 1     | 0        | 1              | $D = A - 1$                    | Decrement $A$        |
| 1      | 1     | 1        | 1              | $D = A$                        | Transfer $A$         |

 




# Arithmetic Circuit

TABLE 4-4 Arithmetic Circuit Function Table


| Select |       |          | Input<br>$Y$   | Output<br>$D = A + Y + C_{in}$ | Microoperation       |
|--------|-------|----------|----------------|--------------------------------|----------------------|
| $S_1$  | $S_0$ | $C_{in}$ |                |                                |                      |
| 0      | 0     | 0        | $B$            | $D = A + B$                    | Add                  |
| 0      | 0     | 1        | $B$            | $D = A + B + 1$                | Add with carry       |
| 0      | 1     | 0        | $\overline{B}$ | $D = A + \overline{B}$         | Subtract with borrow |
| 0      | 1     | 1        | $\overline{B}$ | $D = A + \overline{B} + 1$     | Subtract             |
| 1      | 0     | 0        | 0              | $D = A$                        | Transfer $A$         |
| 1      | 0     | 1        | 0              | $D = A + 1$                    | Increment $A$        |
| 1      | 1     | 0        | 1              | $D = A - 1$                    | Decrement $A$        |
| 1      | 1     | 1        | 1              | $D = A$                        | Transfer $A$         |

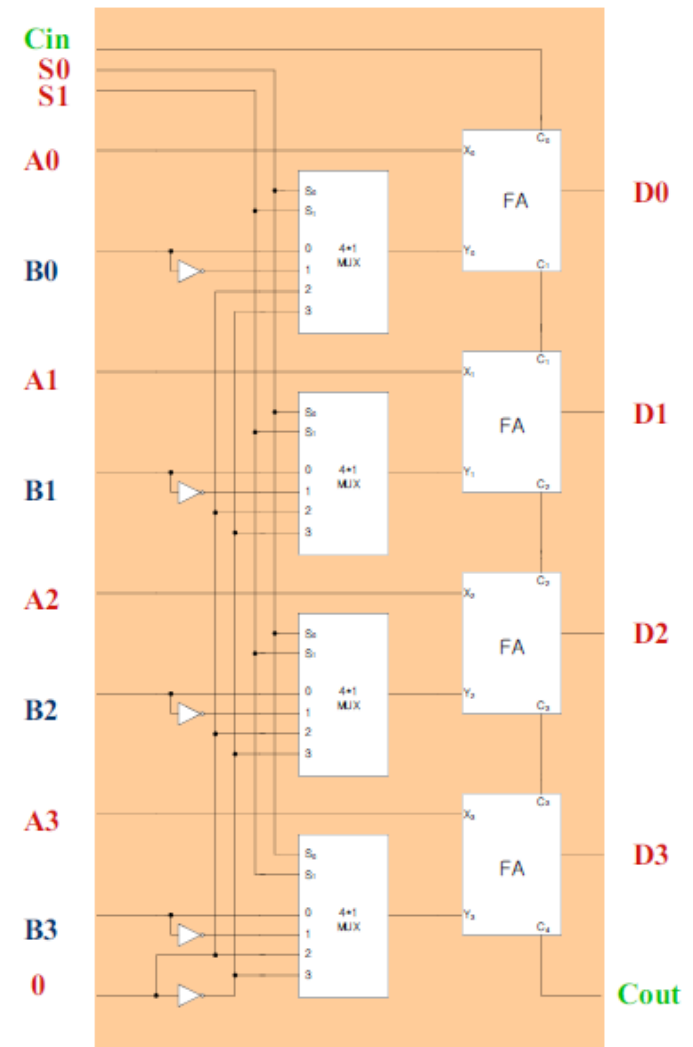

# Arithmetic Circuit

TABLE 4-4 Arithmetic Circuit Function Table

| Select |       |          | Input<br>$Y$   | Output<br>$D = A + Y + C_{in}$ | Microoperation       |
|--------|-------|----------|----------------|--------------------------------|----------------------|
| $S_1$  | $S_0$ | $C_{in}$ |                |                                |                      |
| 0      | 0     | 0        | $B$            | $D = A + B$                    | Add                  |
| 0      | 0     | 1        | $B$            | $D = A + B + 1$                | Add with carry       |
| 0      | 1     | 0        | $\overline{B}$ | $D = A + \overline{B}$         | Subtract with borrow |
| 0      | 1     | 1        | $\overline{B}$ | $D = A + \overline{B} + 1$     | Subtract             |
| 1      | 0     | 0        | 0              | $D = A$                        | Transfer $A$         |
| 1      | 0     | 1        | 0              | $D = A + 1$                    | Increment $A$        |
| 1      | 1     | 0        | 1              | $D = A - 1$                    | Decrement $A$        |
| 1      | 1     | 1        | 1              | $D = A$                        | Transfer $A$         |

 


# Logic Microoperations

Logic microoperations consider *each bit of the register separately* and treat them as binary variables

 
Example : XOR

if ( $P = 1$ ) then  $R1 \leftarrow R1 \oplus R2$  or in RTL  $P : R1 \leftarrow R1 \oplus R2$



# Logic Microoperations

|       |       |       |       |       |
|-------|-------|-------|-------|-------|
| R1 :  | 1     | 0     | 0     | 1     |
| R2 :  | 1     | 1     | 0     | 0     |
| <hr/> |       |       |       |       |
| R1 :  | 0     | 1     | 0     | 1     |
|       | $s_3$ | $s_2$ | $s_1$ | $s_0$ |

 

# Logic Microoperations

Special symbols in RTL :

Left side - condition

**Or** denoted by  $+$   
**And** denoted by  $\cdot$   
**complement** denoted by  $'$

Right side - operation

**Or** denoted by  $\vee$   
**And** denoted by  $\wedge$   
**complement** denoted by  $\overline{\phantom{x}}$   
**Arith. Plus** denoted by  $+$   
**Arith. Mult.** denoted by  $*$

Example:

$P + Q : R1 \leftarrow R1 + R2, R3 \leftarrow R4 \vee R5$

↑                      ↑                      ↑  
or                      addition                      or

# Logic Microoperations

There are 16 different function that can be performed with two binary variables:

**TABLE 4-5** Truth Tables for 16 Functions of Two Variables

| <i>x</i> | <i>y</i> | <i>F</i> <sub>0</sub> | <i>F</i> <sub>1</sub> | <i>F</i> <sub>2</sub> | <i>F</i> <sub>3</sub> | <i>F</i> <sub>4</sub> | <i>F</i> <sub>5</sub> | <i>F</i> <sub>6</sub> | <i>F</i> <sub>7</sub> | <i>F</i> <sub>8</sub> | <i>F</i> <sub>9</sub> | <i>F</i> <sub>10</sub> | <i>F</i> <sub>11</sub> | <i>F</i> <sub>12</sub> | <i>F</i> <sub>13</sub> | <i>F</i> <sub>14</sub> | <i>F</i> <sub>15</sub> |
|----------|----------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|------------------------|------------------------|------------------------|------------------------|------------------------|------------------------|
| 0        | 0        | 0                     | 0                     | 0                     | 0                     | 0                     | 0                     | 0                     | 0                     | 1                     | 1                     | 1                      | 1                      | 1                      | 1                      | 1                      | 1                      |
| 0        | 1        | 0                     | 0                     | 0                     | 0                     | 1                     | 1                     | 1                     | 1                     | 0                     | 0                     | 0                      | 0                      | 1                      | 1                      | 1                      | 1                      |
| 1        | 0        | 0                     | 0                     | 1                     | 1                     | 0                     | 0                     | 1                     | 1                     | 0                     | 0                     | 1                      | 1                      | 0                      | 0                      | 1                      | 1                      |
| 1        | 1        | 0                     | 1                     | 0                     | 1                     | 0                     | 1                     | 0                     | 1                     | 0                     | 1                     | 0                      | 1                      | 0                      | 1                      | 0                      | 1                      |

$F \leftarrow 0$

# Logic Microoperations

There are 16 different function that can be performed with two binary variables:

**TABLE 4-5** Truth Tables for 16 Functions of Two Variables

| <i>x</i> | <i>y</i> | <i>F</i> <sub>0</sub> | <i>F</i> <sub>1</sub> | <i>F</i> <sub>2</sub> | <i>F</i> <sub>3</sub> | <i>F</i> <sub>4</sub> | <i>F</i> <sub>5</sub> | <i>F</i> <sub>6</sub> | <i>F</i> <sub>7</sub> | <i>F</i> <sub>8</sub> | <i>F</i> <sub>9</sub> | <i>F</i> <sub>10</sub> | <i>F</i> <sub>11</sub> | <i>F</i> <sub>12</sub> | <i>F</i> <sub>13</sub> | <i>F</i> <sub>14</sub> | <i>F</i> <sub>15</sub> |
|----------|----------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|------------------------|------------------------|------------------------|------------------------|------------------------|------------------------|
| 0        | 0        | 0                     | 0                     | 0                     | 0                     | 0                     | 0                     | 0                     | 0                     | 1                     | 1                     | 1                      | 1                      | 1                      | 1                      | 1                      | 1                      |
| 0        | 1        | 0                     | 0                     | 0                     | 0                     | 1                     | 1                     | 1                     | 1                     | 0                     | 0                     | 0                      | 0                      | 1                      | 1                      | 1                      | 1                      |
| 1        | 0        | 0                     | 0                     | 1                     | 1                     | 0                     | 0                     | 1                     | 1                     | 0                     | 0                     | 1                      | 1                      | 0                      | 0                      | 1                      | 1                      |
| 1        | 1        | 0                     | 1                     | 0                     | 1                     | 0                     | 1                     | 0                     | 1                     | 0                     | 1                     | 0                      | 1                      | 0                      | 1                      | 0                      | 1                      |


$$F \leftarrow xy$$

# Logic Microoperations

There are 16 different function that can be performed with two binary variables:

**TABLE 4-5** Truth Tables for 16 Functions of Two Variables

| <i>x</i> | <i>y</i> | <i>F</i> <sub>0</sub> | <i>F</i> <sub>1</sub> | <i>F</i> <sub>2</sub> | <i>F</i> <sub>3</sub> | <i>F</i> <sub>4</sub> | <i>F</i> <sub>5</sub> | <i>F</i> <sub>6</sub> | <i>F</i> <sub>7</sub> | <i>F</i> <sub>8</sub> | <i>F</i> <sub>9</sub> | <i>F</i> <sub>10</sub> | <i>F</i> <sub>11</sub> | <i>F</i> <sub>12</sub> | <i>F</i> <sub>13</sub> | <i>F</i> <sub>14</sub> | <i>F</i> <sub>15</sub> |
|----------|----------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|------------------------|------------------------|------------------------|------------------------|------------------------|------------------------|
| 0        | 0        | 0                     | 0                     | 0                     | 0                     | 0                     | 0                     | 0                     | 0                     | 1                     | 1                     | 1                      | 1                      | 1                      | 1                      | 1                      | 1                      |
| 0        | 1        | 0                     | 0                     | 0                     | 0                     | 1                     | 1                     | 1                     | 1                     | 0                     | 0                     | 0                      | 0                      | 1                      | 1                      | 1                      | 1                      |
| 1        | 0        | 0                     | 0                     | 1                     | 1                     | 0                     | 0                     | 1                     | 1                     | 0                     | 0                     | 1                      | 1                      | 0                      | 0                      | 1                      | 1                      |
| 1        | 1        | 0                     | 1                     | 0                     | 1                     | 0                     | 1                     | 0                     | 1                     | 0                     | 1                     | 0                      | 1                      | 0                      | 1                      | 0                      | 1                      |

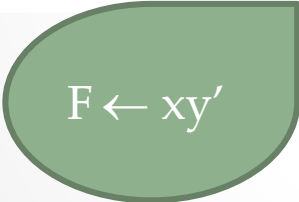
$$F \leftarrow xy'$$



# Logic Microoperations

There are 16 different function that can be performed with two binary variables:

**TABLE 4-5** Truth Tables for 16 Functions of Two Variables

| <i>x</i> | <i>y</i> | <i>F</i> <sub>0</sub> | <i>F</i> <sub>1</sub> | <i>F</i> <sub>2</sub> | <i>F</i> <sub>3</sub> | <i>F</i> <sub>4</sub> | <i>F</i> <sub>5</sub> | <i>F</i> <sub>6</sub> | <i>F</i> <sub>7</sub> | <i>F</i> <sub>8</sub> | <i>F</i> <sub>9</sub> | <i>F</i> <sub>10</sub> | <i>F</i> <sub>11</sub> | <i>F</i> <sub>12</sub> | <i>F</i> <sub>13</sub> | <i>F</i> <sub>14</sub> | <i>F</i> <sub>15</sub> |
|----------|----------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|------------------------|------------------------|------------------------|------------------------|------------------------|------------------------|
| 0        | 0        | 0                     | 0                     | 0                     | 0                     | 0                     | 0                     | 0                     | 0                     | 1                     | 1                     | 1                      | 1                      | 1                      | 1                      | 1                      | 1                      |
| 0        | 1        | 0                     | 0                     | 0                     | 0                     | 1                     | 1                     | 1                     | 1                     | 0                     | 0                     | 0                      | 0                      | 1                      | 1                      | 1                      | 1                      |
| 1        | 0        | 0                     | 0                     | 1                     | 1                     | 0                     | 0                     | 1                     | 1                     | 0                     | 0                     | 1                      | 1                      | 0                      | 0                      | 1                      | 1                      |
| 1        | 1        | 0                     | 1                     | 0                     | 1                     | 0                     | 1                     | 0                     | 1                     | 0                     | 1                     | 0                      | 1                      | 0                      | 1                      | 0                      | 1                      |

$F \leftarrow ?$

# Logic Microoperations

There are 16 different function that can be performed with two binary variables:

**TABLE 4-5** Truth Tables for 16 Functions of Two Variables

| <i>x</i> | <i>y</i> | <i>F</i> <sub>0</sub> | <i>F</i> <sub>1</sub> | <i>F</i> <sub>2</sub> | <i>F</i> <sub>3</sub> | <i>F</i> <sub>4</sub> | <i>F</i> <sub>5</sub> | <i>F</i> <sub>6</sub> | <i>F</i> <sub>7</sub> | <i>F</i> <sub>8</sub> | <i>F</i> <sub>9</sub> | <i>F</i> <sub>10</sub> | <i>F</i> <sub>11</sub> | <i>F</i> <sub>12</sub> | <i>F</i> <sub>13</sub> | <i>F</i> <sub>14</sub> | <i>F</i> <sub>15</sub> |
|----------|----------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|-----------------------|------------------------|------------------------|------------------------|------------------------|------------------------|------------------------|
| 0        | 0        | 0                     | 0                     | 0                     | 0                     | 0                     | 0                     | 0                     | 0                     | 1                     | 1                     | 1                      | 1                      | 1                      | 1                      | 1                      | 1                      |
| 0        | 1        | 0                     | 0                     | 0                     | 0                     | 1                     | 1                     | 1                     | 1                     | 0                     | 0                     | 0                      | 0                      | 1                      | 1                      | 1                      | 1                      |
| 1        | 0        | 0                     | 0                     | 1                     | 1                     | 0                     | 0                     | 1                     | 1                     | 0                     | 0                     | 1                      | 1                      | 0                      | 0                      | 1                      | 1                      |
| 1        | 1        | 0                     | 1                     | 0                     | 1                     | 0                     | 1                     | 0                     | 1                     | 0                     | 1                     | 0                      | 1                      | 0                      | 1                      | 0                      | 1                      |

$$F \leftarrow x \oplus y$$

# Logic Microoperations

TABLE 4-6 Sixteen Logic Microoperations

| Boolean function      | Microoperation                       | Name           |
|-----------------------|--------------------------------------|----------------|
| $F_0 = 0$             | $F \leftarrow 0$                     | Clear          |
| $F_1 = xy$            | $F \leftarrow A \wedge B$            | AND            |
| $F_2 = xy'$           | $F \leftarrow A \wedge \overline{B}$ |                |
| $F_3 = x$             | $F \leftarrow A$                     | Transfer $A$   |
| $F_4 = x'y$           | $F \leftarrow \overline{A} \wedge B$ |                |
| $F_5 = y$             | $F \leftarrow B$                     | Transfer $B$   |
| $F_6 = x \oplus y$    | $F \leftarrow A \oplus B$            | Exclusive-OR   |
| $F_7 = x + y$         | $F \leftarrow A \vee B$              | OR             |
| $F_8 = (x + y)'$      | $F \leftarrow \overline{A \vee B}$   | NOR            |
| $F_9 = (x \oplus y)'$ | $F \leftarrow \overline{A \oplus B}$ | Exclusive-NOR  |
| $F_{10} = y'$         | $F \leftarrow \overline{B}$          | Complement $B$ |
| $F_{11} = x + y'$     | $F \leftarrow A \vee \overline{B}$   |                |
| $F_{12} = x'$         | $F \leftarrow \overline{A}$          | Complement $A$ |
| $F_{13} = x' + y$     | $F \leftarrow \overline{A} \vee B$   |                |
| $F_{14} = (xy)'$      | $F \leftarrow \overline{A \wedge B}$ | NAND           |
| $F_{15} = 1$          | $F \leftarrow \text{all 1's}$        | Set to all 1's |

TABLE 4-5 Truth Tables for 16


| $x$ | $y$ | $F_0$ | $F_1$ | $F_2$ | $F_3$ | $F_4$ | $F_5$ | $F_6$ | $F_7$ |
|-----|-----|-------|-------|-------|-------|-------|-------|-------|-------|
| 0   | 0   | 0     | 0     | 0     | 0     | 0     | 0     | 0     | 0     |
| 0   | 1   | 0     | 0     | 0     | 0     | 1     | 1     | 1     | 1     |
| 1   | 0   | 0     | 0     | 1     | 1     | 0     | 0     | 1     | 1     |
| 1   | 1   | 0     | 1     | 0     | 1     | 0     | 1     | 0     | 1     |

| $x$ | $y$ | $F_8$ | $F_9$ | $F_{10}$ | $F_{11}$ | $F_{12}$ | $F_{13}$ | $F_{14}$ | $F_{15}$ |
|-----|-----|-------|-------|----------|----------|----------|----------|----------|----------|
| 0   | 0   | 1     | 1     | 1        | 1        | 1        | 1        | 1        | 1        |
| 0   | 1   | 0     | 0     | 0        | 0        | 1        | 1        | 1        | 1        |
| 1   | 0   | 0     | 0     | 1        | 1        | 0        | 0        | 1        | 1        |
| 1   | 1   | 0     | 1     | 0        | 1        | 0        | 1        | 0        | 1        |

# LM – HW implementaion

- Logic gates are inserted for each bit or pair of bits in the registers.
- Most computers use only 4 operations: AND, OR, XOR and complement.
- All 12 others can be derived.

Figure 4-10 One stage of logic circuit.

 

(a) Logic diagram

| $S_1$ | $S_0$ | Output           | Operation  |
|-------|-------|------------------|------------|
| 0     | 0     | $E = A \wedge B$ | AND        |
| 0     | 1     | $E = A \vee B$   | OR         |
| 1     | 0     | $E = A \oplus B$ | XOR        |
| 1     | 1     | $E = \bar{A}$    | Complement |

(b) Function table

# LM - applications

- Logic microoperations are very useful for *manipulating individual bits* or *a portion of a word* stored in a register
- Used to change bit values, delete a group of bits, or insert new bit values

Selective set:

$$A \leftarrow A \vee B$$

Sets to 1 the bits in register A where there are corresponding 1's in register B.

It does not effect bit positions that have 0's in B.

|       |   |   |   |   |
|-------|---|---|---|---|
| A :   | 1 | 0 | 1 | 0 |
| B :   | 1 | 1 | 0 | 0 |
| <hr/> |   |   |   |   |
| A :   | 1 | 1 | 1 | 0 |

# LM - applications

- Logic microoperations are very useful for *manipulating individual bits* or *a portion of a word* stored in a register
- Used to change bit values, delete a group of bits, or insert new bit values

## Selective complement:

$$A \leftarrow A \oplus B$$

Complements to 1 the bits in register A where there are corresponding 1's in register B. It does not effect bit positions that have 0's in B.

|       |   |   |   |   |
|-------|---|---|---|---|
| A :   | 1 | 0 | 1 | 0 |
| B :   | 1 | 1 | 0 | 0 |
| <hr/> |   |   |   |   |
| A :   | 0 | 1 | 1 | 0 |

# LM - applications

- Logic microoperations are very useful for *manipulating individual bits* or *a portion of a word* stored in a register
- Used to change bit values, delete a group of bits, or insert new bit values

Selective clear:

$$A \leftarrow A \wedge \bar{B}$$

Clears to 0 the bits in register A where there are corresponding 1's in register B.

It does not effect bit positions that have 0's in B.

|       |   |   |   |   |
|-------|---|---|---|---|
| A :   | 1 | 0 | 1 | 0 |
| B :   | 1 | 1 | 0 | 0 |
| <hr/> |   |   |   |   |
| A :   | 0 | 0 | 1 | 0 |

$\wedge$  not

# LM - applications

- Logic microoperations are very useful for *manipulating individual bits* or *a portion of a word* stored in a register
- Used to change bit values, delete a group of bits, or insert new bit values

Selective mask:

$$A \leftarrow A \wedge B$$

The mask operation is similar to the selective-clear operation.

Except that the bits of A are cleared only where there are corresponding 0's in B.

|       |   |   |   |   |
|-------|---|---|---|---|
| A :   | 1 | 0 | 1 | 0 |
| B :   | 1 | 1 | 0 | 0 |
| <hr/> |   |   |   |   |
| A :   | 1 | 0 | 0 | 0 |




# LM - applications

 
## Insert:

- The insert operation inserts a new value into a group of bits.
- This is done by :
  1. Masking the bits
  2. ORing them with the required value

We would like to change the two rightmost bits of A to 0 1



Clear the bits you want to change

 

Set the bits to the desired pattern

# LM - applications

- Logic microoperations are very useful for *manipulating individual bits* or *a portion of a word* stored in a register
- Used to change bit values, delete a group of bits, or insert new bit values

Clear operation:

$$A \leftarrow A \oplus B$$

The clear operation compares the words in A and B and produces an all 0's result if the two numbers are equal.


|       |   |   |   |   |
|-------|---|---|---|---|
| A :   | 1 | 0 | 1 | 0 |
| B :   | 1 | 0 | 0 | 0 |
| <hr/> |   |   |   |   |
| A :   | 0 | 0 | 1 | 0 |

# Shift Microoperations

- Shift microoperations can be used for serial transfer of data.
- Three types of shift microoperation : *Logical*, *Circular*, and *Arithmetic*

A *logical shift* transfers 0 through the serial input. The bit transferred to the end position through the serial input is assumed to be 0 during a logical shift.

 *Shl* – for shift left (insert 0 from rightmost side)



$R1 \leftarrow \text{shl } R1$


# Shift Microoperations

- Shift microoperations can be used for serial transfer of data.
- Three types of shift microoperation : *Logical*, *Circular*, and *Arithmetic*

A *logical shift* transfers 0 through the serial input.

The bit transferred to the end position through the serial input is assumed to be 0 during a logical shift.

 *Shl* – for shift left (insert 0 from rightmost side)



$R1 \leftarrow \text{shl } R1$


# Shift Microoperations

- Shift microoperations can be used for serial transfer of data.
- Three types of shift microoperation : *Logical*, *Circular*, and *Arithmetic*

A logical shift transfers 0 through the serial input.


The bit transferred to the end position through the serial input is assumed to be 0 during a logical shift.

 Shr – for shift right (insert 0 from leftmost side)



 
# Circular shift

A *circular shift* circulates bits of the register around the two ends without loss of any bit.


 
# Circular shift

A *circular shift* circulates bits of the register around the two ends without loss of any bit.



$R1 \leftarrow \text{cil } R1$

# Arithmetic shift

- An *arithmetic shift* shifts a signed binary number to the left or right.
- An arithmetic shift-left (ashl) multiplies a signed binary number by 2.
- An arithmetic shift-right (ashr) divides a signed binary number by 2.
- Arithmetic shifts must leave the sign bit unchanged.

 



Figure 4-11 Arithmetic shift right.




# Arithmetic shift-left

- The arithmetic shift-left insert 0 into  $R_0$ , and shifts all other bits to the left.
- $R_{n-2}$  becomes  $R_{n-1}$  and  $R_{n-1}$  lost and becomes the sign bit.
- A **sign reversal** occurs (overflow) if the bit in  $R_{n-1}$  changes its value after shift.

 Example: a 4 bit signed R : 1 0 0 1 (= -7)




# Shift – HW implementaion

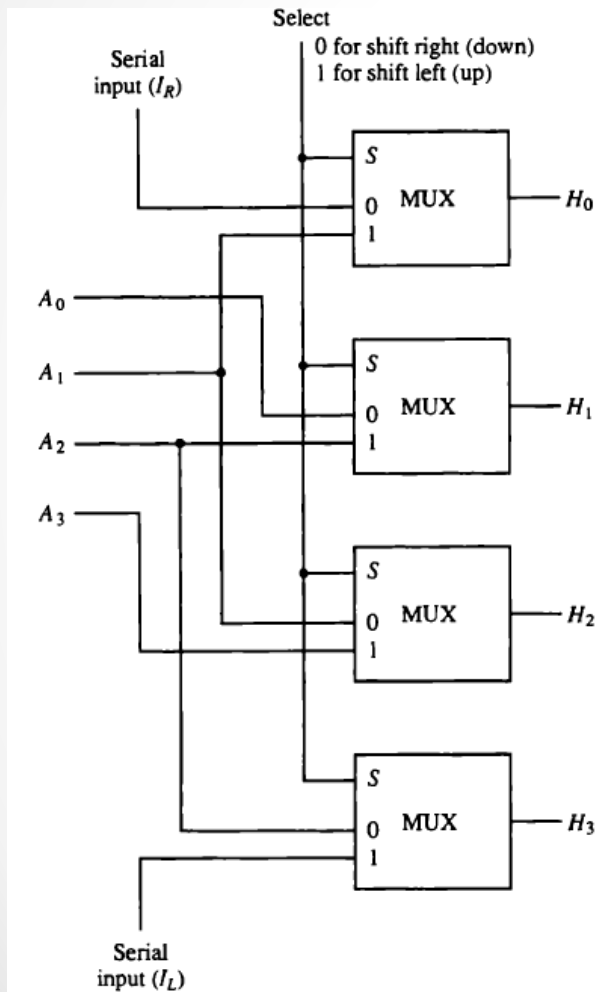

| Function table |        |       |       |       |
|----------------|--------|-------|-------|-------|
| Select         | Output |       |       |       |
| S              | $H_0$  | $H_1$ | $H_2$ | $H_3$ |
| 0              | $I_R$  | $A_0$ | $A_1$ | $A_2$ |
| 1              | $A_1$  | $A_2$ | $A_3$ | $I_L$ |

- When  $S=0$ , the input data is shifted right (down in the diagram).
- When  $S=1$ , the input data is shifted left (up in the diagram).
- A shifter with  $n$  data inputs, requires  $n$  multiplexers.

# ALU - Arithmetical Logical Unit

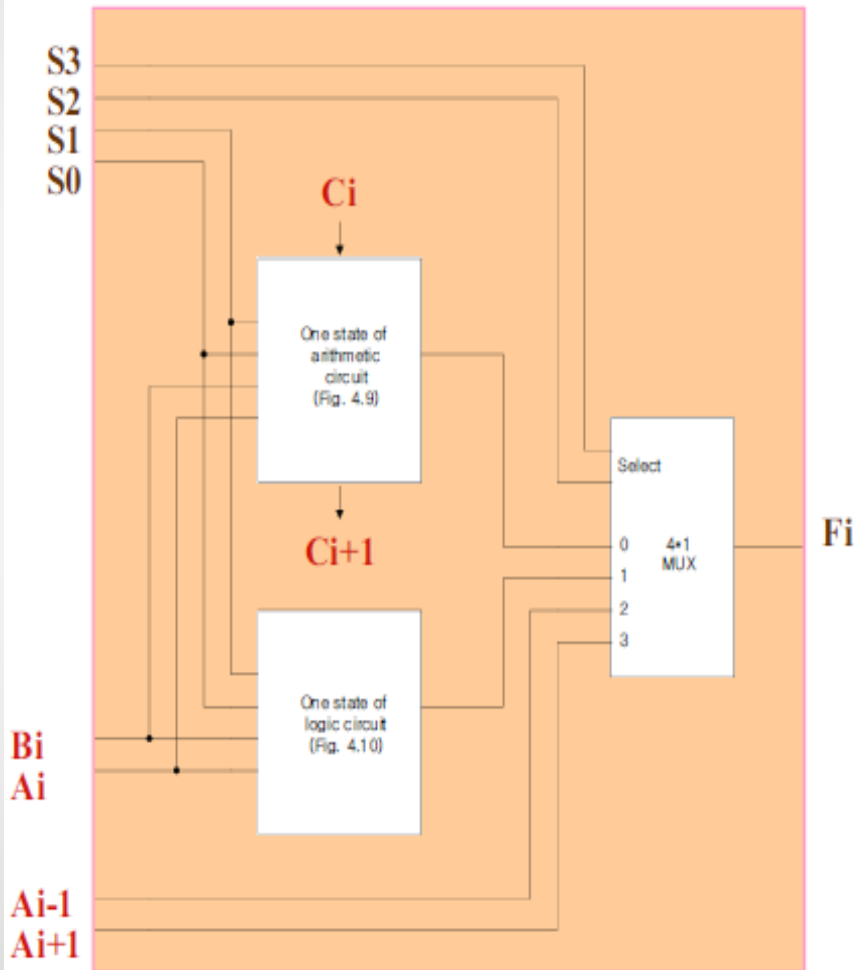

- The contents of specific source registers are placed in the input of the ALU.
- The ALU performs the operation, and the result is then transferred to a destination register.
- The ALU is a combinational circuit, therefore the data transferred from source to destination through the ALU is performed during one clock pulse period.

# ALU - Arithmetical Logical Unit

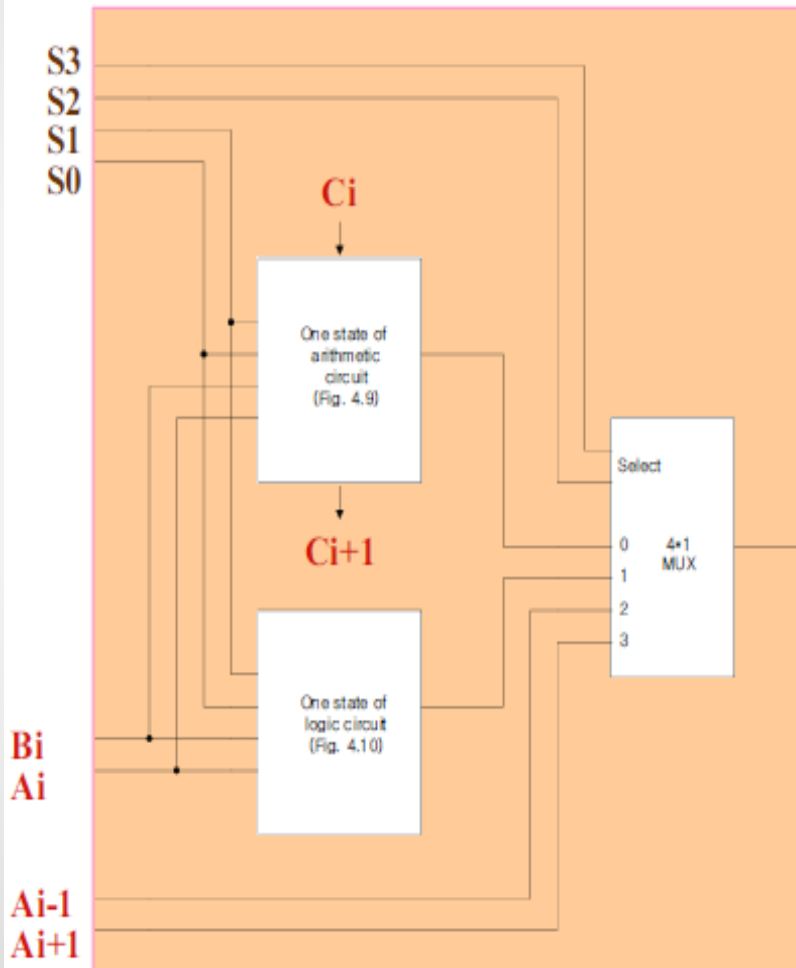


TABLE 4-8 Function Table for Arithmetic Logic Shift Unit

| Operation select |       |       |       |          | Operation             | Function                 |
|------------------|-------|-------|-------|----------|-----------------------|--------------------------|
| $S_3$            | $S_2$ | $S_1$ | $S_0$ | $C_{in}$ |                       |                          |
| 0                | 0     | 0     | 0     | 0        | $F = A$               | Transfer $A$             |
| 0                | 0     | 0     | 0     | 1        | $F = A + 1$           | Increment $A$            |
| 0                | 0     | 0     | 1     | 0        | $F = A + B$           | Addition                 |
| 0                | 0     | 0     | 1     | 1        | $F = A + B + 1$       | Add with carry           |
| 0                | 0     | 1     | 0     | 0        | $F = A + \bar{B}$     | Subtract with borrow     |
| 0                | 0     | 1     | 0     | 1        | $F = A + \bar{B} + 1$ | Subtraction              |
| 0                | 0     | 1     | 1     | 0        | $F = A - 1$           | Decrement $A$            |
| 0                | 0     | 1     | 1     | 1        | $F = A$               | Transfer $A$             |
| 0                | 1     | 0     | 0     | x        | $F = A \wedge B$      | AND                      |
| 0                | 1     | 0     | 1     | x        | $F = A \vee B$        | OR                       |
| 0                | 1     | 1     | 0     | x        | $F = A \oplus B$      | XOR                      |
| 0                | 1     | 1     | 1     | x        | $F = \bar{A}$         | Complement $A$           |
| 1                | 0     | x     | x     | x        | $F = \text{shr } A$   | Shift right $A$ into $F$ |
| 1                | 1     | x     | x     | x        | $F = \text{shl } A$   | Shift left $A$ into $F$  |

# ALU - Arithmetical Logical Unit

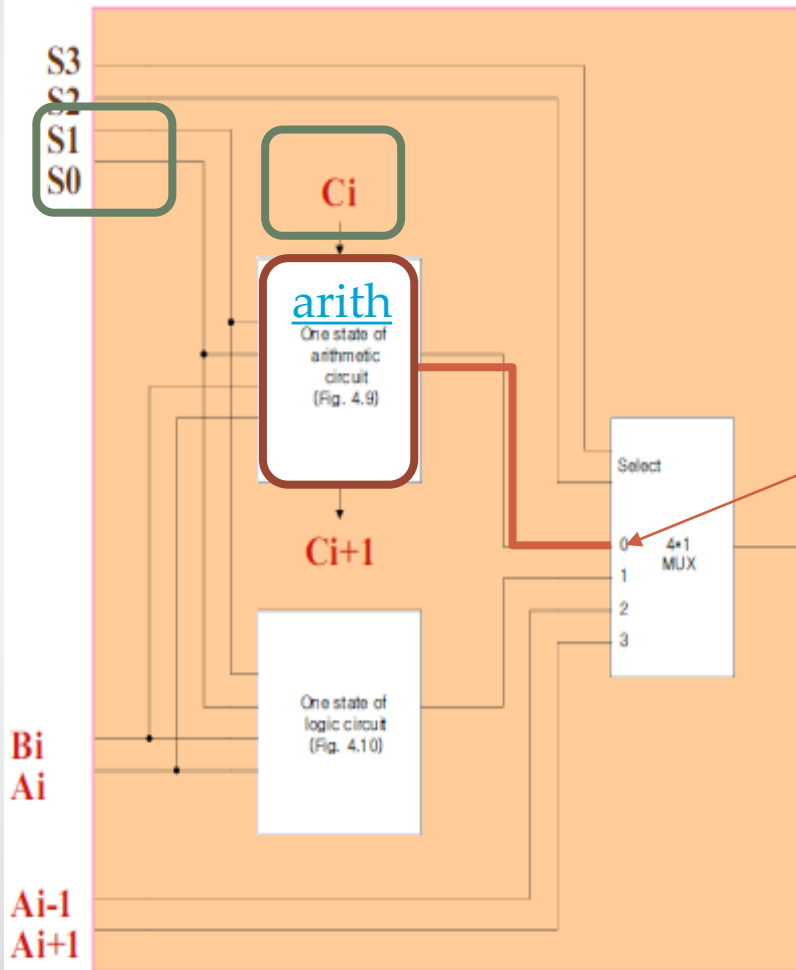


TABLE 4-8 Function Table for Arithmetic Logic Shift Unit

| Operation select |       |       |       |          | Operation             | Function                 |
|------------------|-------|-------|-------|----------|-----------------------|--------------------------|
| $S_3$            | $S_2$ | $S_1$ | $S_0$ | $C_{in}$ |                       |                          |
| 0                | 0     | 0     | 0     | 0        | $F = A$               | Transfer $A$             |
| 0                | 0     | 0     | 0     | 1        | $F = A + 1$           | Increment $A$            |
| 0                | 0     | 0     | 1     | 0        | $F = A + B$           | Addition                 |
| 0                | 0     | 0     | 1     | 1        | $F = A + B + 1$       | Add with carry           |
| 0                | 0     | 1     | 0     | 0        | $F = A + \bar{B}$     | Subtract with borrow     |
| 0                | 0     | 1     | 0     | 1        | $F = A + \bar{B} + 1$ | Subtraction              |
| 0                | 0     | 1     | 1     | 0        | $F = A - 1$           | Decrement $A$            |
| 0                | 0     | 1     | 1     | 1        | $F = A$               | Transfer $A$             |
| 0                | 1     | 0     | 0     | x        | $F = A \wedge B$      | AND                      |
| 0                | 1     | 0     | 1     | x        | $F = A \vee B$        | OR                       |
| 0                | 1     | 1     | 0     | x        | $F = A \oplus B$      | XOR                      |
| 0                | 1     | 1     | 1     | x        | $F = \bar{A}$         | Complement $A$           |
| 1                | 0     | x     | x     | x        | $F = \text{shr } A$   | Shift right $A$ into $F$ |
| 1                | 1     | x     | x     | x        | $F = \text{shl } A$   | Shift left $A$ into $F$  |

# ALU - Arithmetical Logical Unit

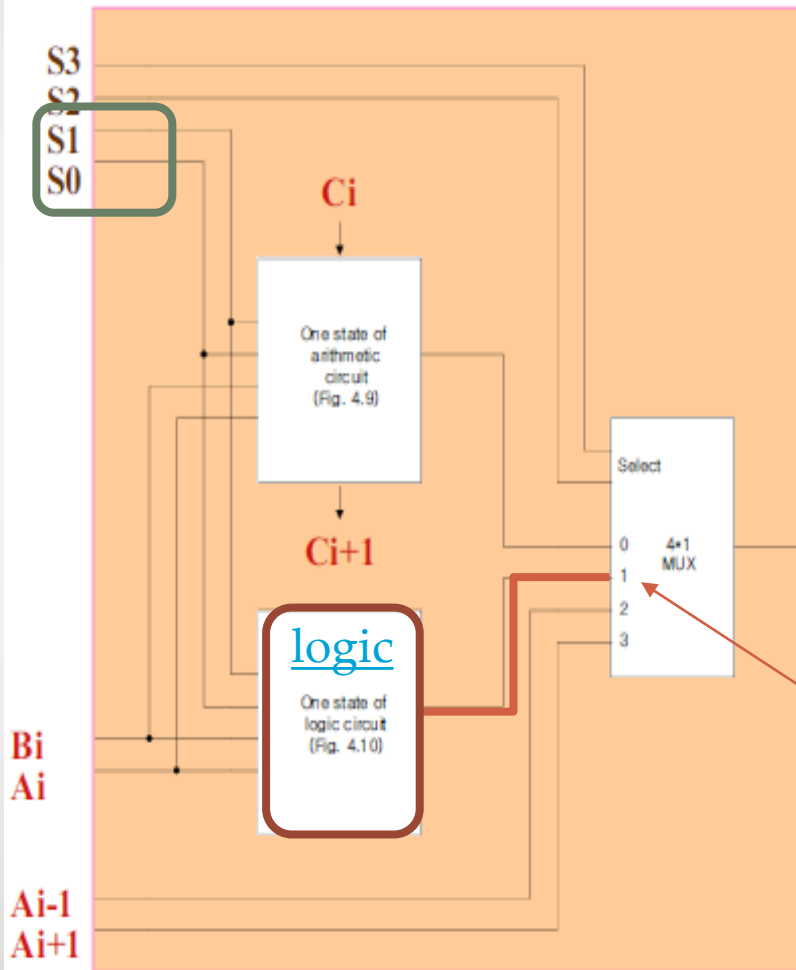


TABLE 4-8 Function Table for Arithmetic Logic Shift Unit

| Operation select |       |       |       |          | Operation             | Function                 |
|------------------|-------|-------|-------|----------|-----------------------|--------------------------|
| $S_3$            | $S_2$ | $S_1$ | $S_0$ | $C_{in}$ |                       |                          |
| 0                | 0     | 0     | 0     | 0        | $F = A$               | Transfer $A$             |
| 0                | 0     | 0     | 0     | 1        | $F = A + 1$           | Increment $A$            |
| 0                | 0     | 0     | 1     | 0        | $F = A + B$           | Addition                 |
| 0                | 0     | 0     | 1     | 1        | $F = A + B + 1$       | Add with carry           |
| 0                | 0     | 1     | 0     | 0        | $F = A + \bar{B}$     | Subtract with borrow     |
| 0                | 0     | 1     | 0     | 1        | $F = A + \bar{B} + 1$ | Subtraction              |
| 0                | 0     | 1     | 1     | 0        | $F = A - 1$           | Decrement $A$            |
| 0                | 0     | 1     | 1     | 1        | $F = A$               | Transfer $A$             |
| 0                | 1     | 0     | 0     | x        | $F = A \wedge B$      | AND                      |
| 0                | 1     | 0     | 1     | x        | $F = A \vee B$        | OR                       |
| 0                | 1     | 1     | 0     | x        | $F = A \oplus B$      | XOR                      |
| 0                | 1     | 1     | 1     | x        | $F = \bar{A}$         | Complement $A$           |
| 1                | 0     | x     | x     | x        | $F = shr A$           | Shift right $A$ into $F$ |
| 1                | 1     | x     | x     | x        | $F = shl A$           | Shift left $A$ into $F$  |

# ALU - Arithmetical Logical Unit

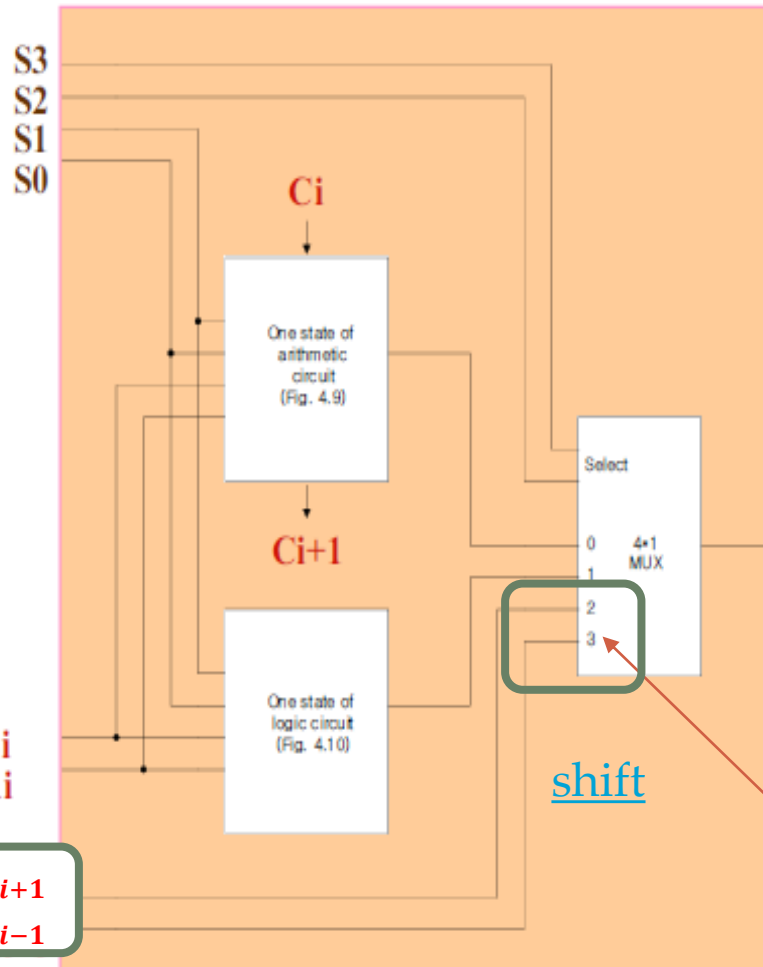


TABLE 4-8 Function Table for Arithmetic Logic Shift Unit

| Operation select |       |       |       |          | Operation             | Function                 |
|------------------|-------|-------|-------|----------|-----------------------|--------------------------|
| $S_3$            | $S_2$ | $S_1$ | $S_0$ | $C_{in}$ |                       |                          |
| 0                | 0     | 0     | 0     | 0        | $F = A$               | Transfer $A$             |
| 0                | 0     | 0     | 0     | 1        | $F = A + 1$           | Increment $A$            |
| 0                | 0     | 0     | 1     | 0        | $F = A + B$           | Addition                 |
| 0                | 0     | 0     | 1     | 1        | $F = A + B + 1$       | Add with carry           |
| 0                | 0     | 1     | 0     | 0        | $F = A + \bar{B}$     | Subtract with borrow     |
| 0                | 0     | 1     | 0     | 1        | $F = A + \bar{B} + 1$ | Subtraction              |
| 0                | 0     | 1     | 1     | 0        | $F = A - 1$           | Decrement $A$            |
| 0                | 0     | 1     | 1     | 1        | $F = A$               | Transfer $A$             |
| 0                | 1     | 0     | 0     | x        | $F = A \wedge B$      | AND                      |
| 0                | 1     | 0     | 1     | x        | $F = A \vee B$        | OR                       |
| 0                | 1     | 1     | 0     | x        | $F = A \oplus B$      | XOR                      |
| 0                | 1     | 1     | 1     | x        | $F = \bar{A}$         | Complement $A$           |
| 1                | 0     | x     | x     | x        | $F = \text{shr } A$   | Shift right $A$ into $F$ |
| 1                | 1     | x     | x     | x        | $F = \text{shl } A$   | Shift left $A$ into $F$  |