

# Computer Architecture Lec 5b

Dr. Esti Stein

(Partly taken from Dr. Alon Schclar slides)

Based on slides by:  
**Prof. Myung-Eui Lee**

Korea University of Technology & Education  
Department of Information & Communication

Taken from: **M.  
Mano/Computer Design and  
Architecture 3<sup>rd</sup> Ed.**

# Summary of Control Functions & Microoperations

Fetch	$R'T_0:$	$AR \leftarrow PC$
	$R'T_1:$	$IR \leftarrow M[AR], \quad PC \leftarrow PC + 1$
Decode	$R'T_2:$	$D_0, \dots, D_7 \leftarrow \text{Decode } IR(12-14),$ $AR \leftarrow IR(0-11), \quad I \leftarrow IR(15)$
Indirect	$D_7IT_3:$	$AR \leftarrow M[AR]$
Interrupt:		
	$T_0T_1T_2(IEN)(FGI + FGO):$	$R \leftarrow 1$
	$RT_0:$	$AR \leftarrow 0, \quad TR \leftarrow PC$
	$RT_1:$	$M[AR] \leftarrow TR, \quad PC \leftarrow 0$
	$RT_2:$	$PC \leftarrow PC + 1, \quad IEN \leftarrow 0, \quad R \leftarrow 0, \quad SC \leftarrow 0$
Memory-reference:		
AND	$D_0T_4:$	$DR \leftarrow M[AR]$
	$D_0T_5:$	$AC \leftarrow AC \wedge DR, \quad SC \leftarrow 0$
ADD	$D_1T_4:$	$DR \leftarrow M[AR]$
	$D_1T_5:$	$AC \leftarrow AC + DR, \quad E \leftarrow C_{out}, \quad SC \leftarrow 0$
LDA	$D_2T_4:$	$DR \leftarrow M[AR]$
	$D_2T_5:$	$AC \leftarrow DR, \quad SC \leftarrow 0$
STA	$D_3T_4:$	$M[AR] \leftarrow AC, \quad SC \leftarrow 0$
BUN	$D_4T_4:$	$PC \leftarrow AR, \quad SC \leftarrow 0$
BSA	$D_5T_4:$	$M[AR] \leftarrow PC, \quad AR \leftarrow AR + 1$
	$D_5T_5:$	$PC \leftarrow AR, \quad SC \leftarrow 0$
ISZ	$D_6T_4:$	$DR \leftarrow M[AR]$
	$D_6T_5:$	$DR \leftarrow DR + 1$
	$D_6T_6:$	$M[AR] \leftarrow DR, \quad \text{if } (DR = 0) \text{ then } (PC \leftarrow PC + 1), \quad SC \leftarrow 0$

# Summary of Control Functions & Microoperations

## Register-reference:

	$D_7I'T_3 = r$ (common to all register-reference instructions)
	$IR(i) = B_i$ ( $i = 0, 1, 2, \dots, 11$ )
	$r:$ $SC \leftarrow 0$
CLA	$rB_{11}: AC \leftarrow 0$
CLE	$rB_{10}: E \leftarrow 0$
CMA	$rB_9: AC \leftarrow \overline{AC}$
CME	$rB_8: E \leftarrow \overline{E}$
CIR	$rB_7: AC \leftarrow \text{shr } AC, AC(15) \leftarrow E, E \leftarrow AC(0)$
CIL	$rB_6: AC \leftarrow \text{shl } AC, AC(0) \leftarrow E, E \leftarrow AC(15)$
INC	$rB_5: AC \leftarrow AC + 1$
SPA	$rB_4: \text{If } (AC(15) = 0) \text{ then } (PC \leftarrow PC + 1)$
SNA	$rB_3: \text{If } (AC(15) = 1) \text{ then } (PC \leftarrow PC + 1)$
SZA	$rB_2: \text{If } (AC = 0) \text{ then } PC \leftarrow PC + 1$
SZE	$rB_1: \text{If } (E = 0) \text{ then } (PC \leftarrow PC + 1)$
HLT	$rB_0: S \leftarrow 0$

## Input-output:

	$D_7IT_3 = p$ (common to all input-output instructions)
	$IR(i) = B_i$ ( $i = 6, 7, 8, 9, 10, 11$ )
	$p:$ $SC \leftarrow 0$
INP	$pB_{11}: AC(0-7) \leftarrow INPR, FGI \leftarrow 0$
OUT	$pB_{10}: OUTR \leftarrow AC(0-7), FGO \leftarrow 0$
SKI	$pB_9: \text{If } (FGI = 1) \text{ then } (PC \leftarrow PC + 1)$
SKO	$pB_8: \text{If } (FGO = 1) \text{ then } (PC \leftarrow PC + 1)$
ION	$pB_7: IEN \leftarrow 1$
IOF	$pB_6: IEN \leftarrow 0$

# The Basic Computer Components


1. A memory unit with 4096 words of 16 bits each
2. Nine registers: *AR*, *PC*, *DR*, *AC*, *IR*, *TR*, *OUTR*, *INPR*, and *SC*
3. Seven flip-flops: *I*, *S*, *E*, *R*, *IEN*, *FGI*, and *FGO* (**JK or D**).
4. Two decoders: a  $3 \times 8$  operation decoder and a  $4 \times 16$  timing decoder
5. A 16-bit common bus with 16  $8 \times 1$  multiplexers
6. Control logic gates
7. Adder and logic circuit connected to the input of *AC*

# Control Logic Gates

The inputs to this circuit comes from:


1. I
2. IR (11:0)
3. AC (15:0) [is AC = 0, is AC < 0, is AC ≥ 0]
4. DR (15:0) [ is DR = 0]
5. S, E, R, IEN, FGI, FGO

S E R IEN FGI FGO

 

Control Logic Block Diagram

# Control Logic Gates

 

1. Signals to control the inputs of the nine registers
2. Signals to control the read and write inputs of memory
3. Signals to set, clear, or complement the flip-flops
4. Signals for  $S_2$ ,  $S_1$ , and  $S_0$  to select a register for the bus
5. Signals to control the AC adder and logic circuit

# Control of Registers

Here, the control inputs of a register  $R_i$  are:

**LD ( $R_i$ ), INC ( $R_i$ ), CLR ( $R_i$ )**

Register with INC, LD, CLR


 


Figure 2-11 4-bit binary counter with parallel load and synchronous clear.

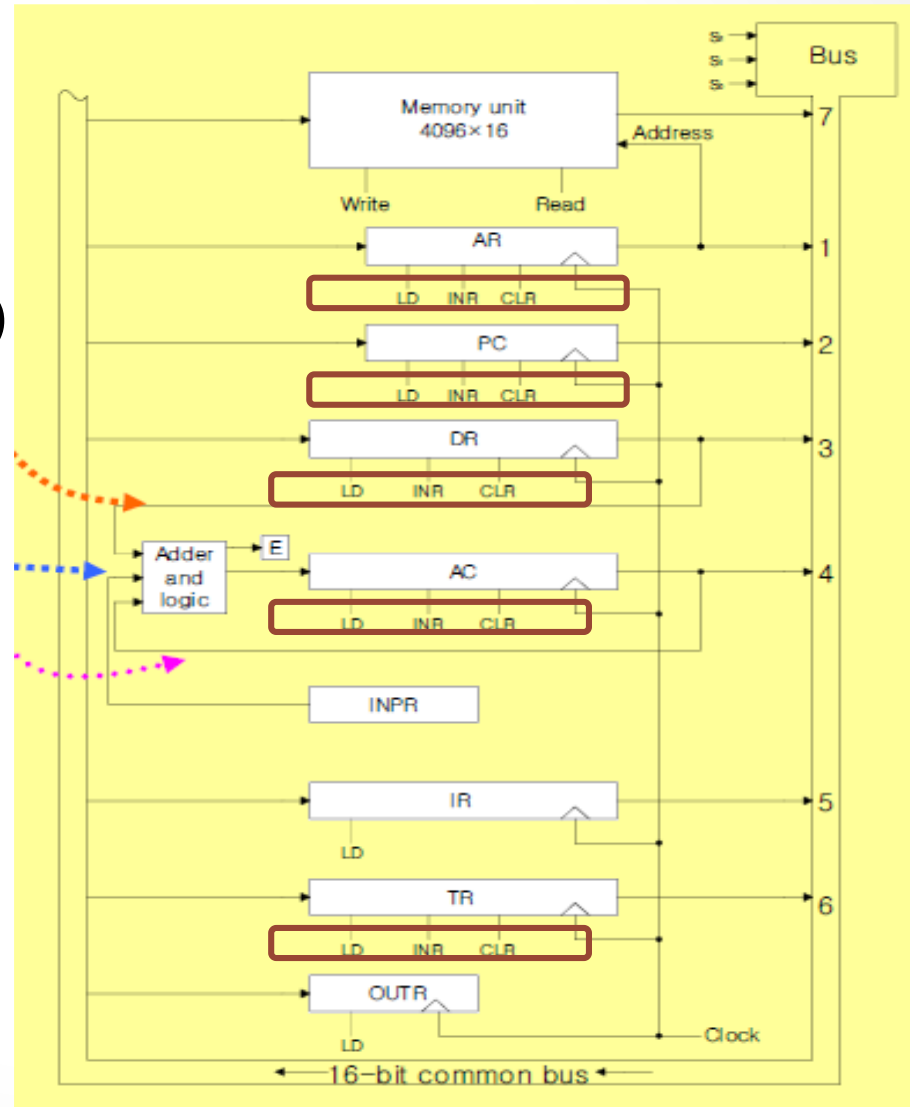



# Control of Registers – AR(1)

Look for statements that change the content of the register

Fetch	$R'T_0$ :	$AR \leftarrow PC$
	$R'T_1$ :	$IR \leftarrow M[AR], \quad PC \leftarrow PC + 1$
Decode	$R'T_2$ :	$D_0, \dots, D_7 \leftarrow \text{Decode } IR(12-14),$ $AR \leftarrow IR(0-1), \quad I \leftarrow IR(15)$
Indirect	$D_7IT_3$ :	$AR \leftarrow M[AR]$
Interrupt:	$T_0T_1T_2(IEN)(FGI + FGO)$ :	$R \leftarrow 1$
	$RT_0$ :	$AR \leftarrow 0, \quad TR \leftarrow PC$
	$RT_1$ :	$M[AR] \leftarrow TR, \quad PC \leftarrow 0$
	$RT_2$ :	$PC \leftarrow PC + 1, \quad IEN \leftarrow 0, \quad R \leftarrow 0, \quad SC \leftarrow 0$
Memory-reference:		
AND	$D_0T_4$ :	$DR \leftarrow M[AR]$
	$D_0T_5$ :	$AC \leftarrow AC \wedge DR, \quad SC \leftarrow 0$
ADD	$D_1T_4$ :	$DR \leftarrow M[AR]$
	$D_1T_5$ :	$AC \leftarrow AC + DR, \quad E \leftarrow C_{out}, \quad SC \leftarrow 0$
LDA	$D_2T_4$ :	$DR \leftarrow M[AR]$
	$D_2T_5$ :	$AC \leftarrow DR, \quad SC \leftarrow 0$
STA	$D_3T_4$ :	$M[AR] \leftarrow AC, \quad SC \leftarrow 0$
BUN	$D_4T_4$ :	$PC \leftarrow AR, \quad SC \leftarrow 0$
BSA	$D_5T_4$ :	$M[AR] \leftarrow PC, \quad AR \leftarrow AR + 1$
	$D_5T_5$ :	$PC \leftarrow AR, \quad SC \leftarrow 0$
ISZ	$D_6T_4$ :	$DR \leftarrow M[AR]$
	$D_6T_5$ :	$DR \leftarrow DR + 1$
	$D_6T_6$ :	$M[AR] \leftarrow DR, \quad \text{if } (DR = 0) \text{ then } (PC \leftarrow PC + 1), \quad SC \leftarrow 0$



# Control of Registers – AR(2)

Look for statements that change the content of the register

Register-reference:

NONE

CLA  
CLE  
CMA  
CME  
CIR  
CIL  
INC  
SPA  
SNA  
SZA  
SZE  
HLT

$D_7I'T_3 = r$  (common to all register-reference instructions)

$IR(i) = B_i$  ( $i = 0, 1, 2, \dots, 11$ )

$r:$   $SC \leftarrow 0$   
 $rB_{11}:$   $AC \leftarrow 0$   
 $rB_{10}:$   $E \leftarrow 0$   
 $rB_9:$   $AC \leftarrow \overline{AC}$   
 $rB_8:$   $E \leftarrow \overline{E}$   
 $rB_7:$   $AC \leftarrow \text{shr } AC, \quad AC(15) \leftarrow E, \quad E \leftarrow AC(0)$   
 $rB_6:$   $AC \leftarrow \text{shl } AC, \quad AC(0) \leftarrow E, \quad E \leftarrow AC(15)$   
 $rB_5:$   $AC \leftarrow AC + 1$   
 $rB_4:$  If  $(AC(15) = 0)$  then  $(PC \leftarrow PC + 1)$   
 $rB_3:$  If  $(AC(15) = 1)$  then  $(PC \leftarrow PC + 1)$   
 $rB_2:$  If  $(AC = 0)$  then  $PC \leftarrow PC + 1$   
 $rB_1:$  If  $(E = 0)$  then  $(PC \leftarrow PC + 1)$   
 $rB_0:$   $S \leftarrow 0$

Input-output:

INP  
OUT  
SKI  
SKO  
ION  
IOF


$D_7IT_3 = p$  (common to all input-output instructions)

$IR(i) = B_i$  ( $i = 6, 7, 8, 9, 10, 11$ )

$p:$   $SC \leftarrow 0$   
 $pB_{11}:$   $AC(0-7) \leftarrow INPR, \quad FGI \leftarrow 0$   
 $pB_{10}:$   $OUTR \leftarrow AC(0-7), \quad FGO \leftarrow 0$   
 $pB_9:$  If  $(FGI = 1)$  then  $(PC \leftarrow PC + 1)$   
 $pB_8:$  If  $(FGO = 1)$  then  $(PC \leftarrow PC + 1)$   
 $pB_7:$   $IEN \leftarrow 1$   
 $pB_6:$   $IEN \leftarrow 0$
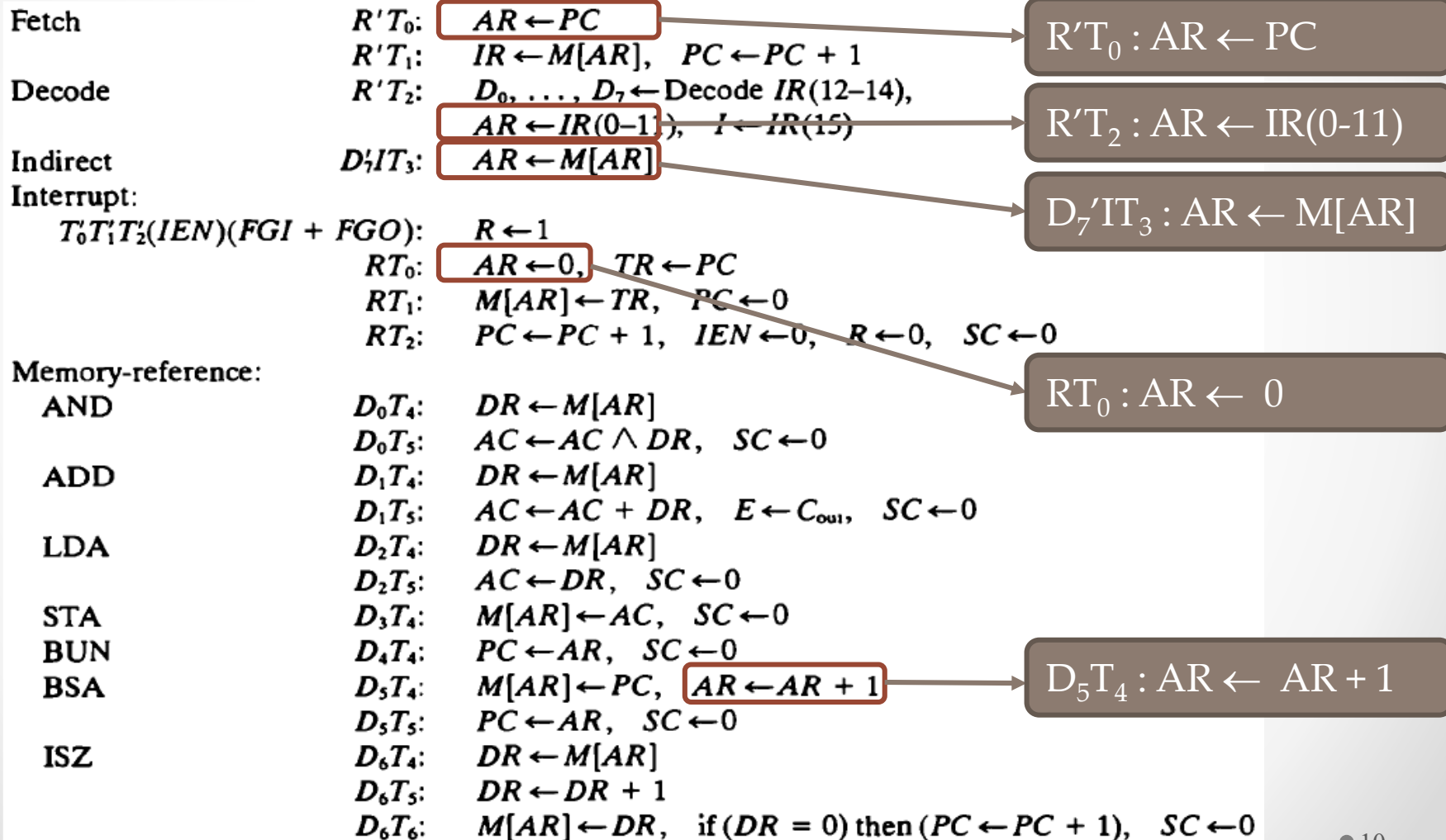
# Control of Registers – AR(3)

Extract the RTL statements that was chosen



# Control of Registers – AR(4)

Divide the RTL statements according to the register control inputs

The control inputs of register AR are:

**LD (R), INC (R), CLR (R)**

$R'T_0 : AR \leftarrow PC$

$R'T_2 : AR \leftarrow IR(0-11)$

$D_7'IT_3 : AR \leftarrow M[AR]$

$LD(R) = R'T_0 + R'T_2 + D_7'IT_3$

$INC(R) = D_5T_4$

$RT_0 : AR \leftarrow 0$

$CLR(R) = RT_0$

$D_5T_4 : AR \leftarrow AR + 1$

# Control of Registers – AR(5)


Construct the logic circle for these inputs

$$\text{LD (R)} = R'T_0 + R'T_2 + D_7'IT_3$$

$$\text{INC (R)} = D_5T_4$$

$$\text{CLR (R)} = RT_0$$


Figure 5-16 Control gates associated with AR.

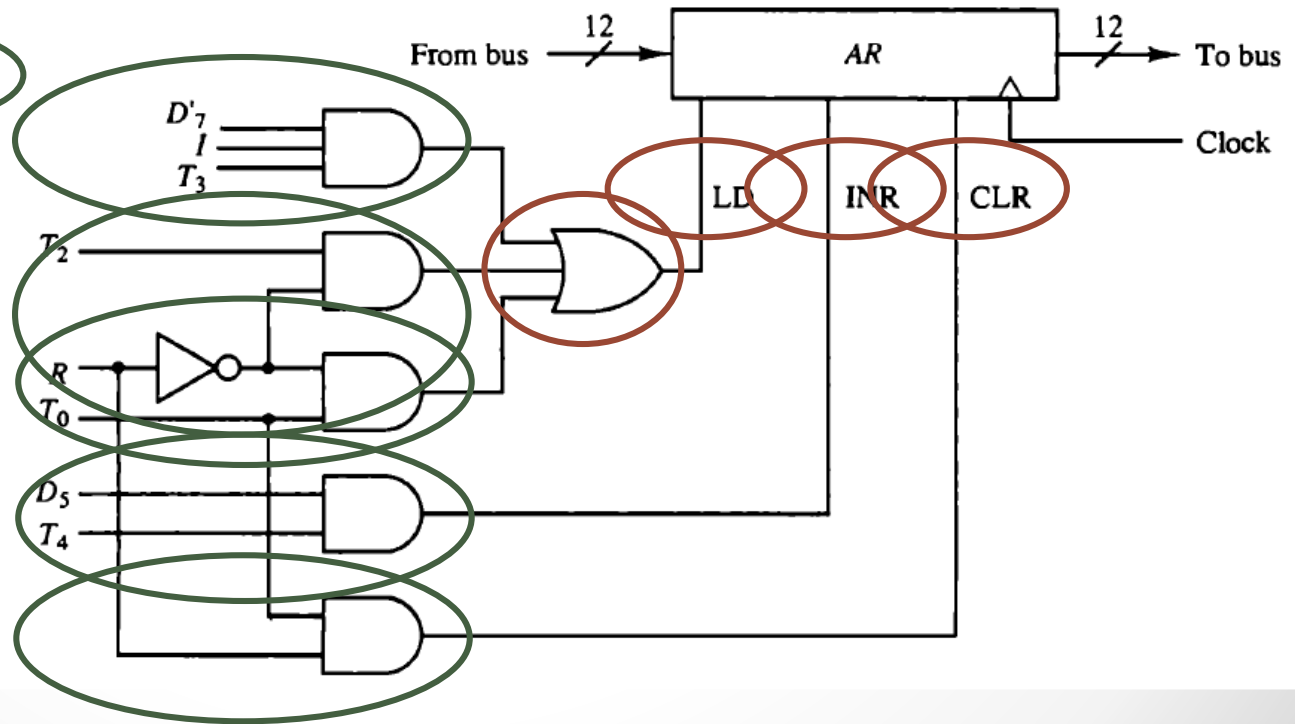

# Control of Memory

Here, the control inputs of the memory are:

**READ, WRITE**

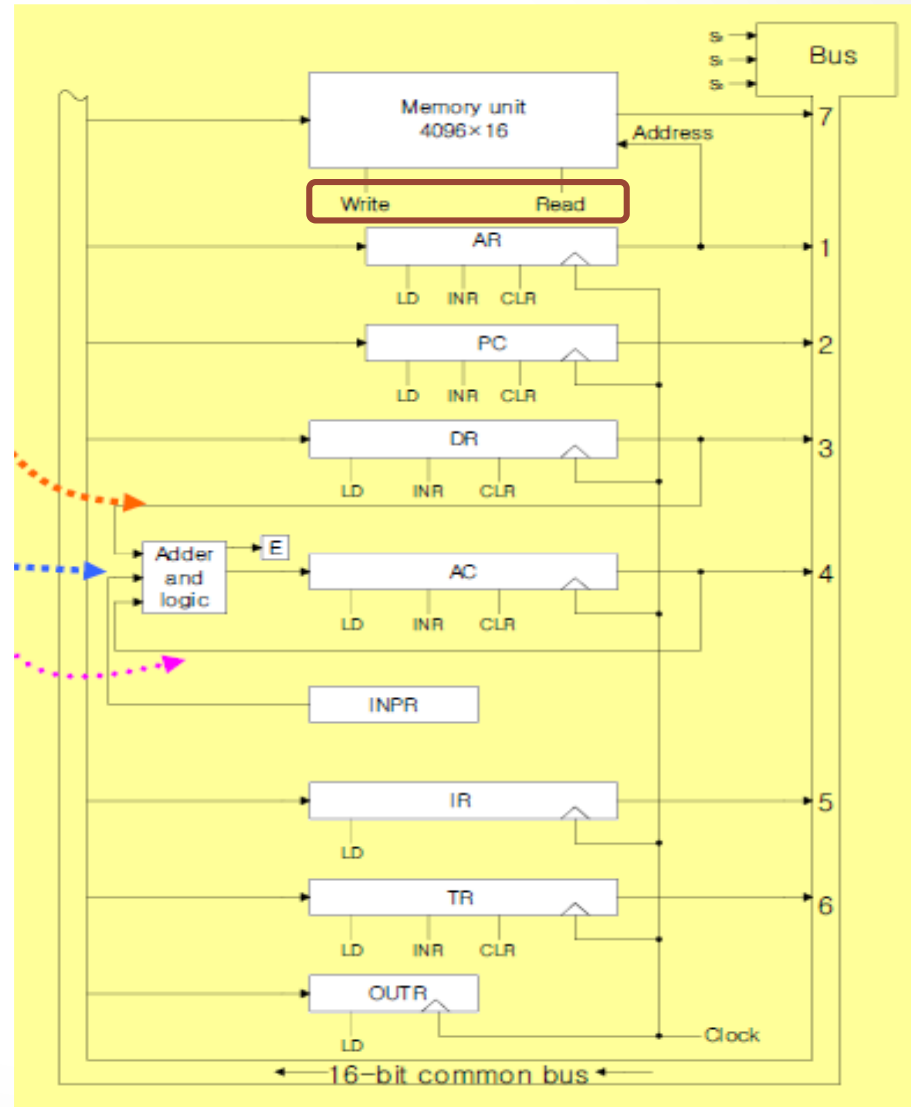

# Control of Memory

Look for statements that READs from the memory:  $\leftarrow M[AR]$

Fetch	$R'T_0:$	$AR \leftarrow PC$
	$R'T_1:$	$IR \leftarrow M[AR], \quad PC \leftarrow PC + 1$
Decode	$R'T_2:$	$D_0, \dots, D_7 \leftarrow \text{Decode } IR(12-14),$ $AR \leftarrow IR(0-11), \quad I \leftarrow IR(15)$
Indirect	$D_7IT_3:$	$AR \leftarrow M[AR]$
Interrupt:		
	$T_0T_1T_2(IEN)(FGI + FGO):$	$R \leftarrow 1$
	$RT_0:$	$AR \leftarrow 0, \quad TR \leftarrow PC$
	$RT_1:$	$M[AR] \leftarrow TR, \quad PC \leftarrow 0$
	$RT_2:$	$PC \leftarrow PC + 1, \quad IEN \leftarrow 0, \quad R \leftarrow 0, \quad SC \leftarrow 0$
Memory-reference:		
AND	$D_0T_4:$	$DR \leftarrow M[AR]$
	$D_0T_5:$	$AC \leftarrow AC \wedge DR, \quad SC \leftarrow 0$
ADD	$D_1T_4:$	$DR \leftarrow M[AR]$
	$D_1T_5:$	$AC \leftarrow AC + DR, \quad E \leftarrow C_{out}, \quad SC \leftarrow 0$
LDA	$D_2T_4:$	$DR \leftarrow M[AR]$
	$D_2T_5:$	$AC \leftarrow DR, \quad SC \leftarrow 0$
STA	$D_3T_4:$	$M[AR] \leftarrow AC, \quad SC \leftarrow 0$
BUN	$D_4T_4:$	$PC \leftarrow AR, \quad SC \leftarrow 0$
BSA	$D_5T_4:$	$M[AR] \leftarrow PC, \quad AR \leftarrow AR + 1$
	$D_5T_5:$	$PC \leftarrow AR, \quad SC \leftarrow 0$
ISZ	$D_6T_4:$	$DR \leftarrow M[AR]$
	$D_6T_5:$	$DR \leftarrow DR + 1$
	$D_6T_6:$	$M[AR] \leftarrow DR, \quad \text{if } (DR = 0) \text{ then } (PC \leftarrow PC + 1), \quad SC \leftarrow 0$

# Control of Memory


$$\text{READ} = R'T_1 + D_7'IT_3 + (D_0 + D_1 + D_2 + D_6)T_4$$

Fetch	$R'T_0:$	$AR \leftarrow PC$
	$R'T_1:$	$IR \leftarrow M[AR], \quad PC \leftarrow PC + 1$
Decode	$R'T_2:$	$D_0, \dots, D_7 \leftarrow \text{Decode } IR(12-14),$ $AR \leftarrow IR(0-11), \quad I \leftarrow IR(15)$
Indirect	$D_7'IT_3:$	$AR \leftarrow M[AR]$
Interrupt:		
	$T_0T_1T_2'(IEN)(FGI + FGO):$	$R \leftarrow 1$
	$RT_0:$	$AR \leftarrow 0, \quad TR \leftarrow PC$
	$RT_1:$	$M[AR] \leftarrow TR, \quad PC \leftarrow 0$
	$RT_2:$	$PC \leftarrow PC + 1, \quad IEN \leftarrow 0, \quad R \leftarrow 0, \quad SC \leftarrow 0$
Memory-reference:		
AND	$D_0T_4:$	$DR \leftarrow M[AR]$
	$D_0T_5:$	$AC \leftarrow AC \wedge DR, \quad SC \leftarrow 0$
ADD	$D_1T_4:$	$DR \leftarrow M[AR]$
	$D_1T_5:$	$AC \leftarrow AC + DR, \quad E \leftarrow C_{out}, \quad SC \leftarrow 0$
LDA	$D_2T_4:$	$DR \leftarrow M[AR]$
	$D_2T_5:$	$AC \leftarrow DR, \quad SC \leftarrow 0$
STA	$D_3T_4:$	$M[AR] \leftarrow AC, \quad SC \leftarrow 0$
BUN	$D_4T_4:$	$PC \leftarrow AR, \quad SC \leftarrow 0$
BSA	$D_5T_4:$	$M[AR] \leftarrow PC, \quad AR \leftarrow AR + 1$
	$D_5T_5:$	$PC \leftarrow AR, \quad SC \leftarrow 0$
ISZ	$D_6T_4:$	$DR \leftarrow M[AR]$
	$D_6T_5:$	$DR \leftarrow DR + 1$
	$D_6T_6:$	$M[AR] \leftarrow DR, \quad \text{if } (DR = 0) \text{ then } (PC \leftarrow PC + 1), \quad SC \leftarrow 0$



# Flip-flop Control

 1. A memory unit with 4096 words of 16 bits each
2. Nine registers: *AR*, *PC*, *DR*, *AC*, *IR*, *TR*, *OUTR*, *INPR*, and *SC*
3. Seven flip-flops: *I*, *S*, *E*, *R*, *IEN*, *FGI*, and *FGO*
4. Two decoders: a  $3 \times 8$  operation decoder and a  $4 \times 16$  timing decoder
5. A 16-bit common bus
6. Control logic gates
7. Adder and logic circuit connected to the input of *AC*



# Flip-flop Control - IEN

Look for statements that change the content of IEN

Fetch	$R'T_0:$	$AR \leftarrow PC$	
	$R'T_1:$	$IR \leftarrow M[AR], \quad PC \leftarrow PC + 1$	
Decode	$R'T_2:$	$D_0, \dots, D_7 \leftarrow \text{Decode } IR(12-14),$ $AR \leftarrow IR(0-11), \quad I \leftarrow IR(15)$	
Indirect	$D_7IT_3:$	$AR \leftarrow M[AR]$	
Interrupt:	$T_0T_1T_2(IEN)(FGI + FGO):$	$R \leftarrow 1$	
	$RT_0:$	$AR \leftarrow 0, \quad TR \leftarrow PC$	
	$RT_1:$	$M[AR] \leftarrow TR, \quad PC \leftarrow 0$	
	$RT_2:$	$PC \leftarrow PC + 1, \quad IEN \leftarrow 0, \quad R \leftarrow 0, \quad SC \leftarrow 0$	$RT_2 : IEN \leftarrow 0$
Memory-reference:			
AND	$D_0T_4:$	$DR \leftarrow M[AR]$	
	$D_0T_5:$	$AC \leftarrow AC \wedge DR, \quad SC \leftarrow 0$	
ADD	$D_1T_4:$	$DR \leftarrow M[AR]$	
	$D_1T_5:$	$AC \leftarrow AC + DR, \quad E \leftarrow C_{out}, \quad SC \leftarrow 0$	
LDA	$D_2T_4:$	$DR \leftarrow M[AR]$	
	$D_2T_5:$	$AC \leftarrow DR, \quad SC \leftarrow 0$	
STA	$D_3T_4:$	$M[AR] \leftarrow AC, \quad SC \leftarrow 0$	
BUN	$D_4T_4:$	$PC \leftarrow AR, \quad SC \leftarrow 0$	
BSA	$D_5T_4:$	$M[AR] \leftarrow PC, \quad AR \leftarrow AR + 1$	
	$D_5T_5:$	$PC \leftarrow AR, \quad SC \leftarrow 0$	
ISZ	$D_6T_4:$	$DR \leftarrow M[AR]$	
	$D_6T_5:$	$DR \leftarrow DR + 1$	
	$D_6T_6:$	$M[AR] \leftarrow DR, \quad \text{if } (DR = 0) \text{ then } (PC \leftarrow PC + 1), \quad SC \leftarrow 0$	

# Flip-flop Control - IEN

Look for statements that change the content of IEN

Register-reference:

CLA  
CLE  
CMA  
CME  
CIR  
CIL  
INC  
SPA  
SNA  
SZA  
SZE  
HLT

$D_7I'T_3 = r$  (common to all register-reference instructions)  
 $IR(i) = B_i$  ( $i = 0, 1, 2, \dots, 11$ )  
 $r$ :  $SC \leftarrow 0$   
 $rB_{11}$ :  $AC \leftarrow 0$   
 $rB_{10}$ :  $E \leftarrow 0$   
 $rB_9$ :  $AC \leftarrow \overline{AC}$   
 $rB_8$ :  $E \leftarrow \overline{E}$   
 $rB_7$ :  $AC \leftarrow \text{shr } AC, \quad AC(15) \leftarrow E, \quad E \leftarrow AC(0)$   
 $rB_6$ :  $AC \leftarrow \text{shl } AC, \quad AC(0) \leftarrow E, \quad E \leftarrow AC(15)$   
 $rB_5$ :  $AC \leftarrow AC + 1$   
 $rB_4$ : If  $(AC(15) = 0)$  then  $(PC \leftarrow PC + 1)$   
 $rB_3$ : If  $(AC(15) = 1)$  then  $(PC \leftarrow PC + 1)$   
 $rB_2$ : If  $(AC = 0)$  then  $PC \leftarrow PC + 1$   
 $rB_1$ : If  $(E = 0)$  then  $(PC \leftarrow PC + 1)$   
 $rB_0$ :  $S \leftarrow 0$

Input-output:

INP  
OUT  
SKI  
SKO  
ION  
IOF

$D_7IT_3 = p$  (common to all input-output instructions)  
 $IR(i) = B_i$  ( $i = 6, 7, 8, 9, 10, 11$ )  
 $p$ :  $SC \leftarrow 0$   
 $pB_{11}$ :  $AC(0-7) \leftarrow INPR, \quad FGI \leftarrow 0$   
 $pB_{10}$ :  $OUTR \leftarrow AC(0-7), \quad FGO \leftarrow 0$   
 $pB_9$ : If  $(FGI = 1)$  then  $(PC \leftarrow PC + 1)$   
 $pB_8$ : If  $(FGO = 1)$  then  $(PC \leftarrow PC + 1)$   
 $pB_7$ :  $IEN \leftarrow 1$   
 $pB_6$ :  $IEN \leftarrow 0$

$pB_7 : IEN \leftarrow 1$

$pB_6 : IEN \leftarrow 0$

$p = D_7IT_3$


## Construct the logic circle for these inputs

[illegible]
 
# QUIZ5

Derive the control gates for the WRITE input of the memory in the basic computer:

- What is the pattern you should look for?
- Write the formula for the WRITE input



# The Bus Control

The bus is controlled by the selection inputs:  
 $S_2 S_1 S_0$


TABLE 5-7 Encoder for Bus Selection Circuit

Inputs							Outputs			Register selected for bus
$x_1$	$x_2$	$x_3$	$x_4$	$x_5$	$x_6$	$x_7$	$S_2$	$S_1$	$S_0$	
0	0	0	0	0	0	0	0	0	0	None
1	0	0	0	0	0	0	0	0	1	AR
0	1	0	0	0	0	0	0	1	0	PC
0	0	1	0	0	0	0	0	1	1	DR
0	0	0	1	0	0	0	1	0	0	AC
0	0	0	0	1	0	0	1	0	1	IR
0	0	0	0	0	1	0	1	1	0	TR
0	0	0	0	0	0	1	1	1	1	Memory

$$S_0 = x_1 + x_3 + x_5 + x_7$$

$$S_1 = x_2 + x_3 + x_6 + x_7$$

$$S_2 = x_4 + x_5 + x_6 + x_7$$

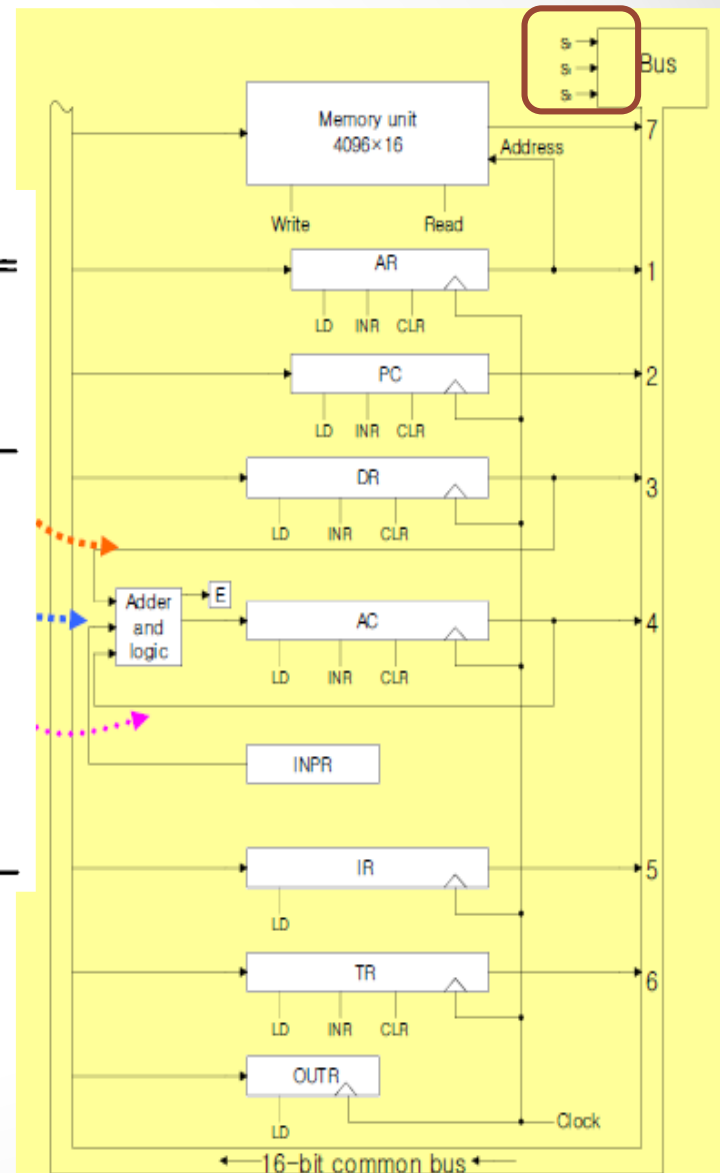

# The Bus Control

The bus is controlled by the selection inputs :  $S_2 S_1 S_0$


$$S_0 = x_1 + x_3 + x_5 + x_7$$

$$S_1 = x_2 + x_3 + x_6 + x_7$$

$$S_2 = x_4 + x_5 + x_6 + x_7$$

When  $x_1 = 1$ , the value of  $S_2S_1S_0$  must be 001, and the output of AR will be selected for the bus.

Look for :  $\dots \leftarrow \text{AR}$

 



# The Bus Control

Fetch	$R'T_0:$	$AR \leftarrow PC$
	$R'T_1:$	$IR \leftarrow M[AR], \quad PC \leftarrow PC + 1$
Decode	$R'T_2:$	$D_0, \dots, D_7 \leftarrow \text{Decode } IR(12-14),$ $AR \leftarrow IR(0-11), \quad I \leftarrow IR(15)$
Indirect	$D_7IT_3:$	$AR \leftarrow M[AR]$
Interrupt:		
	$T_0T_1T_2(IEN)(FGI + FGO):$	$R \leftarrow 1$
	$RT_0:$	$AR \leftarrow 0, \quad TR \leftarrow PC$
	$RT_1:$	$M[AR] \leftarrow TR, \quad PC \leftarrow 0$
	$RT_2:$	$PC \leftarrow PC + 1, \quad IEN \leftarrow 0, \quad R \leftarrow 0, \quad SC \leftarrow 0$
Memory-reference:		
AND	$D_0T_4:$	$DR \leftarrow M[AR]$
	$D_0T_5:$	$AC \leftarrow AC \wedge DR, \quad SC \leftarrow 0$
ADD	$D_1T_4:$	$DR \leftarrow M[AR]$
	$D_1T_5:$	$AC \leftarrow AC + DR, \quad E \leftarrow C_{out}, \quad SC \leftarrow 0$
LDA	$D_2T_4:$	$DR \leftarrow M[AR]$
	$D_2T_5:$	$AC \leftarrow DR, \quad SC \leftarrow 0$
STA	$D_3T_4:$	$M[AR] \leftarrow AC, \quad SC \leftarrow 0$
BUN	$D_4T_4:$	$PC \leftarrow AR, \quad SC \leftarrow 0$
BSA	$D_5T_4:$	$M[AR] \leftarrow PC, \quad AR \leftarrow AR + 1$
	$D_5T_5:$	$PC \leftarrow AR, \quad SC \leftarrow 0$
ISZ	$D_6T_4:$	$DR \leftarrow M[AR]$
	$D_6T_5:$	$DR \leftarrow DR + 1$
	$D_6T_6:$	$M[AR] \leftarrow DR, \quad \text{if } (DR = 0) \text{ then } (PC \leftarrow PC + 1), \quad SC \leftarrow 0$

$$x_1 = D_4T_4 + D_5T_5$$

# The Bus Control


The Boolean functions  
for the Encoder

$$S_0 = x_1 + x_3 + x_5 + x_7$$

$$S_1 = x_2 + x_3 + x_6 + x_7$$

$$S_2 = x_4 + x_5 + x_6 + x_7$$


Figure 5-18 Encoder for bus selection inputs.

 
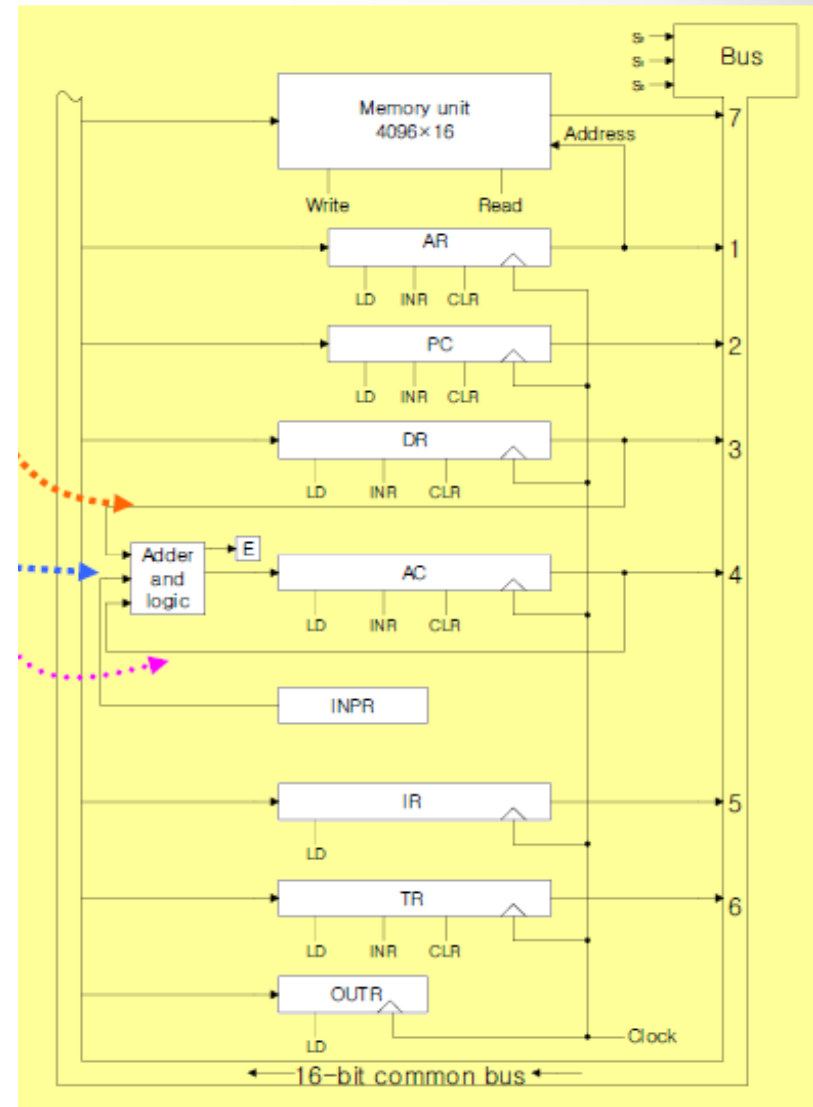
# QUIZ6

Find the logic that makes  $x_7$  to be equal to 1.

- What is the pattern you should look for?
- Write the formula for the  $x_7$  input




# The Basic Computer Components

1. A memory unit with 4096 words of 16 bits each
2. Nine registers: *AR*, *PC*, *DR*, *AC*, *IR*, *TR*, *OUTR*, *INPR*, and *SC*
3. Seven flip-flops: *I*, *S*, *E*, *R*, *IEN*, *FGI*, and *FGO* (**JK or D**).
4. Two decoders: a  $3 \times 8$  operation decoder and a  $4 \times 16$  timing decoder
5. A 16-bit common bus with **16  $8 \times 1$  multiplexers**
6. Control logic gates
7. Adder and logic circuit connected to the input of *AC*

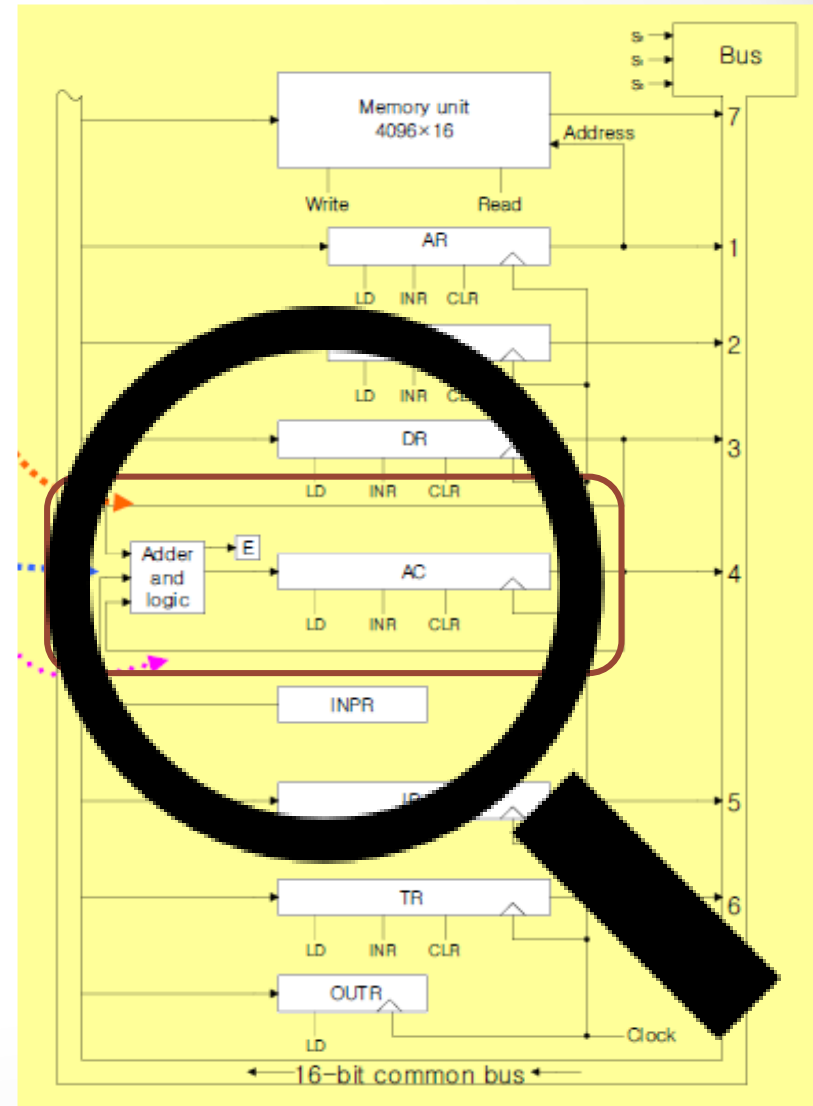
# Design the Accumulator Logic

The circuits associated with the AC register are shown here:



# Design the Accumulator Logic

Figure 5-19 Circuits associated with AC.

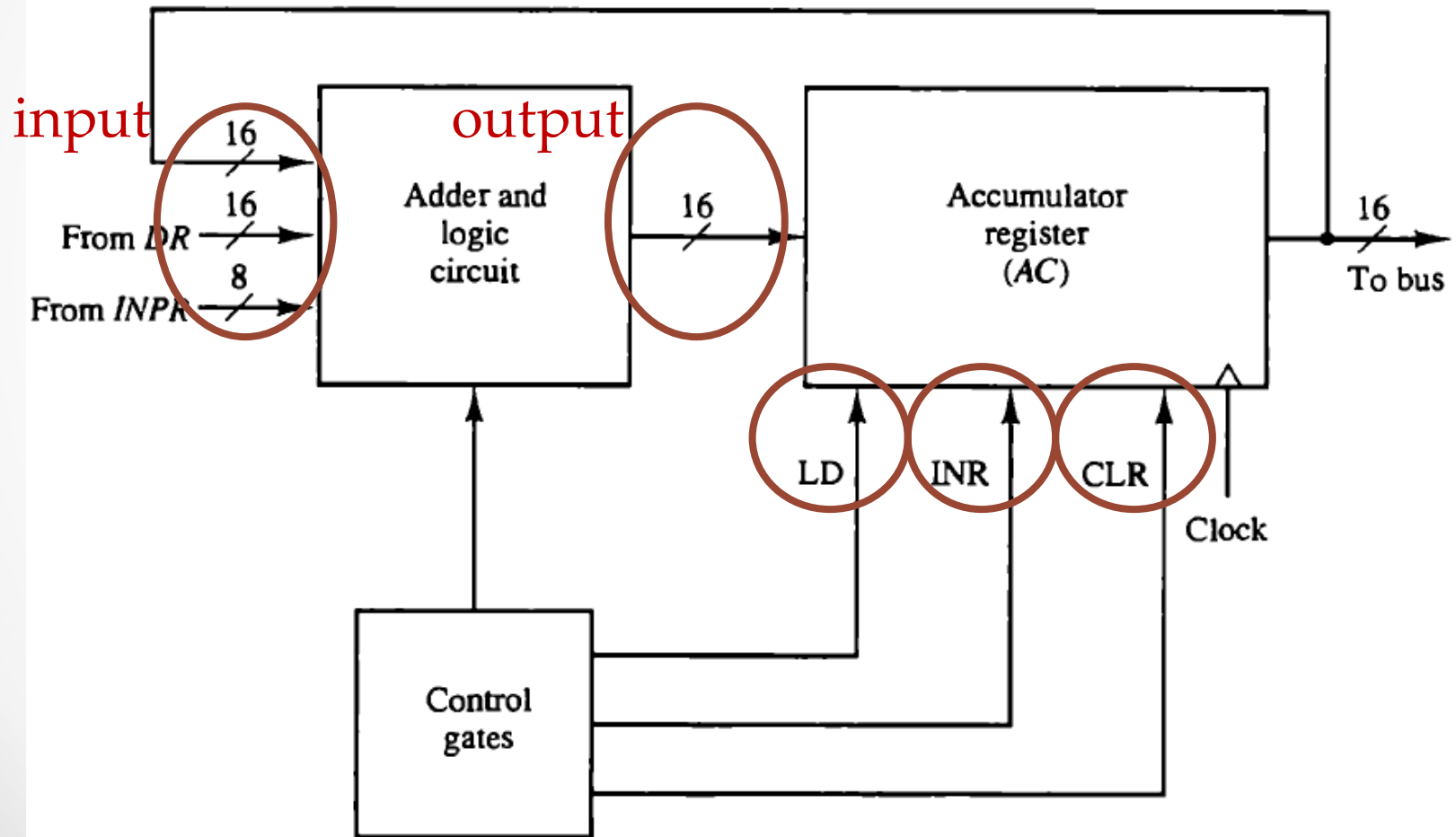

# Design the AC Control


Look for statements that change the AC register

	LOAD	
$D_0T_5:$	$AC \leftarrow AC \wedge DR$	AND with $DR$
$D_1T_5:$	$AC \leftarrow AC + DR$	Add with $DR$
$D_2T_5:$	$AC \leftarrow DR$	Transfer from $DR$
$pB_{11}:$	$AC(0-7) \leftarrow INPR$	Transfer from $INPR$
$rB_9:$	$AC \leftarrow \overline{AC}$	Complement
$rB_7:$	$AC \leftarrow \text{shr } AC, \quad AC(15) \leftarrow E$	Shift right
$rB_6:$	$AC \leftarrow \text{shl } AC, \quad AC(0) \leftarrow E$	Shift left
$rB_{11}:$	$AC \leftarrow 0$	Clear
$rB_5:$	$AC \leftarrow AC + 1$	Increment




# Design the AC Logic

Figure 5-20 Gate structure for controlling the LD, INR, and CLR of AC.

 


# One AC Block, bit $i \in \{0..15\}$

 


The adder and the logic circuit can be subdivided into 16 blocks, with each block corresponding to one bit of AC.

# One AC Block, bit $i \in \{0..15\}$

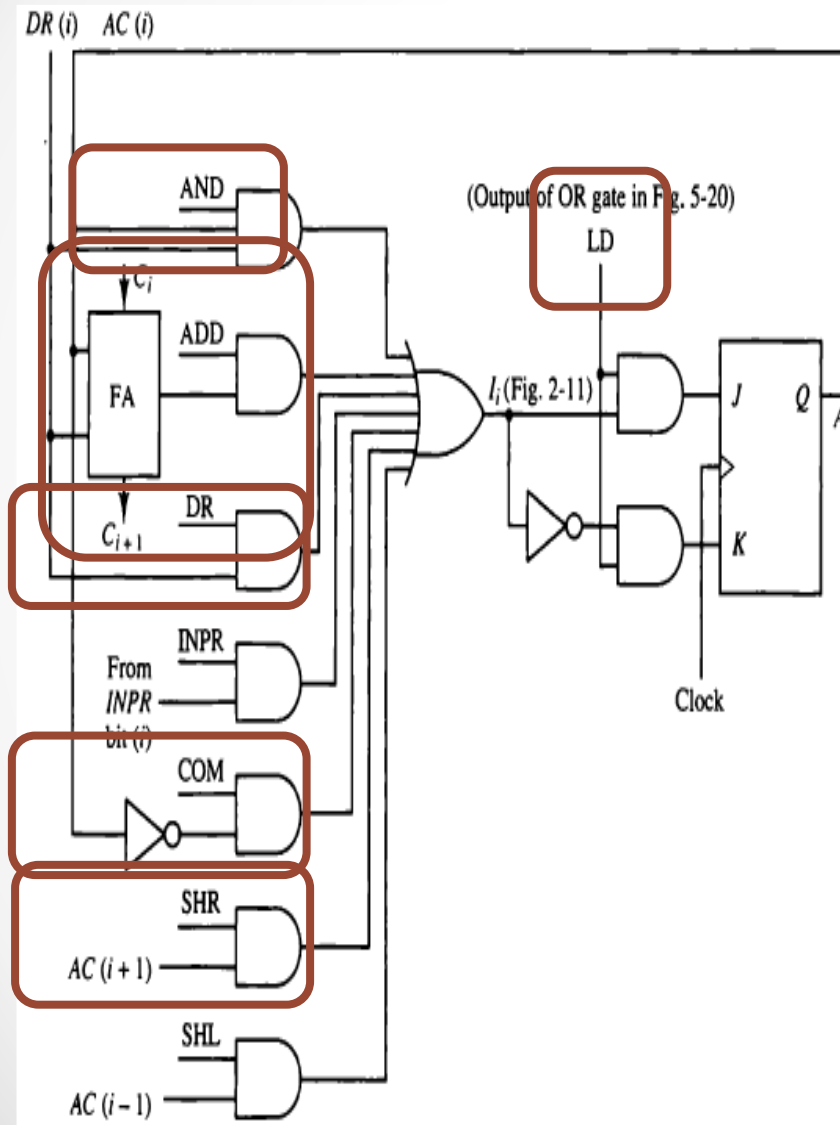

**Figure 5-20** Gate structure for controlling the LD, INR, and CLR of AC.

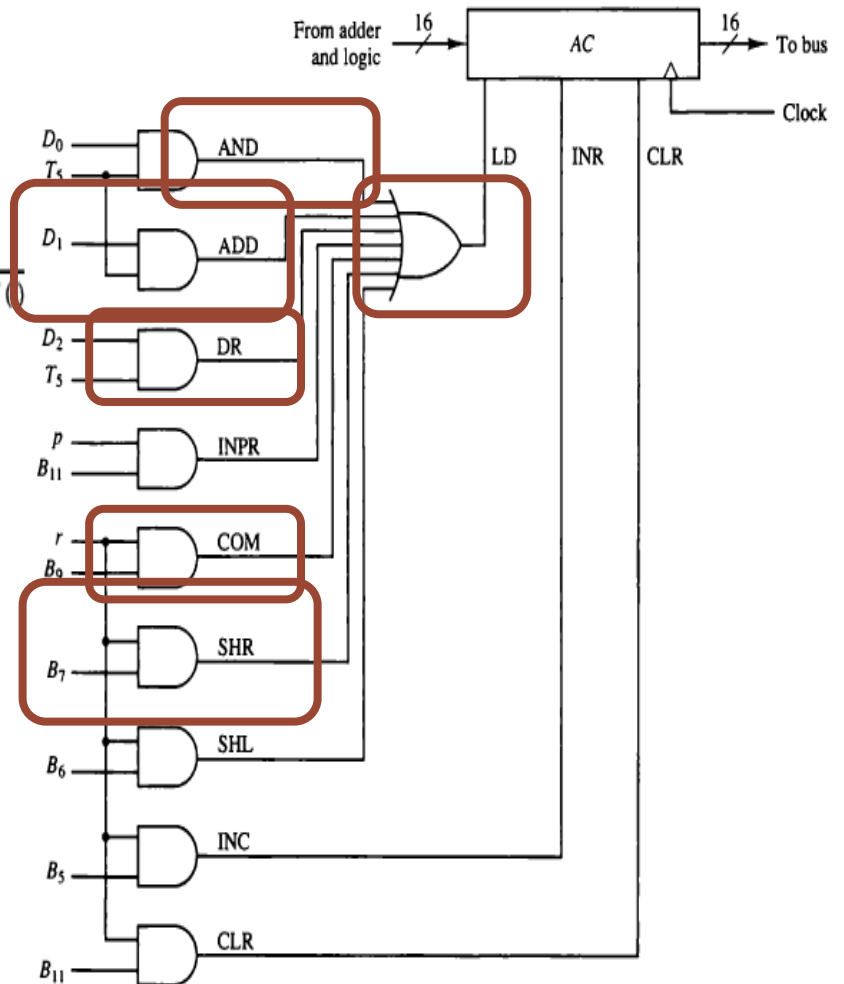

# QUIZ7

The register transfer statements for register R and the memory in a computer are as follows (the X's are control functions):

$X'_3X_1: R \leftarrow M[AR]$     Read memory word into R  
 $X'_1X_2: R \leftarrow AC$     Transfer AC to R  
 $X'_1X_3: M[AR] \leftarrow R$     Write R to memory

- Draw the hardware implementation of R, the memory and AC in block diagram form ( loads into R and memory).
- Show how the control functions  $X_1$  through  $X_3$  select
  - The load control input of R
  - The select inputs of MUXs that you include in the diagram
  - The read and write inputs of the memory

# QUIZ8

Implement the following instruction with operation code of 1:

SB3 :  $AC \leftarrow M[AR] - AC - 3$

Memory-reference:

AND	$D_0T_4:$	$DR \leftarrow M[AR]$
	$D_0T_5:$	$AC \leftarrow AC \wedge DR, \quad SC \leftarrow 0$
ADD	$D_1T_4:$	$DR \leftarrow M[AR]$
	$D_1T_5:$	$AC \leftarrow AC + DR, \quad E \leftarrow C_{out}, \quad SC \leftarrow 0$
LDA	$D_2T_4:$	$DR \leftarrow M[AR]$
	$D_2T_5:$	$AC \leftarrow DR, \quad SC \leftarrow 0$
STA	$D_3T_4:$	$M[AR] \leftarrow AC, \quad SC \leftarrow 0$
BUN	$D_4T_4:$	$PC \leftarrow AR, \quad SC \leftarrow 0$
BSA	$D_5T_4:$	$M[AR] \leftarrow PC, \quad AR \leftarrow AR + 1$
	$D_5T_5:$	$PC \leftarrow AR, \quad SC \leftarrow 0$
ISZ	$D_6T_4:$	$DR \leftarrow M[AR]$
	$D_6T_5:$	$DR \leftarrow DR + 1$
	$D_6T_6:$	$M[AR] \leftarrow DR, \quad \text{if } (DR = 0) \text{ then } (PC \leftarrow PC + 1), \quad SC \leftarrow 0$