

Computer Architecture

Dr. Esti Stein

(Partly taken from Dr. Alon Schclar slides)

Based on slides by:


Prof. Myung-Eui Lee

Korea University of Technology & Education
Department of Information & Communication





Taken from: **M.**

**Mano/Computer Design and
Architecture 3rd Ed.**


Logic Circuits

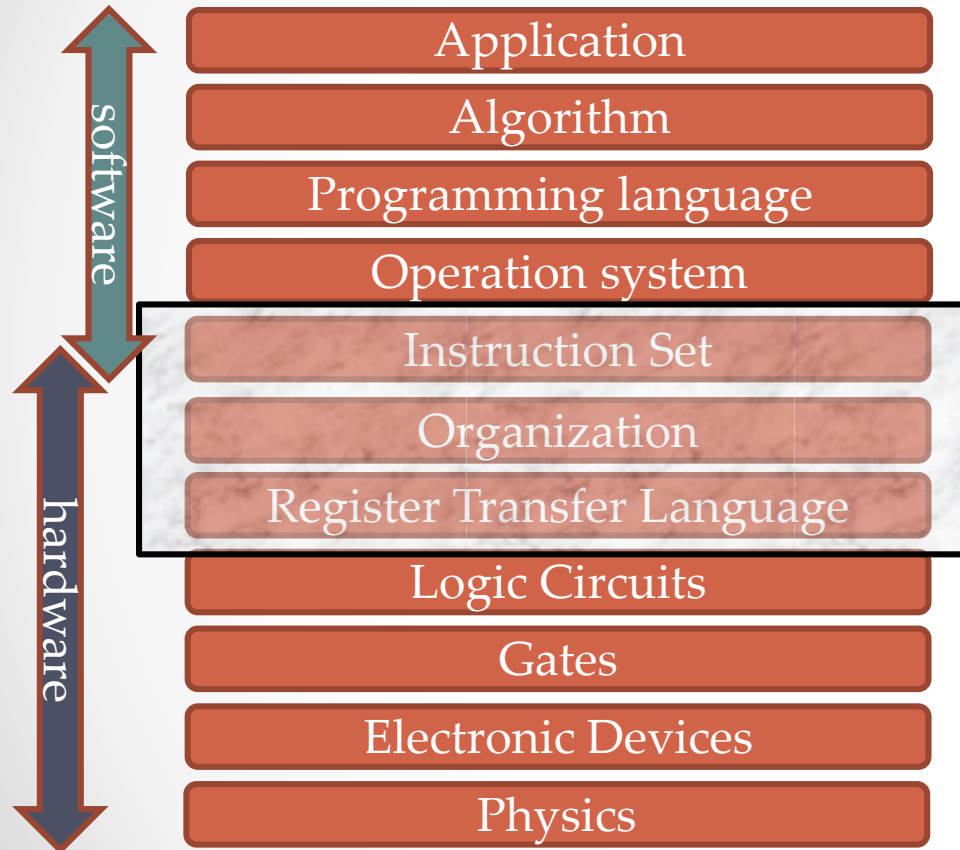

Logic Circuits

 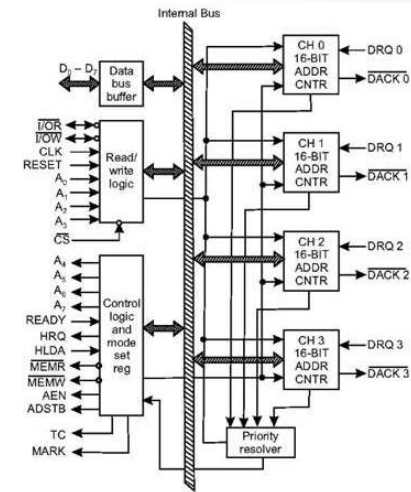 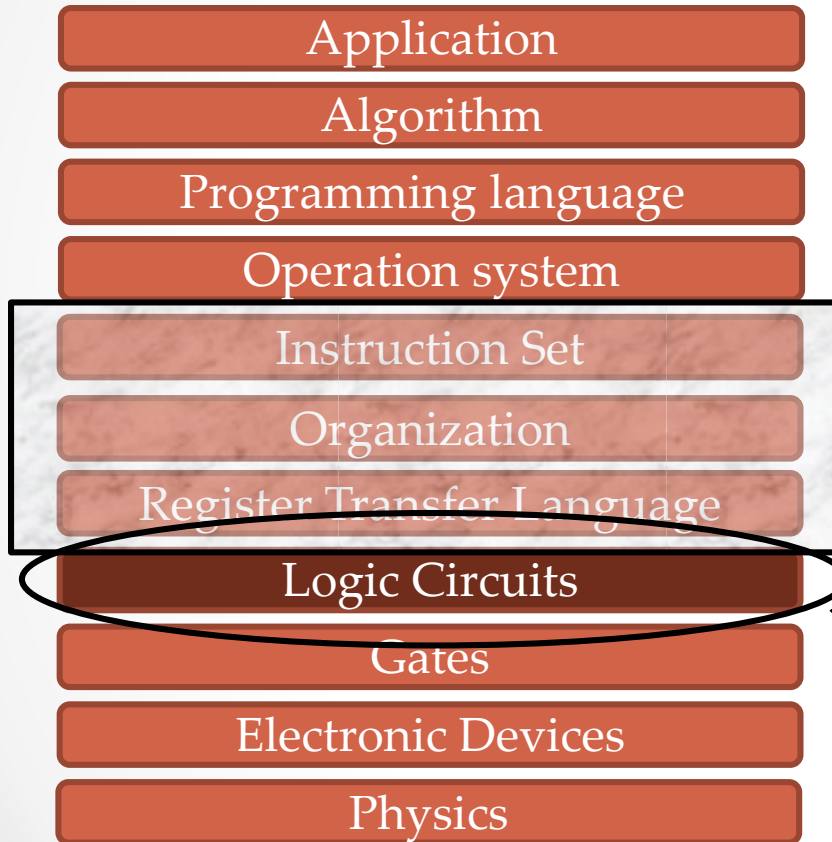

Logic Circuits (LCs)

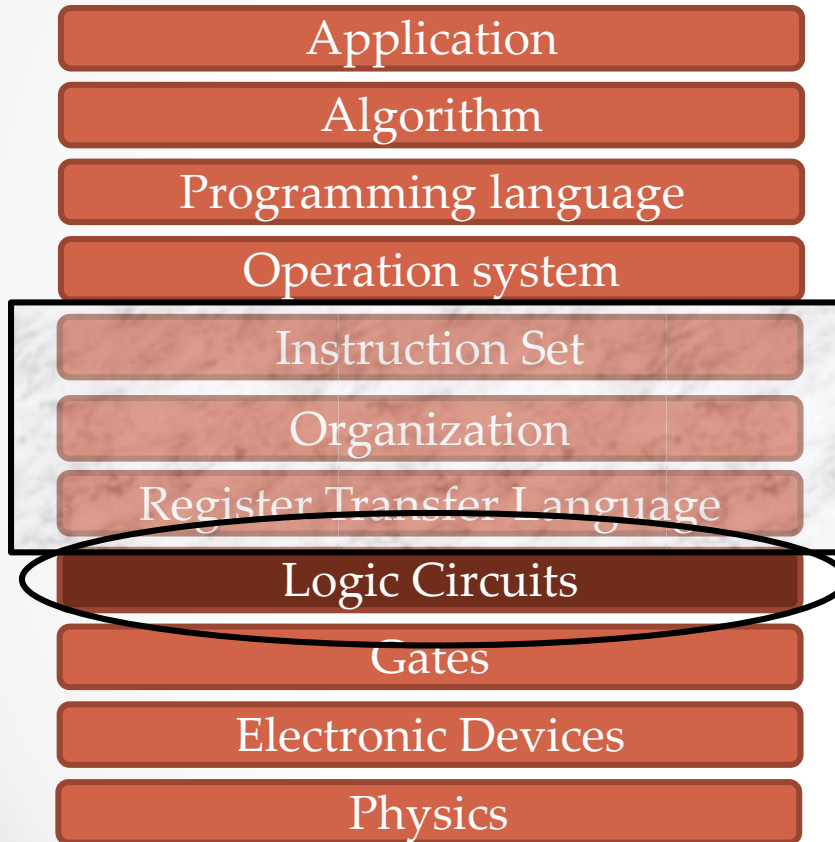

Best defined by:

- their registers
- the data operations on the registers

Microoperations

How to describe LCs


■ 4-1 Register Transfer Language

◆ Microoperation

- The operations executed on data stored in registers (*shift, clear, load, count*)

◆ Internal H/W Organization (*best defined by specifying*)

 1. The set of registers
2. The sequence of microoperations
3. The sequence control of microoperations



The RTL Language

◆ Register Transfer Language

- The **symbolic notation** used to describe the microoperation transfer among registers
 - » The use of **symbols** instead of a **narrative explanation** provides an organized and concise manner
- A convenient tool for describing the internal organization of digital computers in concise and precise manner

Registers


◆ Registers : *Fig. 4-1*

- Designated by Capital Letter(*sometimes followed by numerals*) : MAR(Memory Address Register), PC(Program Counter), IR(Instruction Register), R1(Processor Register)


Figure 4-1 Block diagram of register.




(a) Register *R*

 

(b) Showing individual bits

 

(c) Numbering of bits

 

(d) Divided into two parts


Registers

- The individual F/Fs in an n-bit register : numbered in sequence from 0(*rightmost position*) through n-1
- The numbering of bits in a 16-bit register : marked on top of the box
- A 16-bit register partitioned into two parts : bit 0-7(*symbol "L" Low byte*), bit 8-15(*symbol "H" High byte*)


Figure 4-1 Block diagram of register.




(a) Register *R*

 

(b) Showing individual bits

 

(c) Numbering of bits

 

(d) Divided into two parts

RTL Explanation

◆ Register Transfer : *Information transfer from one register to another*

● $R2 \leftarrow R1$ (*transfer of the content of register R1 into register R2*)

» The content of the source register R1 does not change after the transfer

◆ Control Function : *The transfer occurs only under a predetermined control condition*

● The transfer operation is executed by the hardware only if $P=1$: Fig. 4-2

$$\left. \begin{array}{l} \text{if } (P = 1) \text{ then } (R2 \leftarrow R1) \\ P : R2 \leftarrow R1 \end{array} \right\} =$$

● A comma is used to separate two or more operations (*Executed at the same time*)

$T : R2 \leftarrow R1, R1 \leftarrow R2$


RTL Definition

◆ Basic Symbols for Register Transfer : Tab. 4-1

Symbol	Description	Examples
Letters (and numerals)	Denotes a register	MAR, R2
Parentheses ()	Denotes a part of a register	R2(0-7), R2(L)
Arrow \leftarrow	Denotes transfer of information	R2 \leftarrow R1
Comma ,	Separates two microoperations	R2 \leftarrow R1, R1 \leftarrow R2

Example:

Figure 4-2 Transfer from R1 to R2 when $P = 1$.

 


Meaning:

If P then $R2 \leftarrow R1$

In RTL:

$P : R2 \leftarrow R1$


RTL meaning

 

(b) Timing diagram


Example:

Figure 4-2 Transfer from $R1$ to $R2$ when $P = 1$.

 

$P : R2 \leftarrow R1$

RTL timing

 

- The clock is not included as a variable in the register transfer statements
 - It is assumed that all transfers occur during a clock edge transition.
- The control condition such as ***P*** becomes active just after time ***t***
- The actual transfer occurs when the register is triggered by the next positive transition of the clock at time ***t + 1***.

Reminder

An n-bit counter with parallel load

 


TABLE 2-5 Function Table for the Register of Fig. 2-11

Clock	Clear	Load	Increment	Operation
↑	0	0	0	No change
↑	0	0	1	Increment count by 1
↑	0	1	×	Load inputs I_0 through I_3
↑	1	×	×	Clear outputs to 0

Another Reminder

 


Figure 4-6 4-bit binary adder.

Another Reminder


 


Figure 4-6 4-bit binary adder.

The BUS

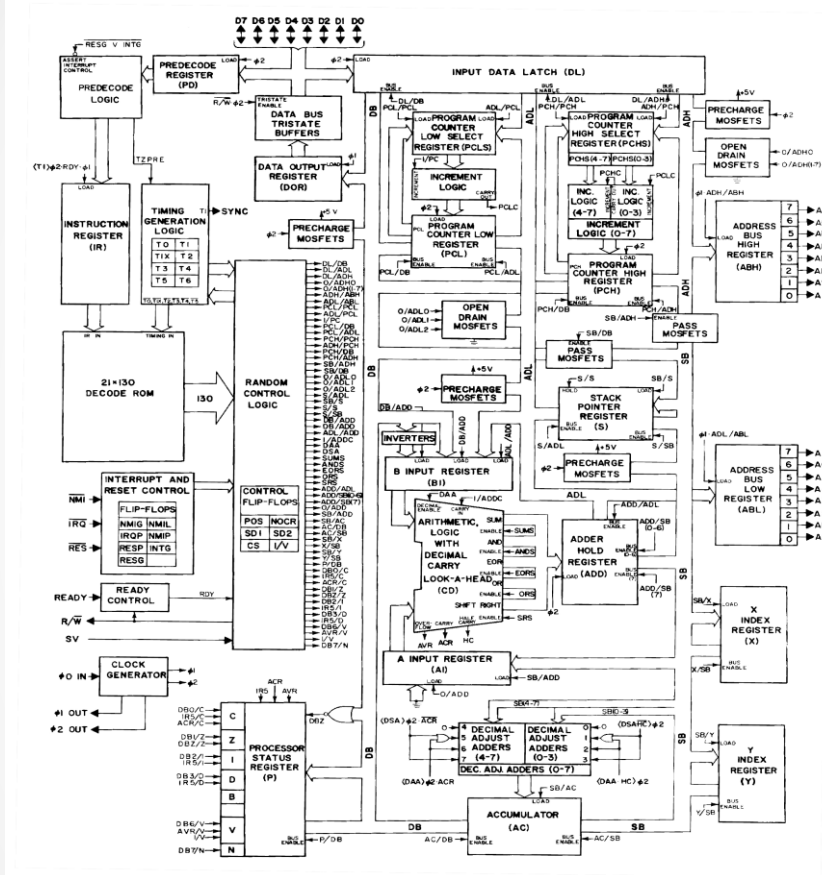


A structure consists of set of common lines (one for each bit of a register) through which data is transferred among them, from one source register at a time.

The 8-bit Z-80 processor was very popular in the late 1970s and early 1980s

The BUS


Control signals determine which source register is selected during each particular register transfer

 A structure consists of set of common lines (one for each bit of a register) through which data is transferred among them, **from one source register at a time.**



The BUS

 
Control signals
determine which
source register is
selected during each
particular register
transfer



$R8 \leftarrow R2$


The BUS

 Control signals
determine which
source register is
selected during each
particular register
transfer




The BUS

Constructed by
using multiplexers

 


The BUS - MUX

Figure 4-3 Bus system for four registers.

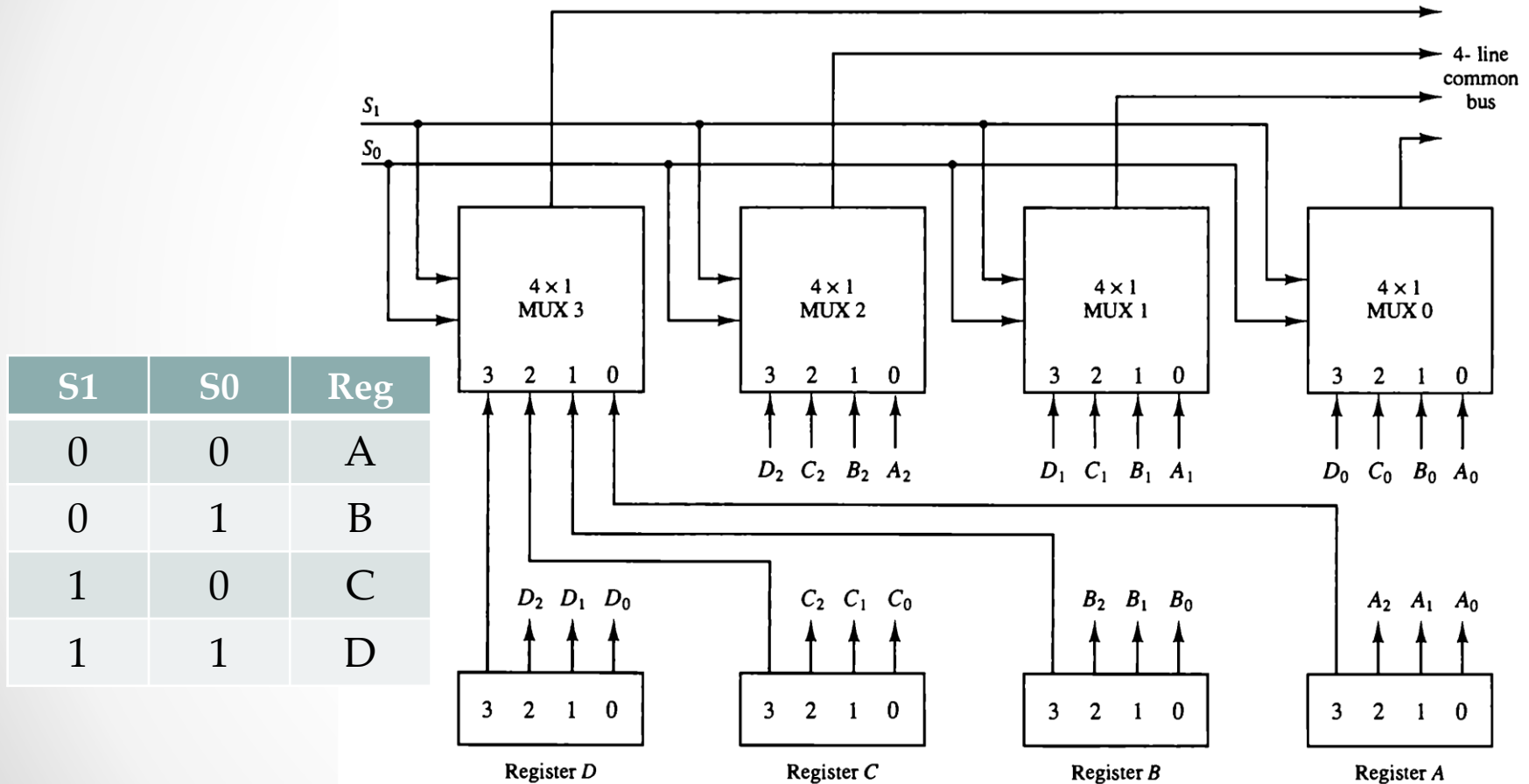


The BUS Transfer in RTL

 - The content of register C is placed on the bus, and the content of the bus is loaded into register R1 by activating its load control input




Simply $R8 \leftarrow R2$

 

The BUS


Constructed by
using Tri-states

 

The BUS – Tristate

- Tri-state buffer gate : Fig. 4-4

 
- » When control input =1 : The output is enabled(output Y = input A) **2 logic states**
- » When control input =0 : The output is disabled(output Y = high-impedance)




A	C	Output
0	0	high imp.
0	1	0
1	0	high imp.
1	1	1

The BUS - MUX

Figure 4-3 Bus system for four registers.

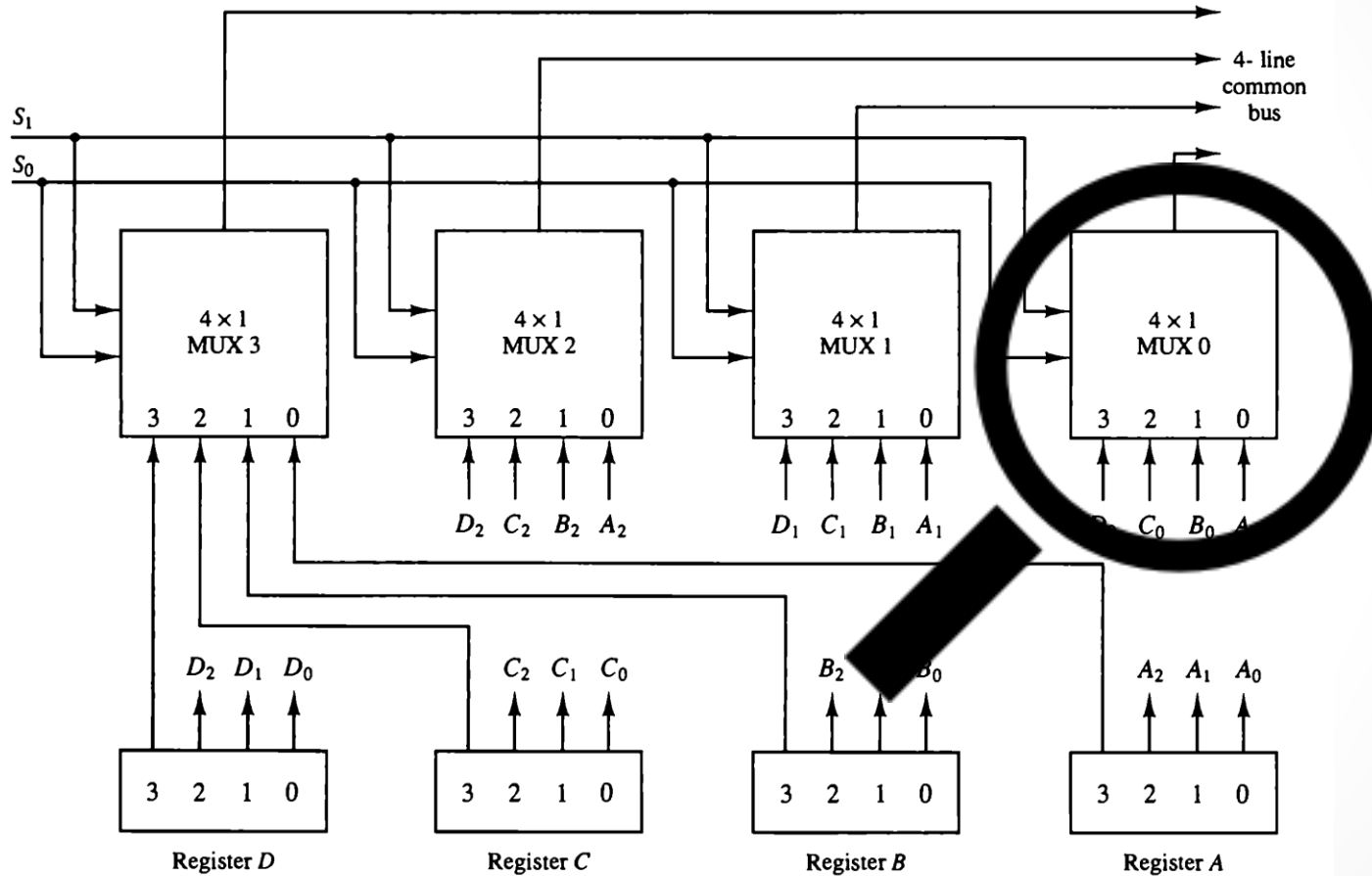


Construct a MUX with a Tristate

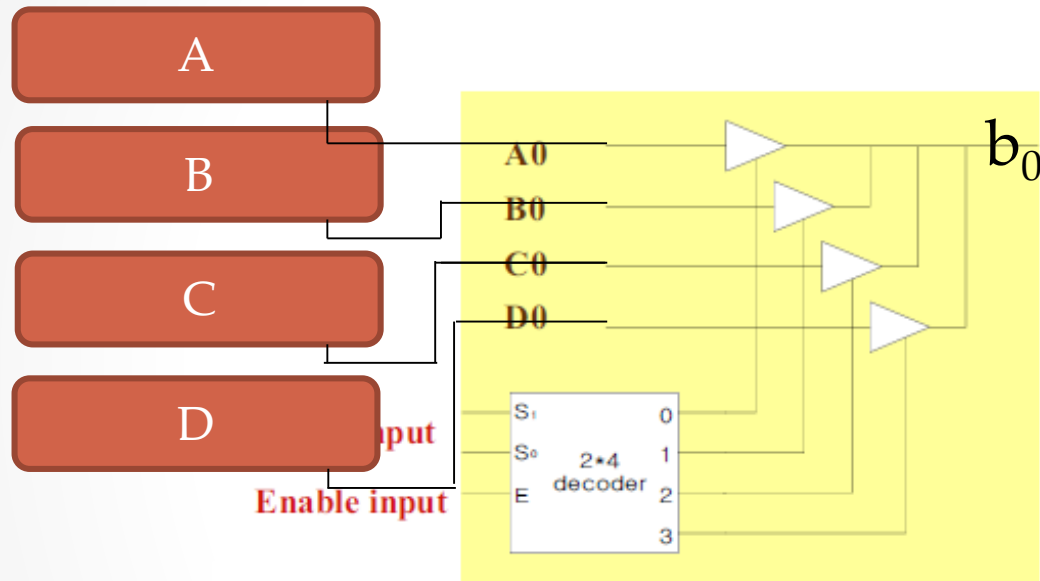


A bus line for
one bit

The MEMORY

 

The MEMORY - read

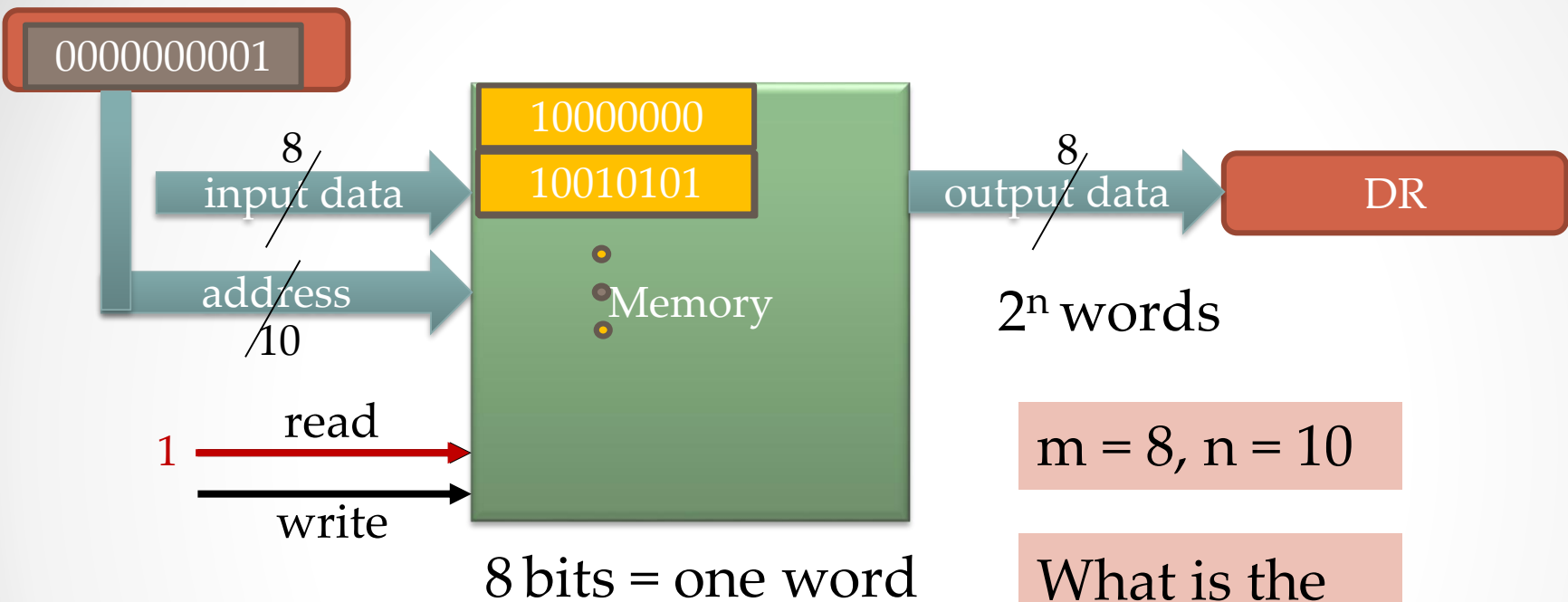


$$m = 8, n = 10$$

What is the size of the memory in bits? $2^{10} \times 8$

Read in RTL is $DR \leftarrow M[AR]$

The MEMORY - write

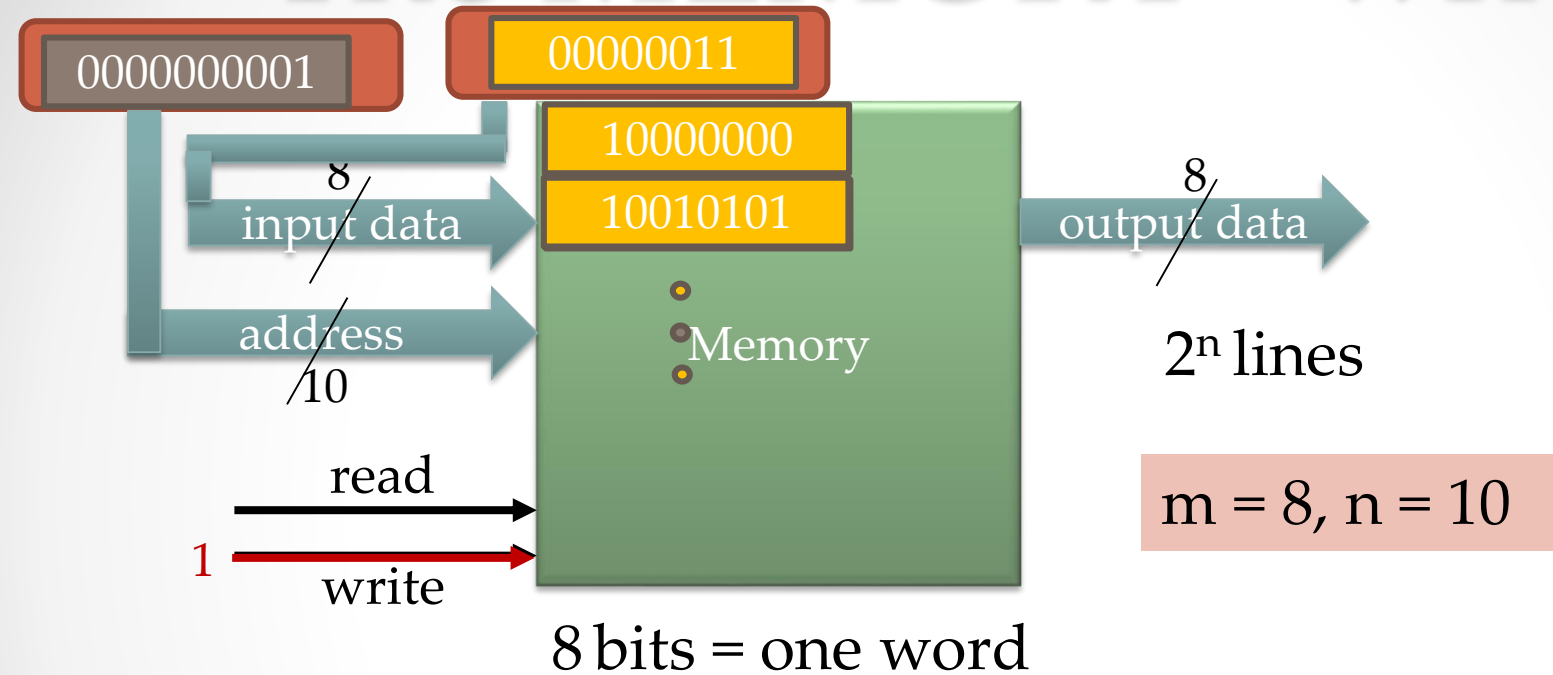

write in RTL is $M[AR] \leftarrow R1$