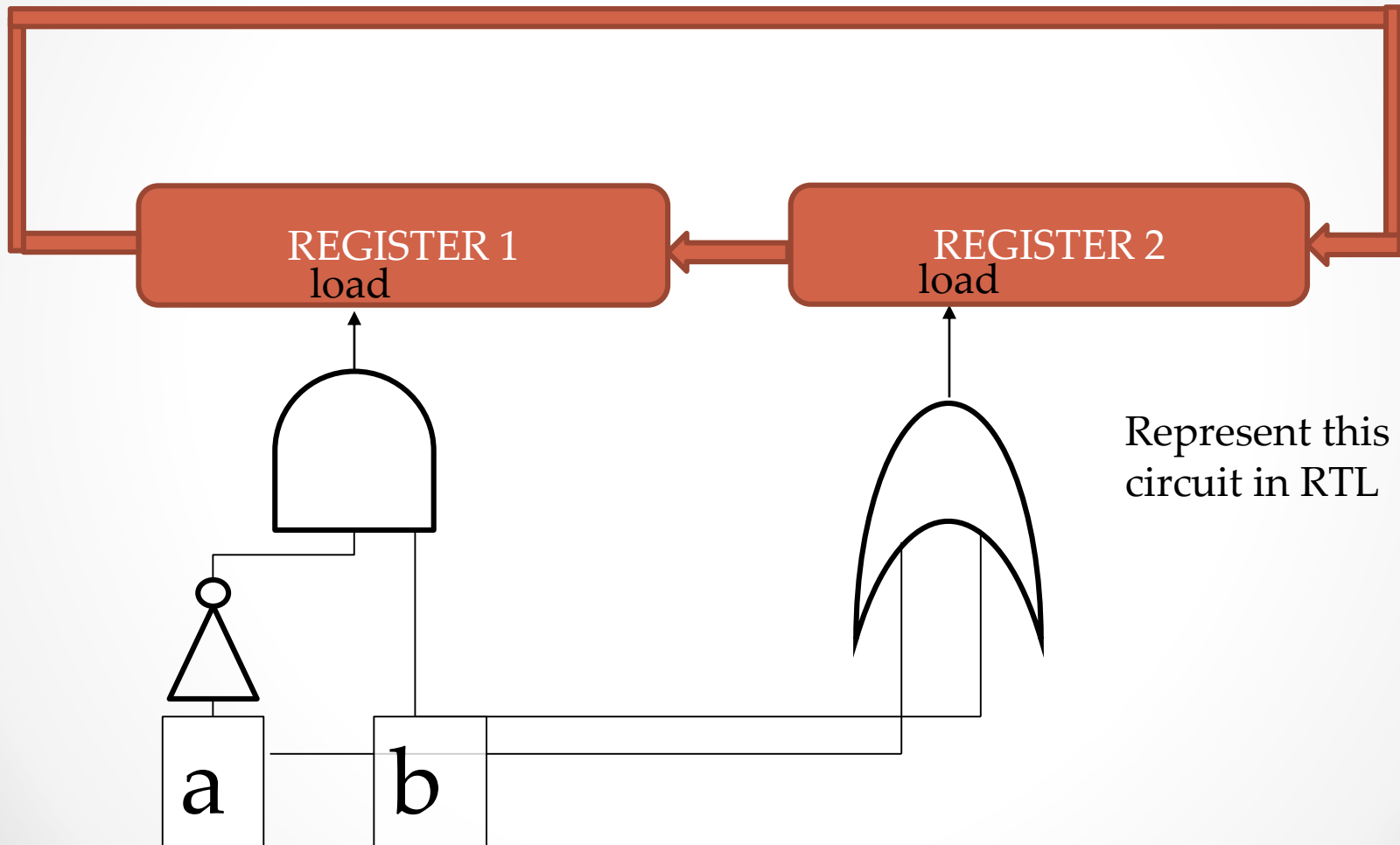


# QUIZ1



# QUIZ2

Represent the following conditional statement in RTL:

if (  $P == 1$  ) then  $R1 \leftarrow R2$  else if (  $Q == 1$  ) then  $R1 \leftarrow R3$

# QUIZ3

Use

- A 4-bit counter with parallel load
- A 4-bit adder

To draw a block that implements the following statements in RTL:

$x : R1 \leftarrow R1 + R2$   
 $x'y : R1 \leftarrow R1 + 1$

Where:


- R1 is the 4-bit counter with parallel load
- R2 is a 4-bit register

# QUIZ4

For the following bus:


How many multiplexers are needed?

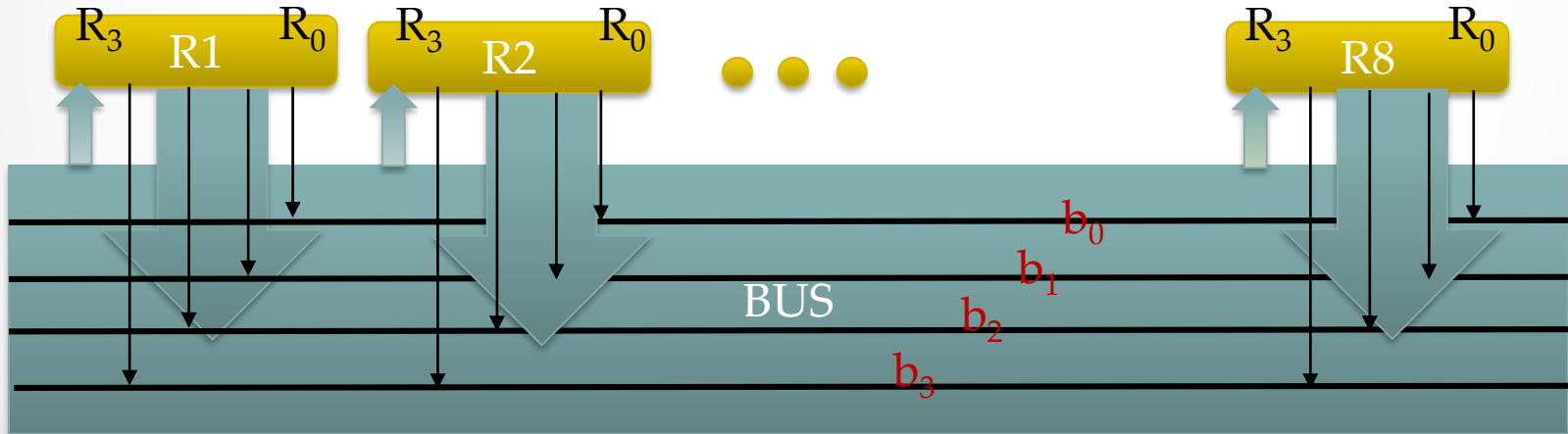What will be the size of each multiplexer?




# QUIZ5

M	A	B	S	C <sub>4</sub>
0	0111	0110		
1	1100	1000		
1	0101	1010		

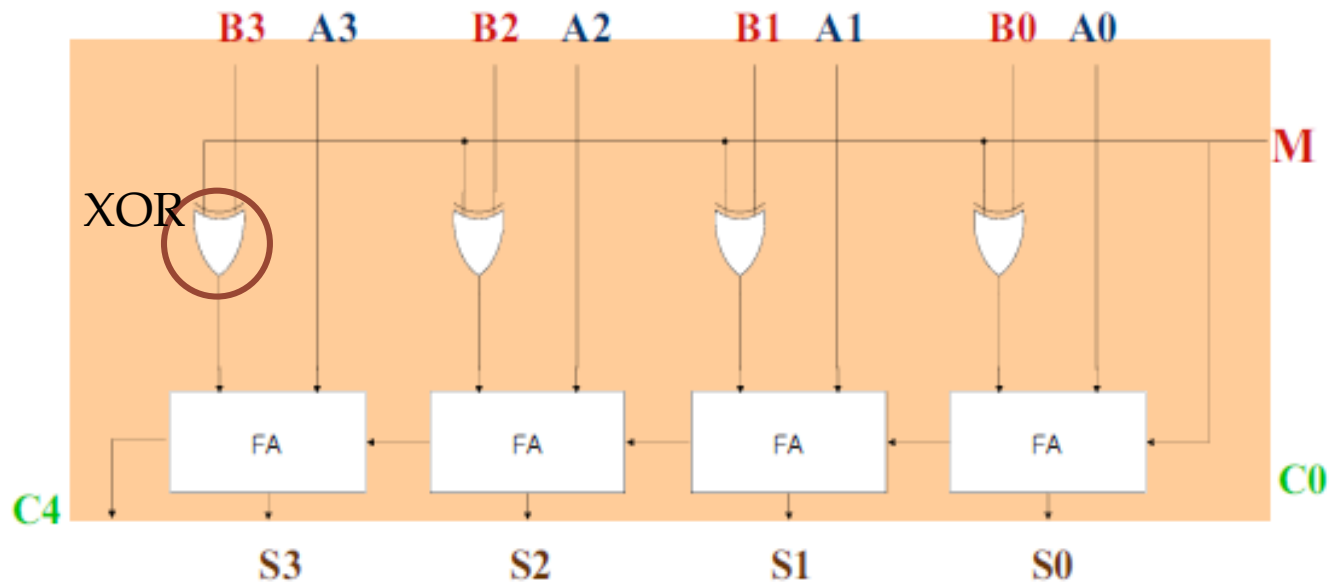

# QUIZ6

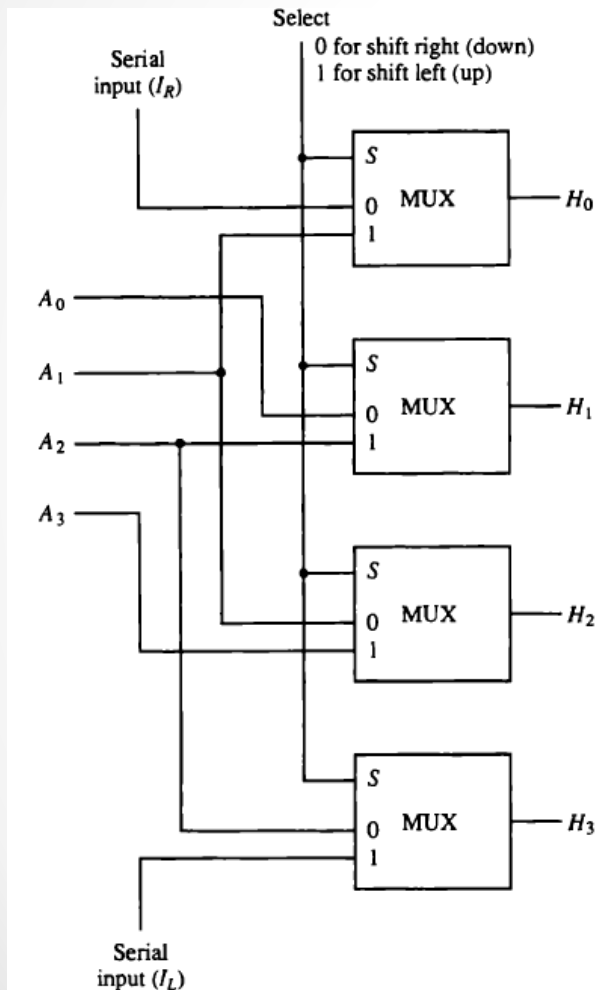

Function table				
Select	Output			
$S$	$H_0$	$H_1$	$H_2$	$H_3$
0	$I_R$	$A_0$	$A_1$	$A_2$
1	$A_1$	$A_2$	$A_3$	$I_L$

Suppose:  
 $A = 1001$ ,  $S = 1$ ,  $I_R = 1$ ,  $I_L = 0$   
 What will be the output  
 value of  
 $H = (H_3H_2H_1H_0)$