

Combinational Circuits

Carmi Merimovich

The Academic College of Tel-Aviv

January 29, 2025

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment
mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

Boolean functions (Platonic world)



Combinational circuits (Real hardware)

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3








Half adder

2-Bits Adder

Full adder

Binary adder

Realizing the Boolean Operators

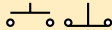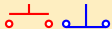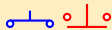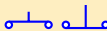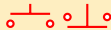  - A switch is a component having three tips 
 - ▶ One control pin
 - ▶ Two data pins
- A switch can be in one of two states
 - ▶ Unpressed : The control is at logic 0
 - ▶ Pressed : The control is at logic 1
- The data pins can be in one of two states
 - ▶ Connected 
 - ▶ Disconnected 
- Naming and drawing convention:
 - ▶ N-switch : Connected \iff Pressed
 - ▶ P-switch : Connected \iff Unpressed

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3









Half adder

2-Bits Adder

Full adder

    Binary adder

Switch Drawings

Type	N	P
Unpressed switch		
Pressed switch		
Bipolar transistor		
FET transistor		

Used in drawings

Switches \equiv Transistors

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

The following implementation of logic gates is an abstraction of the CMOS technology. The CMOS technology was invented at [Fairchild Semiconductor](#) by [Frank Wanlass](#) and [Chih-Tang Sah](#).

CMOS

Complementary Metal-Oxide-Semiconductor

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

Logic Gates

Realizing the Operators \cdot , $+$ and $-$

Later on we will see that there are more gates

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder


2-Bits Adder

Full adder



Binary adder

Not Gate

'Electronic' circuit

 

Gate symbol

  

$$z = \bar{x}$$

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder


2-Bits Adder

Full adder



Binary adder

Not Gate $x = 0$

'Electronic' circuit

 

Gate symbol

  

$$z = \bar{x}$$

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3

Half adder


2-Bits Adder

Full adder



Binary adder

Not Gate $x = 1$

'Electronic' circuit

 

Gate symbol

  

$$z = \bar{x}$$

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder


2-Bits Adder

Full adder



Binary adder

Not Gate

'Electronic' circuit

 

Gate symbol

  

$$z = \bar{x}$$

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3



Half adder

2-Bits Adder

Full adder

Binary adder

And Gate

 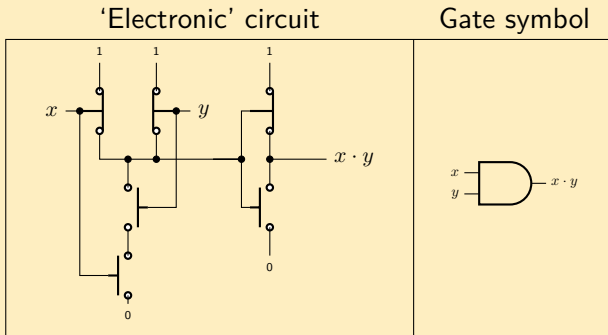

$$z = x \cdot y$$

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3


Half adder

2-Bits Adder

Full adder

Binary adder

And Gate $x = 0, y = 0$

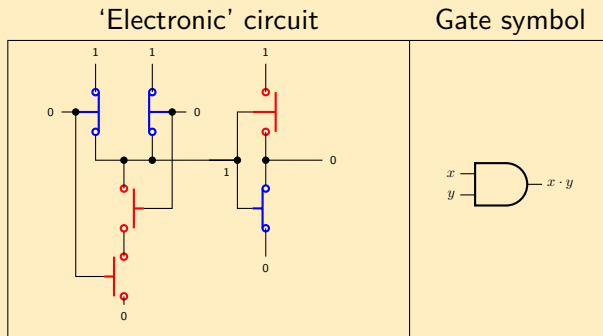

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment


mod 3

Half adder

2-Bits Adder

Full adder


Binary adder

 



$$z = x \cdot y$$

And Gate $x = 0, y = 1$

'Electronic' circuit

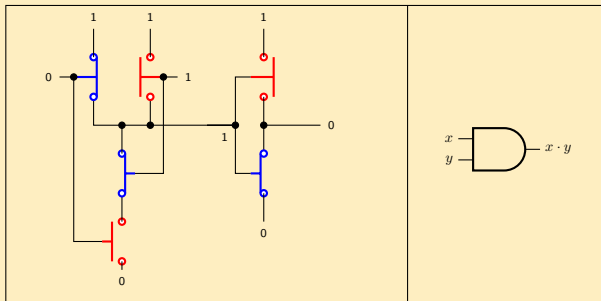

Gate symbol

  

$$z = x \cdot y$$

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder


2-Bits Adder

Full adder

Binary adder

And Gate $x = 1, y = 0$

'Electronic' circuit

 

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment


mod 3

Half adder

2-Bits Adder

Full adder



Binary adder

 

$$z = x \cdot y$$

And Gate $x = 1, y = 1$

'Electronic' circuit

  

$$z = x \cdot y$$

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

And Gate

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment



mod 3

Half adder

2-Bits Adder

Full adder


Binary adder

 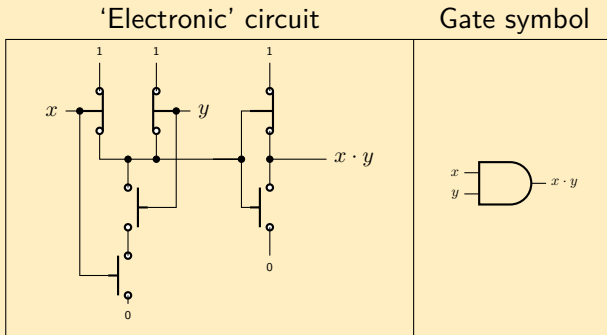


$$z = x \cdot y$$

Or Gate

'Electronic' circuit

 

Gate Symbol

 

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment


mod 3

Half adder

2-Bits Adder

Full adder


Binary adder

 


$$z = x + y_{0/53}$$

Or Gate $x = 0, y = 0$

'Electronic' circuit

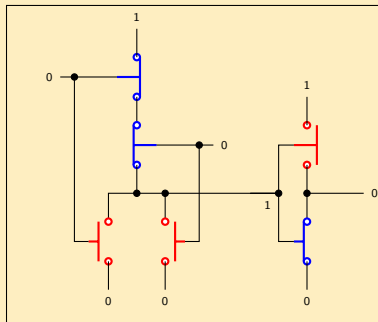

Gate Symbol

 

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment


mod 3

Half adder

2-Bits Adder

Full adder


Binary adder

 


$$z = x + y_{10/53}$$

Or Gate $x = 0, y = 1$

'Electronic' circuit

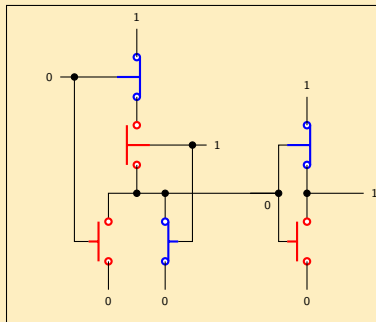

Gate Symbol

 

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment


mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

 

$$z = x + y_{10/53}$$

Or Gate $x = 1, y = 0$

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3


Half adder

2-Bits Adder



Full adder

Binary adder

'Electronic' circuit

 

Gate Symbol

  

$$z = x + y_{10/53}$$

Or Gate $x = 1, y = 1$

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3


Half adder

2-Bits Adder



Full adder

Binary adder

'Electronic' circuit

 


Gate Symbol

  


$$z = x + y_{10/53}$$

Or Gate

'Electronic' circuit

 

Gate Symbol

 

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment


mod 3

Half adder

2-Bits Adder

Full adder


Binary adder

 


$$z = x + y_{0/53}$$

Xor gate (good place as any)

'Electronic' circuit

 

Gate symbol

 

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder


2-Bits Adder

Full adder


Binary adder

Xor gate

'Electronic' circuit

 

Gate symbol

 

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder


2-Bits Adder

Full adder


Binary adder

Xor gate $x = 0, y = 0$

'Electronic' circuit

 

Gate symbol

 

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder


2-Bits Adder

Full adder


Binary adder

Xor gate $x = 0, y = 1$

'Electronic' circuit

 

Gate symbol

 

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder


2-Bits Adder

Full adder


Binary adder

Xor gate $x = 1, y = 0$

'Electronic' circuit

 

Gate symbol

 

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3

Half adder


2-Bits Adder

Full adder


Binary adder

Xor gate $x = 1, y = 1$

'Electronic' circuit

 

Gate symbol

 

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder


2-Bits Adder

Full adder


Binary adder

Xor gate (good place as any)

'Electronic' circuit

 

Gate symbol

 

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder


2-Bits Adder

Full adder


Binary adder

Commutativity and Associativity

 - \cdot , $+$ and \oplus are commutative: Gate inputs are symmetric
- \cdot , $+$ and \oplus are associative: Gatewise we get, e.g.,



 - Or we can use gate with three inputs, e.g.,



- There is a performance **hit** for each additional input pin
- Usually, two successive gate are slower

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

 
 

Half adder

2-Bits Adder

Full adder

Binary adder

Multi Inputs Gates

And gate	
Or gate	
Xor gate	

- Most technologies allow at most 5 input pins

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3

Half adder


2-Bits Adder

Full adder


Binary adder

3-Inputs Gates waveforms

$$t = x \cdot y \cdot z$$

 

$$t = x + y + z$$

 

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder


Full adder

Binary adder

'Electronics' observation regarding gates


The realization of both \neg and \neg have \triangleright at their end

And 'Electronics'

 

$$z = \overline{x \cdot y}$$
$$= x \uparrow y$$

Or 'Electronics'

 

$$z = \overline{x + y}$$
$$= x \downarrow y$$

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

Nand (\uparrow) and Nor (\downarrow) Properties

Nand

Nor

$\bar{x} = \overline{x \cdot x} = x \uparrow x$	$\bar{x} = \overline{x + x} = x \downarrow x$
$x \cdot y = \overline{\overline{x \cdot y}} =$ $= \overline{x \uparrow y} =$ $= (x \uparrow y) \uparrow (x \uparrow y)$	$x \cdot y = \overline{\overline{x \cdot y}} =$ $= \overline{\bar{x} + \bar{y}} =$ $= (x \downarrow x) \downarrow (y \downarrow y)$
$x + y = \overline{\overline{x + y}} =$ $= \overline{\bar{x} \cdot \bar{y}} =$ $= (x \uparrow x) \uparrow (y \uparrow y)$	$x + y = \overline{\overline{x + y}} =$ $= \overline{x \downarrow y} =$ $= (x \downarrow y) \downarrow (x \downarrow y)$

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

Definition

A set of functions and constants is a complete system if every boolean function can be defined with them

Corollary

Both $\{\uparrow\}$ and $\{\downarrow\}$ are complete systems.

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

Nand Gate

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3


Half adder

2-Bits Adder


Full adder

Binary adder

'Electronic' circuit

 

Logic symbol

 

Nor Gate

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3


Half adder

2-Bits Adder


Full adder

Binary adder

   
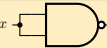

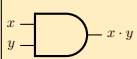
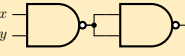
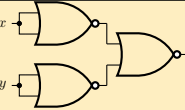
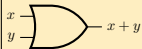
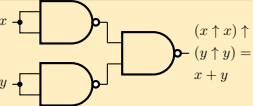
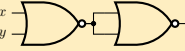
‘Electronic’ circuit



Logic symbol



Realizing the operators with Nand and Nor

Gate	Nand	Nor
 $x \rightarrow \bar{x}$	 $x \uparrow x = \bar{x}$	 $x \downarrow x = \bar{x}$
 $x \cdot y$	 $(x \uparrow y) \uparrow = x \cdot y$	 $(x \downarrow x) \downarrow (y \downarrow y) = x \cdot y$
 $x + y$	 $(x \uparrow x) \uparrow (y \uparrow y) = x + y$	 $(x \downarrow y) \downarrow (x \downarrow y) = x + y$

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder


Full adder

Binary adder


Realization of XOR should be here

Two final gates

 - The buffer gate (important in real circuits):



- The nxor gate:

 

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3




Half adder

2-Bits Adder

Full adder

Binary adder

 Associative complement

Nand gate	
Nor gate	
Nxor gate	

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

(Carmi) Lecture 6 reached here

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

Combinational Circuits

(Realization of boolean functions)

Recall that the boolean operators are boolean functions

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

Functions to be Realized

- Seven Segment
- mod 3
- Half adder
- 2-bit binary adder
- Full adder
- Binary adder

The boolean functions are from the previous chapter

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder


Binary adder

Realizing the Seven-Segment

The formule are from the previous lecture

1. Block diagram
2. Logic circuit

Seven-Segment (block diagram)

 

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

Seven-Segment (formulae)

SOP

$$a = m_0 + m_2 + m_3 + m_5 + m_7 + m_8 + m_9$$

$$b = m_0 + m_1 + m_2 + m_3 + m_4 + m_7 + m_8 + m_9$$

$$c = m_0 + m_1 + m_3 + m_4 + m_5 + m_6 + m_7 + m_8 + m_9$$

$$d = m_0 + m_2 + m_3 + m_5 + m_6 + m_8$$

$$e = m_0 + m_2 + m_6 + m_8$$

$$f = m_0 + m_4 + m_5 + m_6 + m_8 + m_9$$

$$g = m_2 + m_3 + m_4 + m_5 + m_6 + m_8 + m_9$$

POS

$$a = \bar{m}_1 \bar{m}_4 \bar{m}_6$$

$$b = \bar{m}_5 \bar{m}_6$$

$$c = \bar{m}_2$$

$$d = \bar{m}_1 \bar{m}_4 \bar{m}_7$$

$$e = \bar{m}_1 \bar{m}_3 \bar{m}_4 \bar{m}_5 \bar{m}_7 \bar{m}_9$$

$$f = \bar{m}_1 \bar{m}_2 \bar{m}_3 \bar{m}_7$$

$$g = \bar{m}_0 \bar{m}_1 \bar{m}_7$$

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3


Half adder

2-Bits Adder

Full adder

Binary adder

Seven Segment (SOP)

 

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

Seven Segment (SOP)

Combinational
Circuits

© C.M.

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

Seven Segment (SOP)

Combinational
Circuits

© C.M.

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment


mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

 

Seven Segment (SOP)

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment


mod 3

Half adder


2-Bits Adder

Full adder

Binary adder

 

Seven Segment (SOP)

 

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

Seven Segment (SOP)

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment


mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

 

Seven Segment (SOP)

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment


mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

 

Seven Segment (SOP)

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment


mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

 

Seven Segment (SOP)

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment



mod 3

Half adder


2-Bits Adder

Full adder

Binary adder

  

Seven Segment (SOP)

 

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

Seven Segment (POS)

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment


mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

 

Seven Segment (POS)

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

Seven Segment (POS)

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment


mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

 

Seven Segment (POS)

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment


mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

 

Seven Segment (POS)

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment


mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

 

Seven Segment (POS)

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment


mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

 

Seven Segment (POS)

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment


mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

 

Seven Segment (POS)

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment


mod 3

Half adder



2-Bits Adder

Full adder

Binary adder

 

Seven Segment (POS)

  

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

Seven Segment (POS)

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment


mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

 

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder


Binary adder

Realizing mod 3

The formule are from the previous lecture

1. Block diagram
2. Logic circuit

mod 3 Block Diagram

 

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

$$f_1 = \bar{n}_3\bar{n}_2n_1\bar{n}_0 + \bar{n}_3n_2\bar{n}_1n_0 + n_3\bar{n}_2\bar{n}_1\bar{n}_0 + n_3\bar{n}_2n_1n_0 + \\ n_3n_2n_1\bar{n}_0$$

$$f_0 = \bar{n}_3\bar{n}_2\bar{n}_1n_0 + \bar{n}_3n_2\bar{n}_1\bar{n}_0 + \bar{n}_3n_2n_1n_0 + n_3\bar{n}_2n_1\bar{n}_0 + \\ n_3n_2\bar{n}_1n_0$$

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3


Half adder

2-Bits Adder

Full adder

Binary adder

mod 3 f_1 -Circuit

 

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3


Half adder

2-Bits Adder

Full adder

Binary adder

mod 3 f_0 -Circuit

 

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

Realizing the Half Adder

The formule are from the Boolean Algebra lecture

1. Block diagram
2. Logic circuit


Half Adder (block diagram)

Half Adder (previous lecture)

$$f_1 = x \cdot y$$

$$f_0 = x \oplus y$$

Two bits in, two bits out

 

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

Half Adder (circuit)

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment


mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

 

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

Realizing 2-Bits Adder

(The formulae are from the Boolean Algebra chapter)

2-Bits Binary Adder (Function)

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder


Binary adder

$$f_2 = \bar{x}_1 x_0 y_1 y_0 + x_1 \bar{x}_0 y_1 \bar{y}_0 + x_1 \bar{x}_0 y_1 y_0 + x_1 x_0 \bar{y}_1 y_0 + x_1 x_0 y_1 \bar{y}_0 + x_1 x_0 y_1 y_0$$

$$f_1 = \bar{x}_1 \bar{x}_0 y_1 \bar{y}_0 + \bar{x}_1 \bar{x}_0 y_1 y_0 + \bar{x}_1 x_0 \bar{y}_1 y_0 + \bar{x}_1 x_0 y_1 \bar{y}_0 + x_1 \bar{x}_0 \bar{y}_1 \bar{y}_0 + x_1 \bar{x}_0 \bar{y}_1 y_0 + x_1 x_0 \bar{y}_1 \bar{y}_0 + x_1 x_0 y_1 y_0$$

$$f_0 = \bar{x}_1 \bar{x}_0 y_1 \bar{y}_0 + \bar{x}_1 \bar{x}_0 y_1 y_0 + \bar{x}_1 x_0 \bar{y}_1 \bar{y}_0 + \bar{x}_1 x_0 y_1 \bar{y}_0 + x_1 \bar{x}_0 \bar{y}_1 y_0 + x_1 \bar{x}_0 y_1 y_0 + x_1 x_0 \bar{y}_1 \bar{y}_0 + x_1 x_0 y_1 \bar{y}_0$$

2-Bits Adder f_2 -Circuit

 

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3


Half adder

2-Bits Adder

Full adder

Binary adder

2-Bits Adder f_1 -Circuit

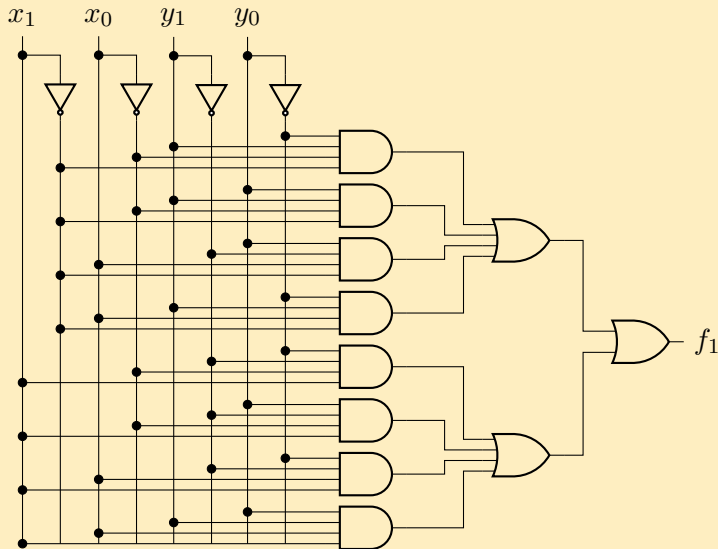

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3


Half adder

2-Bits Adder

Full adder

Binary adder

2-Bits Adder f_0 -Circuit

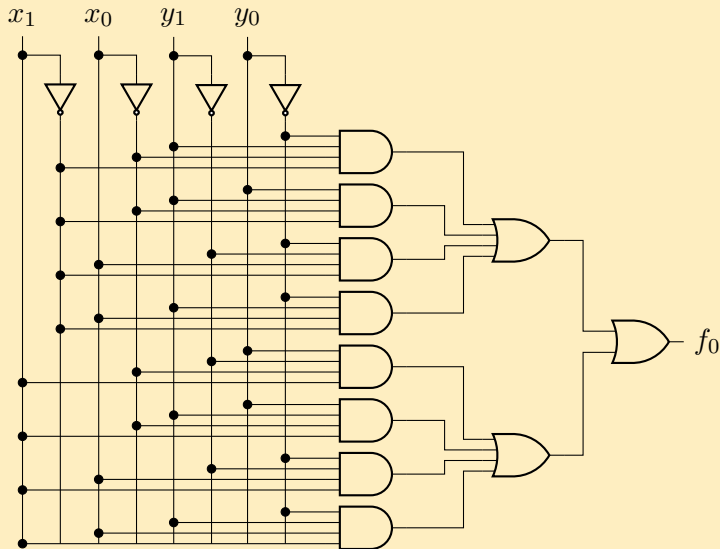

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder


Binary adder

Realizing the Full Adder

Formuale are from the boolean algebras lecture

1. Block diagram
2. Logic circuit

Full Adder (block diagram)

 

$$f_0(x, y, z) = x \oplus y \oplus z$$

$$\begin{aligned} f_1(x, y, z) &= \bar{x}yz + x\bar{y}z + xy\bar{z} + xyz = \\ &= (x + y + z)(x + y + \bar{z})(x + \bar{y} + z)(\bar{x} + y + z) = \\ &= yz + xz + xy \end{aligned}$$

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3


Half adder

2-Bits Adder

Full adder

Binary adder

Full adder (f_1 SOP)

 

$$f_0(x, y, z) = x \oplus y \oplus z$$

$$f_1(x, y, z) = \bar{x}yz + x\bar{y}z + xy\bar{z} + xyz$$

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3


Half adder

2-Bits Adder

Full adder

Binary adder

Full adder (f_1 POS circuits)

 

$$f_0(x, y, z) = x \oplus y \oplus z$$

$$f_1(x, y, z) = (x + y + z)(x + y + \bar{z})(x + \bar{y} + z)(\bar{x} + y + z)$$

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3


Half adder

2-Bits Adder

Full adder

Binary adder

Full adder (simplified circuit)

 

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

$$f_0(x, y, z) = x \oplus y \oplus z$$

$$f_1(x, y, z) = yz + xz + xy$$

Full adder (nands)

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3


Half adder

2-Bits Adder


Full adder

Binary adder

SOP

 

NANDS

 

Full adder (nors)

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment


mod 3

Half adder

2-Bits Adder

Full adder

Binary adder

 

$$f_0(x, y, z) = x \oplus y \oplus z$$

$$f_1(x, y, z) = (x + y + z)(x + y + \bar{z})(x + \bar{y} + z)(\bar{x} + y + z)$$

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder


Binary adder

Realizing the Binary Adder

The formule are from the previous lecture

1. Block diagram
2. Logic circuit

Binary adder (block diagram)

 

Theme

Transistors

Gates

n -ary Gates

Circuits

Seven segment

mod 3


Half adder

2-Bits Adder

Full adder

Binary adder

Binary Adder (circuit)

 

Theme

Transistors

Gates

n-ary Gates

Circuits

Seven segment

mod 3

Half adder

2-Bits Adder

Full adder

Binary adder