

(The Course) Verilog Environment

Carmi Merimovich

The Academic College of Tel-Aviv

January 29, 2025

- Circuits drawings are not useful as input to programs
- We have hardware description languages (HDLs)
 - ▶ Two languages are mainstream
 - ▶ The one we will **not** use is VHDL
 - ▶ It is ADA like, I hate it
- Verilog is the language we will use
- Verilog is **not** a programming language
- The Web is choke full of material on Verilog
- Books titled 'digital design' and 'Verilog' will also do
- This chapter aims to show how to use the software
- Definitely **not** to teach Verilog

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

- iverilog - Verilog compiler
- vvp - Circuit emulator
- GTKWave - Waveform viewer
- gmake/make - (recommended) make

Installing

- All of the programs above are GPL'ed
- There is an easy Windows [installer](#)
- The programs are in the bin folders
- You can add them to your path (I did not)
- gmake can be found in, e.g., strawberry Perl
 - ▶ folder: C:\Strawberry\c\bin

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Levels used in this course

- Gate level - Will be used to synthesize circuits
- Data flow - Will be used for testbenches
- Behavioral - If there is no other way

The reasons for the above are pedagogical

Namely, in a first course, students should use only gates

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Gate	Verilog Primitive
 $y = \bar{x}$	<code>not(y,x)</code>
 $y = x$	<code>buf(y,x)</code>
 $y = \begin{cases} x & c = 1 \\ Z & c = 0 \end{cases}$	<code>bufif1(y,x,c)</code>
 $y = x_0 \cdot \dots \cdot x_n$	<code>and(y,x0,...,xn)</code>
 $y = x_0 + \dots + x_n$	<code>or(y,x0,...,xn)</code>
 $y = x_0 \oplus \dots \oplus x_n$	<code>xor(y,x0,...,xn)</code>
 $y = \overline{x_0 + \dots + x_n}$	<code>nor(y,x0,...,xn)</code>
 $y = \overline{x_0 \cdot \dots \cdot x_n}$	<code>nand(y,x0,...,xn)</code>
 $y = \overline{x_0 \oplus \dots \oplus x_n}$	<code>xnor(y,x0,...,xn)</code>

Do not use the primitives directly

There is no delay when using them

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Demo: a 3-input Gate with Delay

Introducing the Following Features

Verilog

© C.M.

- Gate primitive invocation
- Module definition

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Gate Level Example

Listing 1: demo/1/and3.v

```
'timescale 1ns/1ns

module and3(
    output xyz,
    input  x,
    input  y,
    input  z);

    and #(7ns) (xyz,x,y,z);

endmodule
```

[Primitives](#)[Demo: and3](#)[Library](#)[Seven-Segment](#)[mod 3](#)[Half Adder](#)[2-Bits Adder](#)[Full Adder](#)[Binary Adder](#)

- Without the optional `timescale`, iverilog has issues
- As it stands we have defined a circuit
- No input, no output, no nothing
- We **must** check it
- We will add a **testbench**
- Testbenches are simulations, we use data flow for them

Primitives

Demo: `and3`

Library

Seven-Segment

`mod 3`

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Introducing the following Features

Verilog

© C.M.

- Multiple modules in the same .v files
- Module instancing
- logic definition
- wire definition
- assign statement
- repeat statement
- initial block
- \$dumpfile, \$dumpvars, \$finish

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Listing 2: demo/2/and3.v

```
'timescale 1ns/1ns

module and3(
    output xyz,
    input  x,
    input  y,
    input  z);

    and #(7ns) (xyz,x,y,z);

endmodule

module and3_tb;
```

[Primitives](#)[Demo: and3](#)[Library](#)[Seven-Segment](#)[mod 3](#)[Half Adder](#)[2-Bits Adder](#)[Full Adder](#)[Binary Adder](#)

Demo: and3 with testbench II

Verilog

© C.M.

```
logic x,y,z;  // Simulator thing
wire t;
and3 a(t,x,y,z);
```

```
initial begin
    $dumpfile("and3.vcd");
    $dumpvars;
```

```
x = 0;
```

```
y = 0;
```

```
z = 0;
```

```
repeat (2) begin
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Demo: and3 with testbench III

Verilog

© C.M.

```
repeat (2) begin
    repeat (2) begin
        #20ns;
        $display(x,y,z,t);
        z = z + 1;
    end
    y = y + 1;
end
x = x + 1;
end
$finish();
end
endmodule
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Compiling and3.v $\Rightarrow$ and3

```
c:\iverilog\bin\iverilog -g2012 -oand3 and3.v
```

- -gyear - Verilog standard year
- -o output - Default is a.out
- file(s) - list of Verilog files to compile

Root module

- Modules not instanced will be root instanced
- -sroot can be used to specify the root module

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Simulate and3 $\Rightarrow$ and3.vcd (due to \$dumpfile)

```
c:\iverilog\bin\vvp and3
```

View and3.vcd

```
c:\iverilog\gtkwave\bin\gtkwave and3
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

(Carmi) Lecture 7 reached here

Listing 3: demo/2/makefile

```
dir      = c:/iverilog/bin/
dir2     = c:/iverilog/gtkwave/bin/
module   = and3

all: $(module).vcd

$(module): $(module).v
    $(dir)iverilog \
        -g2012 \
        -o $(module) \
        $(module).v

$(module).vcd: $(module)
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

```
$(dir)vvp $(module)
$(dir2)gtkwave $(module).vcd

clean:
    -del    $(module)
    -del    $(module).vcd
```

[Primitives](#)[Demo: and3](#)[Library](#)[Seven-Segment](#)[mod 3](#)[Half Adder](#)[2-Bits Adder](#)[Full Adder](#)[Binary Adder](#)

Listing 4: demo/3/and3.v

```
'timescale 1ns/1ns

module and3(
    output xyz,
    input  x,
    input  y,
    input  z);

    and #(7ns) (xyz,x,y,z);

endmodule
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Listing 5: demo/3/and3_tb.v

```
'timescale 1ns/1ns

module and3_tb;

    logic x,y,z;
    wire t;
    and3 a(t,x,y,z);

    initial begin
        $dumpfile("and3.vcd");
        $dumpvars;
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Splitting to Several Files: and3_tb II

Verilog

© C.M.

```
x = 0;
y = 0;
z = 0;

repeat (2) begin
    repeat (2) begin
        repeat (2) begin
            #20ns;
            $display(x,y,z,t);
            z = z + 1;
        end
        y = y + 1;
    end
    x = x + 1;
end
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Splitting to Several Files: and3_tb III

Verilog

© C.M.

```
    $finish();  
end  
endmodule
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Two options

- List of files:

```
c:\iverilog\bin\iverilog -g2012 -oand3 and3.v and3_tb.v
```

- Command file

```
c:\iverilog\bin\iverilog -g2012 -oand3 -cand3.cf
```

and in the file and3.cf

```
and3.v
```

```
and3_tb.v
```

Primitives

Demo: and3

Library

Seven-Segment
mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

verilog.zip and demo.zip

(extraction of .zip files from the site)

Folder Structure

Verilog

© C.M.

```
demo
├── makefile
├── 1
├── 2
├── 3
├── halfAdder
│   ├── makefile
│   └── :
├── fullAdder
│   └── :
├── binaryAdder
│   └── :
├── lib
│   └── :
└── libSrc
    ├── makefile
    ├── andGate
    │   └── :
    ├── and2Gate
    └── :
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

- A folder can be designated a library with the `-y` option
- A file in the library should contain only **one** module
- The file name and the module name must be **identical**
- A library is searched when an instanced module is not found

We supply a library

- It contains gates with delays
- It is in the folder `lib`
- The source code, so to speak, is in the `verilog` folder

Primitives

Demo: `and3`

Library

Seven-Segment

`mod 3`

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Do not be misled

- The library delays are in order to get the gist of delays
- The delays are technology specific
- Usually the transitions times of $0 \rightarrow 1$ and $1 \rightarrow 0$ are different
- (Verilog has the machinery for different delays)

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

2-pins	3-pins	4-pins	5-pins
andGate	and3Gate	and4Gate	and5Gate
orGate	or3Gate	or4Gate	or5Gate
xorGate	xor3Gate	xor4Gate	xor5Gate
nandGate	nand3Gate	nand4Gate	nand5Gate
norGate	nor3Gate	nor4Gate	nor5Gate

- 1-pin: notGate, bufGate, bufifGate
- n -pins: andMulti, orMulti, xorMulti, nandMulti, norMulti

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Completing the Motivation

The previous chapter circuits in Verilog

The code is in the demo folder

Seven-Segment (formulae)

Verilog

© C.M.

$$m_0 = \bar{b}_3 \bar{b}_2 \bar{b}_1 \bar{b}_0$$

$$m_1 = \bar{b}_3 \bar{b}_2 \bar{b}_1 b_0$$

$$m_2 = \bar{b}_3 \bar{b}_2 b_1 \bar{b}_0$$

$$m_3 = \bar{b}_3 \bar{b}_2 b_1 b_0$$

$$m_4 = \bar{b}_3 b_2 \bar{b}_1 \bar{b}_0$$

$$m_5 = \bar{b}_3 b_2 \bar{b}_1 b_0$$

$$m_6 = \bar{b}_3 b_2 b_1 \bar{b}_0$$

$$m_7 = \bar{b}_3 b_2 b_1 b_0$$

$$m_8 = b_3 \bar{b}_2 \bar{b}_1 \bar{b}_0$$

$$m_9 = b_3 \bar{b}_2 \bar{b}_1 b_0$$

$$a = \bar{m}_1 \bar{m}_4 \bar{m}_6$$

$$b = \bar{m}_5 \bar{m}_6$$

$$c = \bar{m}_2$$

$$d = \bar{m}_1 \bar{m}_4 \bar{m}_7$$

$$e = \bar{m}_1 \bar{m}_3 \bar{m}_4 \bar{m}_5 \bar{m}_7 \bar{m}_9$$

$$f = \bar{m}_1 \bar{m}_2 \bar{m}_3 \bar{m}_7$$

$$g = \bar{m}_0 \bar{m}_1 \bar{m}_7$$

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Listing 6: segments7.v

```
'timescale 1ns/1ns

module segments7(
    output a,
    output b,
    output c,
    output d,
    output e,
    output f,
    output g,
    input  n3,
    input  n2,
    input  n1,
```

[Primitives](#)[Demo: and3](#)[Library](#)[Seven-Segment](#)[mod 3](#)[Half Adder](#)[2-Bits Adder](#)[Full Adder](#)[Binary Adder](#)

Seven Segment (module) II

Verilog

© C.M.

```
    input  n0
);

wire n0n, n1n, n2n, n3n;
notGate ng0(n0n, n0);
notGate ng1(n1n, n1);
notGate ng2(n2n, n2);
notGate ng3(n3n, n3);

wire m0n,m1n,m2n,m3n,m4n,m5n,m6n,m7n;
nand4Gate nnd0(m0n,n3n,n2n,n1n,n0n);
nand4Gate nnd1(m1n,n3n,n2n,n1n,n0 );
nand4Gate nnd2(m2n,n3n,n2n,n1 ,n0n);
nand4Gate nnd3(m3n,n3n,n2n,n1 ,n0 );
nand4Gate nnd4(m4n,n3n,n2 ,n1n,n0n);
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Seven Segment (module) III

Verilog

© C.M.

```
nand4Gate nnd5(m5n,n3n,n2 ,n1n,n0 );
nand4Gate nnd6(m6n,n3n,n2 ,n1 ,n0n);
nand4Gate nnd7(m7n,n3n,n2 ,n1 ,n0 );
nand4Gate nnd8(m8n,n3 ,n2n,n1n,n0n);
nand4Gate nnd9(m9n,n3 ,n2n,n1n,n0 );

wire eTmp;
and3Gate anda(a,m1n,m4n,m6n);
andGate andb(b,m5n,m6n);
assign c = m2n;
and3Gate andd(d,m1n,m4n,m7n);
and4Gate ande1(eTmp,m1n,m3n,m4n,m5n);
and3Gate ande(e,eTmp,m7n,m9n);
and4Gate andf(f,m1n,m2n,m3n,m7n);
and3Gate andg(g,m0n,m1n,m7n);
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Seven Segment (module) IV

Verilog

© C.M.

```
endmodule
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Listing 7: segments7_tb.v

```
'timescale 1ns/1ns

module segments7_tb;
    logic x3,x2,x1,x0;
    wire a,b,c,d,e,f,g;

    segments7 m(a,b,c,d,e,f,g,x3,x2,x1,x0);

    initial begin
        $dumpfile("segments7.vcd");
        $dumpvars;

        x3 = 0;
```

[Primitives](#)[Demo: and3](#)[Library](#)[Seven-Segment](#)[mod 3](#)[Half Adder](#)[2-Bits Adder](#)[Full Adder](#)[Binary Adder](#)

Seven Segment (testbench) II

Verilog

© C.M.

```
x2 = 0;
x1 = 0;
x0 = 0;

repeat (2) begin
  repeat (2) begin
    repeat (2) begin
      repeat (2) begin
        #30ns;
        $display(x3,x2,x1,x0);
        carmi(a,b,c,d,e,f,g);
        $display();
        x0 = x0 + 1;
      end
      x1 = x1 + 1;
    end
  end
end
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Seven Segment (testbench) III

Verilog

© C.M.

```
        end
        x2 = x2 + 1;
    end
    x3 = x3 + 1;
end
$finish();
end

task carmi(input a,b,c,d,e,f,g);
if ((a == 1) || (f == 1))
    $write("*");
else
    $write(" ");

if (a == 1)
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Seven Segment (testbench) IV

Verilog

© C.M.

```
    $write("****");  
else  
    $write("    ");  
  
if ((a == 1) || (b == 1))  
    $write("*\n");  
else  
    $write(" \n");  
  
repeat (2) begin  
    if (f == 1)  
        $write("*    ");  
    else  
        $write("    ");
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Seven Segment (testbench) V

Verilog

© C.M.

```
    if (b == 1)
        $write("*\n");
    else
        $write("\n");
end

if ((f == 1) || (g == 1) || (e == 1))
    $write("*");
else
    $write(" ");

if (g == 1)
    $write("****");
else
    $write("      ");
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Seven Segment (testbench) VI

Verilog

© C.M.

```
if ((b == 1) || (g == 1) || (c == 1))
    $write("*\n");
else
    $write(" \n");

repeat (2) begin
    if (e == 1)
        $write("*      ");
    else
        $write("      ");

    if (c == 1)
        $write("*\n");
    else
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Seven Segment (testbench) VII

Verilog

© C.M.

```
        $write("\n");
end

if ((e == 1) || (d == 1))
    $write("*");
else
    $write(" ");

if (d == 1)
    $write("****");
else
    $write("      ");

if ((d == 1) || (c == 1))
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Seven Segment (testbench) VIII

Verilog

© C.M.

```
        $write("*\n");  
    else  
        $write(" \n");  
  
    endtask;  
  
endmodule
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

mod 3

(The circuits are from the logic gates chapter)

$$f_1 = \bar{n}_3\bar{n}_2n_1\bar{n}_0 + \bar{n}_3n_2\bar{n}_1n_0 + n_3\bar{n}_2\bar{n}_1\bar{n}_0 + n_3\bar{n}_2n_1n_0 + \\ n_3n_2n_1\bar{n}_0$$

$$f_0 = \bar{n}_3\bar{n}_2\bar{n}_1n_0 + \bar{n}_3n_2\bar{n}_1\bar{n}_0 + \bar{n}_3n_2n_1n_0 + n_3\bar{n}_2n_1\bar{n}_0 + \\ n_3n_2\bar{n}_1n_0$$

[Primitives](#)[Demo: and3](#)[Library](#)[Seven-Segment](#)[mod 3](#)[Half Adder](#)[2-Bits Adder](#)[Full Adder](#)[Binary Adder](#)

Listing 8: mod3.v

```
'timescale 1ns/1ns

module mod3(
    output f1,
    output f0,
    input  n3,
    input  n2,
    input  n1,
    input  n0
);

    wire n3n, n2n, n1n, n0n;
    notGate not1(n3n, n3);
```

[Primitives](#)[Demo: and3](#)[Library](#)[Seven-Segment](#)[mod 3](#)[Half Adder](#)[2-Bits Adder](#)[Full Adder](#)[Binary Adder](#)

mod 3 (module) II

Verilog

© C.M.

```
notGate not2(n2n, n2);  
notGate not3(n1n, n1);  
notGate not4(n0n, n0);
```

```
wire m1, m2, m4, m5, m7, m8, m10,  
      m11, m13, m14;
```

```
and4Gate and1(m1,      n3n,n2n,n1n,n0 );  
and4Gate and2(m2,      n3n,n2n,n1 ,n0n);  
and4Gate and4(m4,      n3n,n2 ,n1n,n0n);  
and4Gate and5(m5,      n3n,n2 ,n1n,n0 );  
and4Gate and7(m7,      n3n,n2 ,n1 ,n0);  
and4Gate and8(m8,      n3 ,n2n,n1n,n0n);  
and4Gate and10(m10,    n3 ,n2n,n1 ,n0n);  
and4Gate and11(m11,    n3 ,n2n,n1 ,n0 );
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

mod 3 (module) III

Verilog

© C.M.

```
and4Gate and13(m13, n3 ,n2 ,n1n,n0 );
and4Gate and14(m14, n3 ,n2 ,n1 ,n0n);

or5Gate o1(f1, m2, m5, m8, m11, m14);
or5Gate o0(f0, m1, m4, m7, m10, m13);
endmodule
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Listing 9: mod3_tb.v

```
'timescale 1ns/1ns

module mod3_tb;
    logic x3,x2,x1,x0;
    wire f1, f0;

    mod3 m(f1,f0,x3,x2,x1,x0);

    initial begin
        $dumpfile("mod3.vcd");
        $dumpvars;

        x3 = 0;
```

[Primitives](#)[Demo: and3](#)[Library](#)[Seven-Segment](#)[mod 3](#)[Half Adder](#)[2-Bits Adder](#)[Full Adder](#)[Binary Adder](#)

mod 3 (testbench) II

Verilog

© C.M.

```
x2 = 0;
x1 = 0;
x0 = 0;

repeat (2) begin
    repeat (2) begin
        repeat (2) begin
            repeat (2) begin
                #30ns;
                $display(x3,x2,x1,x0," ",f1,f0);
                x0 = x0 + 1;
            end
            x1 = x1 + 1;
        end
        x2 = x2 + 1;
    end
end
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

mod 3 (testbench) III

Verilog

© C.M.

```
        end
        x3 = x3 + 1;
    end
    $finish();
end
endmodule
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

(Carmi) Lecture 8 reached here

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder


Half Adder

The circuit is from the Logic Gates lecture

Half Adder: Circuit

Verilog

© C.M.

 

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Listing 10: halfAdder.v

```
'timescale 1ns/1ns

module halfAdder(
    output f1,
    output f0,
    input  x,
    input  y
);
    andGate a1(f1,x,y);
    xorGate x1(f0,x,y);
endmodule
```

[Primitives](#)[Demo: and3](#)[Library](#)[Seven-Segment](#)[mod 3](#)[Half Adder](#)[2-Bits Adder](#)[Full Adder](#)[Binary Adder](#)

Listing 11: halfAdder_tb.v

```
'timescale 1ns/1ns

module halfAdder_tb;
    logic x,y;
    wire c, s;

    halfAdder h(c, s, x, y);

    initial begin
        $dumpfile("halfAdder.vcd");
        $dumpvars;

        x = 0;
```

[Primitives](#)[Demo: and3](#)[Library](#)[Seven-Segment](#)[mod 3](#)[Half Adder](#)[2-Bits Adder](#)[Full Adder](#)[Binary Adder](#)

Half Adder: Testbench II

Verilog

© C.M.

```
y = 0;
repeat (2) begin
    repeat (2) begin
        #20ns;
        $display(x,y,c,s);
        y = y + 1;
    end
    x = x + 1;
end
$finish();
end

endmodule
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

2-Bits Adder

2-Bits Binary Adder (Function)

Verilog

© C.M.

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

$$f_2 = \bar{x}_1 x_0 y_1 y_0 + x_1 \bar{x}_0 y_1 \bar{y}_0 + x_1 \bar{x}_0 y_1 y_0 + x_1 x_0 \bar{y}_1 y_0 + x_1 x_0 y_1 \bar{y}_0 + x_1 x_0 y_1 y_0$$

$$f_1 = \bar{x}_1 \bar{x}_0 y_1 \bar{y}_0 + \bar{x}_1 \bar{x}_0 y_1 y_0 + \bar{x}_1 x_0 \bar{y}_1 y_0 + \bar{x}_1 x_0 y_1 \bar{y}_0 + x_1 \bar{x}_0 \bar{y}_1 \bar{y}_0 + x_1 \bar{x}_0 \bar{y}_1 y_0 + x_1 x_0 \bar{y}_1 \bar{y}_0 + x_1 x_0 y_1 y_0$$

$$f_0 = \bar{x}_1 \bar{x}_0 y_1 \bar{y}_0 + \bar{x}_1 \bar{x}_0 y_1 y_0 + \bar{x}_1 x_0 \bar{y}_1 \bar{y}_0 + \bar{x}_1 x_0 y_1 \bar{y}_0 + x_1 \bar{x}_0 \bar{y}_1 y_0 + x_1 \bar{x}_0 y_1 y_0 + x_1 x_0 \bar{y}_1 \bar{y}_0 + x_1 x_0 y_1 \bar{y}_0$$

Listing 12: add2bits.v

```
'timescale 1ns/1ns

module add2bits(
    output f2,
    output f1,
    output f0,
    input  n3,
    input  n2,
    input  n1,
    input  n0
);

    wire n3n, n2n, n1n, n0n;
```

[Primitives](#)[Demo: and3](#)[Library](#)[Seven-Segment](#)[mod 3](#)[Half Adder](#)[2-Bits Adder](#)[Full Adder](#)[Binary Adder](#)

2-Bits Adder (module) II

Verilog

© C.M.

```
notGate not1(n3n, n3);
notGate not2(n2n, n2);
notGate not3(n1n, n1);
notGate not4(n0n, n0);
```

```
wire m1, m2, m3, m4, m5, m6, m7, m8, m9, m10,
      m11, m13, m14, m15;
```

```
and4Gate and1(m1, n3n, n2n, n1n, n0 );
and4Gate and2(m2, n3n, n2n, n1 , n0n);
and4Gate and3(m3, n3n, n2n, n1 , n0 );
and4Gate and4(m4, n3n, n2 , n1n, n0n);
and4Gate and5(m5, n3n, n2 , n1n, n0 );
and4Gate and6(m6, n3n, n2 , n1 , n0n);
and4Gate and7(m7, n3n, n2 , n1 , n0);
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder
2-Bits Adder

Full Adder

Binary Adder

2-Bits Adder (module) III

Verilog

© C.M.

```
and4Gate and8(m8,    n3 ,n2n,n1n,n0n);
and4Gate and9(m9,    n3 ,n2n,n1n,n0 );
and4Gate and10(m10,  n3 ,n2n,n1 ,n0n);
and4Gate and11(m11,  n3 ,n2n,n1 ,n0 );
and4Gate and12(m12,  n3 ,n2 ,n1n,n0n);
and4Gate and13(m13,  n3 ,n2 ,n1n,n0 );
and4Gate and14(m14,  n3 ,n2 ,n1 ,n0n);
and4Gate and15(m15,  n3 ,n2 ,n1 ,n0);
```

```
wire f2_0, f2_1;
or3Gate o_f20(f2_0,  m7, m10, m11);
or3Gate o_f21(f2_1, m13, m14, m15);
orGate  o_f2(f2, f2_0, f2_1);
```

```
wire f1_0, f1_1;
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

2-Bits Adder (module) IV

Verilog

© C.M.

```
or4Gate o_f10(f1_0, m2, m3, m5, m6);
or4Gate o_f11(f1_1, m8, m9, m12, m15);
orGate o_f1(f1, f1_0, f1_1);

wire f0_0, f0_1;
or4Gate o_f00(f0_0, m1, m3, m4, m6);
or4Gate o_f01(f0_1, m9, m11, m12, m14);
orGate o_f0(f0, f0_0, f0_1);
endmodule
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Listing 13: add2bits_tb.v

```
'timescale 1ns/1ns

module add2bits_tb;
    logic x0,x1,y0,y1;
    wire f2, f1, f0;

    add2bits add2(f2,f1,f0,x1,x0,y1,y0);

    initial begin
        $dumpfile("add2bits.vcd");
        $dumpvars;

        x1 = 0;
```

[Primitives](#)[Demo: and3](#)[Library](#)[Seven-Segment](#)[mod 3](#)[Half Adder](#)[2-Bits Adder](#)[Full Adder](#)[Binary Adder](#)

2-Bit Adder (testbench) II

Verilog

© C.M.

```
x0 = 0;
y1 = 0;
y0 = 0;

repeat (2) begin
    repeat (2) begin
        repeat (2) begin
            repeat (2) begin
                #30;
                $display(x1,x0," ",y1,y0," ",
                        f2,f1,f0);
                y0 = y0 + 1;
            end
            y1 = y1 + 1;
        end
    end
end
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

2-Bit Adder (testbench) III

Verilog

© C.M.

```
        x0 = x0 + 1;
    end
    x1 = x1 + 1;
end
$finish();
end

endmodule
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder


Full Adder

(The circuit is from the Logic Gates lecture)

Full Adder: Simplified Circuit

Verilog

© C.M.

 

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Listing 14: fullAdder.v

```
'timescale 1ns/1ns

module fullAdder(
    output f1,
    output f0,
    input  x,
    input  y,
    input  z
);

    andGate a1(xy,x,y);
    andGate a2(xz,x,z);
    andGate a3(yz,y,z);
```

[Primitives](#)[Demo: and3](#)[Library](#)[Seven-Segment](#)[mod 3](#)[Half Adder](#)[2-Bits Adder](#)[Full Adder](#)[Binary Adder](#)

```
    or3Gate  o1(f1,xy,xz,yz);  
    xor3Gate x1(f0,x,y,z);  
endmodule
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Listing 15: fullAdder_tb.v

```
'timescale 1ns/1ns

module fullAdder_tb;
    wire co, s;
    logic x, y, z;

    fullAdder fa(co,s,x,y,z);

    initial begin
        $dumpfile("fullAdder.vcd");
        $dumpvars;
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Full Adder: Testbench II

Verilog

© C.M.

```
x = 0;
y = 0;
z = 0;

repeat (2) begin
    repeat (2) begin
        repeat (2) begin
            #20ns;
            $display(x,y,z,co,s);
            z = z + 1;
        end
        y = y + 1;
    end
    x = x + 1;
end
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Full Adder: Testbench III

Verilog

© C.M.

```
        $finish();  
    end  
  
endmodule
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Binary Adder

(The circuit is from the Logic Gates lecture)

© C.M.



- Module parameters
- parameter definition
- bus declaration
- bus usage
- signed
- genvar definition

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Listing 16: binaryAdder.v

```
'timescale 1ns/1ns

module binaryAdder #(parameter WIDTH=1) (
    output cOut,
    output v,
    output [WIDTH-1:0] sum,
    input  [WIDTH-1:0] x,
    input  [WIDTH-1:0] y,
    input cIn
);
    wire [WIDTH-1:0] c;

    assign cOut = c[WIDTH-1];
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

```
generate
  if (WIDTH > 1)
    xorGate xg(v,c[WIDTH-1], c[WIDTH-2]);
  else
    xorGate xg(v,c[WIDTH-1], cIn);
endgenerate

fullAdder fa(c[0],sum[0],x[0],y[0],cIn);

for (genvar i = 1; i < WIDTH; i = i + 1)
begin
  fullAdder fa(c[i],sum[i],x[i],y[i],
               c[i-1]);
end
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Binary Adder (module) III

Verilog

© C.M.

```
endmodule
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Listing 17: binaryAdder_tb.v

```
'timescale 1ns/1ns

module binaryAdder_tb;
    parameter N = 8;

    wire c,v;
    wire [N-1:0] sum;
    logic [N-1:0] x, y;

    binaryAdder #(N) ba(c, v, sum, x, y, 1'b0);

    initial begin
        logic signed [N-1:0] sums, xs, ys;
```

[Primitives](#)[Demo: and3](#)[Library](#)[Seven-Segment](#)[mod 3](#)[Half Adder](#)[2-Bits Adder](#)[Full Adder](#)[Binary Adder](#)

Binary Adder: Testbench II

Verilog

© C.M.

```
$dumpfile("binaryAdder.vcd");
$dumpvars;

repeat (100) begin
    x = $urandom_range(0,2**N-1);
    y = $urandom_range(0,2**N-1);
    #60ns;
    xs = x;
    ys = y;
    sums = sum;
    $display("%d %d %d %d ** %d %d %d %d",
            x, y, sum, c,
            xs, ys, sums, v);
end
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

Binary Adder: Testbench III

Verilog

© C.M.

```
        $finish();  
    end  
  
endmodule
```

Primitives

Demo: and3

Library

Seven-Segment

mod 3

Half Adder

2-Bits Adder

Full Adder

Binary Adder

(Carmi) Lecture 9 reached here