

Computer Structure Assignment 3

Combinational Circuits

Carmi Merimovich

December 30, 2024

When asked to build a circuit you should supply:

1. A block diagram.
2. A circuit diagram.
3. A Verilog module with the **exact** signature as specified and with **identical** file name.

1. Follow the steps used in the lectures to build the module `binaryAdder` to build the module `binarySubtractor`. Thus:

- (a) Design, using **only** gates, the module

```
module fullSubtractor(  
    output bo,  
    output s,  
    input  x,y,bi);
```

- (b) Design, using **only** gates and `fullSubtractors`, the module

```
module binarySubtractor #(N) (  
    output b,  
    output v,  
    output [N-1:0] z,  
    input  [N-1:0] x, y,  
    input  bIn)
```

returning in `z` the value $x - y - bIn$ with `b` and `v` being the usual overflow flags.

2. Build a module with the signature

```
module negate #(N) (  
    output V,
```

```

        output [N-1:0] out,
        input  [N-1:0] in)

```

accepting a signed integer and returning its negation. *V* should be true if and only if there is an overflow.

The `binaryAdder` module can be used.

3. Build the module

```

module binarySubtractor1 #(N) (
    output b,
    output v,
    output [N-1:0] z,
    input  [N-1:0] x, y,
    input  bIn)

```

accepting two integers *x*, *y* and returning $x - y - bIn$ in *z*. The *b* and *v* flags are as in the `binaryAdder` module.

Use the `negate` module from the previous question.

The `binaryAdder` can be used.

4. Build an unsigned comparator module:

```

module #(N) comparator(
    output lt, eq, gt,
    input  [N-1:0] x,
    input  [N-1:0] y);

```

The behavior is as follows:

$$\begin{aligned}
 gt &= 1 \iff x > y \\
 eq &= 1 \iff x = y \\
 lt &= 1 \iff x < y
 \end{aligned}$$

5. Build a signed comparator module:

```

module #(N) comparatorSigned(
    output lt, eq, gt,
    input  [N-1:0] x,
    input  [N-1:0] y);

```

The behavior is the same as in the previous questions, just the numbers here are signed.

6. Build (from gates only) a 4×2 priority encoder

```

module encoderPri4(
    output v,
    output [1:0] z,
    input  [3:0] x);

```

7. Build a priority encoder giving the index of the minimal set input.

```
module encoderMin #(SEL) (
    output v,
    output [SEL-1:0] z,
    input  [2**SEL-1:0] x);
```

8. Build a reasonably efficient left and right shifters with the following signatures:

```
module shiftLeft #(SEL) (output [2**SEL-1:0] out,
    input [2**SEL-1:0] in,
    input [SEL-1:0] cnt);

module shiftRight #(SEL) (output [2**SEL-1:0] out, //Logic
    input [2**SEL-1:0] in,
    input [SEL-1:0] cnt);

module shiftARight #(SEL) (output [2**SEL-1:0] out, // Arithmetic
    input [2**SEL-1:0] in,
    input [SEL-1:0] cnt);
```

Note. In `shiftRight` the MSB gets a zero. In `shiftARight` the MSB is replicated. E.g.,

```
shift right      0111 ↦ 0011
shift right      1111 ↦ 0111
shift right arithmetic 0111 ↦ 0011
shift right arithmetic 1111 ↦ 1111
```

9. Build a binary Arithmetic Logic Unit with signature:

```
module alu #(N) (
    output [N-1:0] out,
    input  [N-1:0] in0,in1,
    input  [2:0] op
)
```

where:

op	Operation	
0	out = in0 + in1	addition
1	out = in0 - in1	subtraction
2	out = in0 & in1	bitwise and
3	out = in0 in1	bitwise or
4	out = ~ in0	bitwise not
5	out = in0 << in1	
6	out = in0 >> _u in1	unsignd shift
7	out = in0 >> _s in1	arithmetic shift

10. In this assignment we are interested only in the `bcdAdder` and `bcdSubtractor` modules. The detailed module list below is due to popular demand!

Binary Coded Decimal (BCD) is, well, a binary code for decimal numbers, e.g.;

$$(192)_{10} = (0001\ 1001\ 0010)_{\text{BCD}}.$$

BCD is a signed/magnitude method, where A, C, E, F code a non-negative number and B, D code negative number, e.g.,

$$(+192)_{10} = (1010\ 0001\ 1001\ 0010)_{\text{BCD}},$$

$$(-192)_{10} = (1011\ 0001\ 1001\ 0010)_{\text{BCD}}.$$

4 binary digits which are coding a digit or a sign are called **a nibble**.

- (a) Build a full bcd adder:

```
module bcdFullAdder(
    output cOut,
    output [3:0] z,
    input  [3:0] x,
    input  [3:0] y,
    input  cIn)
```

Your friends are `binaryAdder`, `binarySubtractor`, and `comparator`.

- (b) Build a full bcd subtractor:

```
module bcdFullSubtractor(
    output bOut,
    output [3:0] z,
    input  [3:0] x,
    input  [3:0] y,
    input  bIn)
```

Your friends are `binaryAdder`, `binarySubtractor`, and `comparator`.

- (c) Build the unsigned bcd adder. There are no sign nibbles here!

```
module bcdUAdder #(parameter N=1) (
    output cOut,
    output [3:0] z[N],
    input  [3:0] x[N],
    input  [3:0] y[N],
    input  cIn)
```

- (d) Build the unsigned bcd subtractor. There are no sign nibbles here!

```

module bcdUSubtractor #(parameter N=1) (
    output bOut,
    output [3:0] z[N],
    input [3:0] x[N],
    input [3:0] y[N],
    input bIn)

```

- (e) Build a BCD adder. Here the highest numbered nibbles are sign nibbles!

```

module #(N) bcdAdder(
    output c,
    output [3:0] z[N],
    input [3:0] x[N],
    input [3:0] y[N]);

```

Your friends are `bcdUAdder`, `bcdUSubtractor` and `comparator`. Knowledge of how signed decimal numbers addition is done by humans is assumed.

- (f) Build a BCD subtractor. Here the highest number nibbles are sign nibbles!

```

module #(N) bcdSubtractor(
    output bOut,
    output [3:0] z[N],
    input [3:0] x[N],
    input [3:0] y[N]);

```

Your friend is `bcdAdder`. (This is **really** simple) Knowledge of how signed decimal numbers subtraction is done by humans is assumed.

11. Build (from gates only) a negative decoder with a negative enable. I.e., the decoder is active when the enable line is clear. The output lines are in general set except for the selectd line.

```

module decoderNeg #(parameter SEL=1) (
    output [2**SEL-1:0] m,
    input [SEL-1:0] sel
);

```

The following is **optional**

12. (Not easy) Build an unsigned binary multiplier.

```

module #(N) multiply(
    output [N+N-1:0] z,
    input [N-1:0] x,y)

```

This is really easier than it looks (if optimizations are to be ignored, which they are). Use `muxes` to get either zero or the multiplicand for each bit in the multiplier. Use (wide) adders to add the shifted number we got out of the `muxes`.

13. (Even less easier) Build a unsigned binary divider.

Simple long division will do here.

Use the comparator module and the `binarySubtractor`. Again, `muxes` will decide if subtraction is done with the divider or with zero.