


Flipflops

© Carmi Merimovich

January 29, 2025

- A sequential system contains two parts
 - ▶ A combinational system
 - ▶ Memory
- (Hence, a **computer!**)
- Something like this:

Asynchronous

 

Very fast memory


Async analysis

Latch

Flipflops

- A sequential system contains two parts
 - ▶ A combinational system
 - ▶ Memory
- (Hence, a **computer**!)
- Something like this:

Synchronous

 

Clock signal



- A Clock generating circuit is **analog**
- We supply the clock module
- We have no interest in the veriloging of clock

Listing 1: clock_tb.v

```
'timescale 1ns/1ns

module clock_tb;
  wire clk;
  clock #(20ns) c(clk); // 20ns cycle
  initial begin
    $dumpfile("clock.vcd");
    $dumpvars;
    $monitor($time, " ", clk);
    #5000;
    $finish;
  end
endmodule;
```

(Fast) Memory units

Types

- Latches
- Flipflops

Computer **main** memory uses different components

- Latches and flipflops present their value constantly
- Memory chips present their value **only** on demand
 - ▶ (and are basically analog)

Very fast memory

Async analysis

Latch

Flipflops

Feedback loop



Very fast memory

Async analysis

Latch

Flipflops

How to analyze?


Feedback loop

Very fast memory

Async analysis

Latch


Flipflops

 

State table


x	y	X	Y
0	0	1	1
0	1	0	1
1	0	1	0
1	1	0	0

State Diagram

 

- Stable states yield memory
- No control of the stored value
- Race conditions!

 A feedback loop was translated to the combinational method!



S	R	x	y	X	Y
0	0	0	0	1	1
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	0	0
0	1	0	0	0	1
0	1	0	1	0	1
0	1	1	0	0	0
0	1	1	1	0	0

S	R	x	y	X	Y
1	0	0	0	1	0
1	0	0	1	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	1	0	0	0	0
1	1	0	1	0	0
1	1	1	0	0	0
1	1	1	1	0	0


SR-Latch State Diagram

Very fast memory

Async analysis

Latch

Flipflops

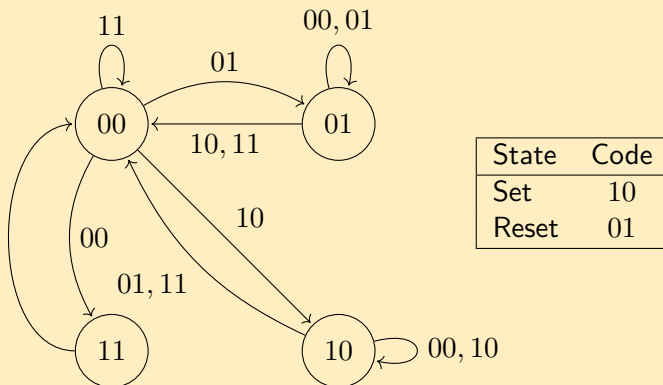


SR-Latch Component

Very fast memory

Async analysis

Latch

Flipflops

 

**Characteristic
Table**

S	R	Q^*
0	0	Q
0	1	0
1	0	1
1	1	??

**Characteristic
Equation**

$$Q^* = S + \bar{R}Q$$

Q^* is arbitrary when returning from $SR = 11$ to $SR = 00$

- Race conditions can happen
 - ▶ The latch is active **all the time**
- Synthesizing circuits is possible
- We will prefer simpler (e.g., *D*-latch) components

Listing 2: demo/02_srLatch/srLatch.v

```
'timescale 1ns/1ns

module srLatch(
    output q,
    output qn,
    input s,
    input r
);

    wire n0, n1;
    norGate ng0(n0, r, n1);
    norGate ng1(n1, s, n0);
```

SR Latch II

```
assign q    = n0;  
assign qn   = n1;  
  
endmodule
```

Very fast memory

Async analysis

Latch

Flipflops

Listing 3: demo/02_srLatch/srLatch_tb.v

```
'timescale 1ns/1ns

module srLatch_tb;
    logic s,r;
    wire q, qn;

    srLatch sr(q, qn, s ,r);

    initial begin
        logic x,y;

        $dumpfile("srLatch.vcd");
        $dumpvars;
```



```
x = 0;
y = 0;

repeat (2) begin
    repeat (2) begin
        s = x;
        r = y;
        #40ns;

        s = 0;
        r = 0;
        #40ns;
        y = y + 1;
```

Very fast memory

Async analysis

Latch

Flipflops

```
        end
        x = x + 1;
    end

    #1000ns;
    $finish;
end

endmodule
```


Gated SR-Latch

Very fast memory

Async analysis


Latch

Flipflops

 

- $E = 0$: Behavior as if $SR = 00$
- $E = 1$: Behavior as a simple SR-latch

Component

 

Listing 4: demo/03_sreLatch/srLatch.v

```
'timescale 1ns/1ns

module sreLatch(
    output q,
    output qn,
    input e,
    input s,
    input r
);

    wire se, re;
    andGate as(se, e, s);
    andGate ar(re, e, r);
```

```
wire n0, n1;  
norGate ng0(n0, re, n1);  
norGate ng1(n1, se, n0);  
  
assign q    = n0;  
assign qn   = n1;  
  
endmodule
```

Very fast memory

Async analysis

Latch

Flipflops

Listing 5: demo/03_sreLatch/sreLatch_tb.v

```
'timescale 1ns/1ns

module sreLatch_tb;
    logic e, s,r;
    wire q, qn;

    sreLatch sre(q, qn, e, s ,r);

    initial begin
        logic x,y;

        $dumpfile("sreLatch.vcd");
        $dumpvars;
```

```
x = 0;
y = 0;
e = 0;

repeat (4) begin
  repeat (2) begin
    repeat (2) begin
      s = x;
      r = y;
      #40ns;

      s = 0;
      r = 0;
```

Very fast memory


Async analysis

Latch

Flipflops

```
        #40ns;  
        y = y + 1;  
    end  
    x = x + 1;  
end  
e = e + 1;  
end  
  
#1000ns;  
$finish;  
end  
  
endmodule
```


Component

 

Q can change only on the raising edge of CLK

$\bar{Q}$ is exposed because it **exists** internally


Very fast memory

Async analysis

Latch

Flipflops

SR-Flipflop State Diagram

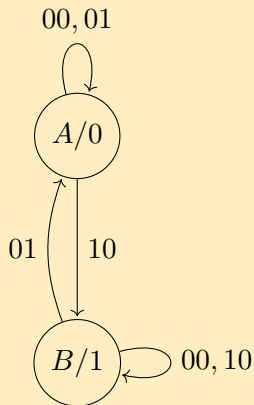

SR-Flipflop Characteristic Table and Equation

**Characteristic
Table**

S	R	$Q(t + 1)$
0	0	Q
0	1	0
1	0	1
1	1	??


**Characteristic
Equation**

$$Q(t + 1) = S + \bar{R}Q$$

when $S = 0$ or $R = 0$

SR-Flipflop Implementation Example

Master-Slave Implementation

 

Q_1 changes **only** when E switches from 0 to 1!

Very fast memory

Async analysis

Latch

Flipflops

Listing 6: demo/04_srFF/srFF.v

```
'timescale 1ns/1ns

module srFF(
    output q,
    output qn,
    input s,
    input r,
    input clk
);

    wire clk_n;
    notGate n(clk_n, clk);
```

```
wire q1,q1n;  
sreLatch sr1(q1,q1n,clk,s,r);  
sreLatch sr2(q,qn,clk,q1,q1n);  
  
endmodule
```

Very fast memory

Async analysis

Latch

Flipflops

Listing 7: demo/04_srFF/srFF_tb.v

```
'timescale 1ns/1ns

module srFF_tb;
    logic s,r;
    wire q, qn;

    wire clk;

    clock #(100) c(clk);

    srFF sr(q, qn, s, r, clk);

    logic x,y,even;
```

```
initial begin

    $dumpfile("srFF.vcd");
    $dumpvars;

    x = 0;
    y = 0;
    s = 0;
    r = 0;
    even = 0;

    #2000ns;
    $finish;
end
```



```
always @(posedge clk) begin
    if (even == 0) begin
        s = 0;
        r = 0;
    end else begin
        y = y + 1;
        if (y == 0) begin
            x = x + 1;
            if (x == 0) y = y + 1;
        end
        s = x;
        r = y;
    end
    even = even + 1;
end
```

SR Flipflop IV

```
end
```

```
endmodule
```

Very fast memory

Async analysis

Latch

Flipflops

(Carmi) Lecture 14 reached here



D-Flipflop

Very fast memory

Async analysis

Latch


Flipflops

  

$$Q(t + 1) = D$$

- On the raising edge of the clock, D is used.
- Then the flipflop freezes
- This is a very very short time in respect to the cycle time

D-Flipflop State Diagram

 

D-Flipflop Characteristic Table and Equation

**Characteristic
Table**

D	$Q(t + 1)$
0	0
1	1

**Characteristic
Equation**

$$Q(t + 1) = D$$


D-Flipflop Implementation Example

Very fast memory

Async analysis

Latch

Flipflops

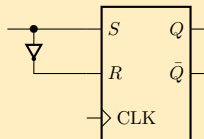

Listing 8: demo/05_dFF/dFF.v

```
'timescale 1ns/1ns

module dFF(
    output q,
    output qn,
    input d,
    input clk
);

    wire dn;
    notGate n(dn, d);
```


D Flipflop II

```
srFF sr(q,qn,d,dn,clk);  
  
endmodule
```

Very fast memory

Async analysis

Latch

Flipflops

Listing 9: demo/05_dFF/dFF_tb.v

```
'timescale 1ns/1ns

module dFF_tb;
    logic d;
    wire q, qn;

    wire clk;

    clock #(100) c(clk);

    dFF dff(q, qn, d, clk);

    logic x;
```

```
initial begin

    $dumpfile("dFF.vcd");
    $dumpvars;

    d = 0;

    #2000ns;
    $finish;
end

always @(posedge clk) begin
    d = d + 1;
end
```

D Flipflop III

```
endmodule
```

Very fast memory

Async analysis

Latch

Flipflops

(Carmi) Lecture 15 reached here



- Seems as if a lecture was given twice...
- Apparently there is Christmas vacation on Wed.

Very fast memory

Async analysis

Latch

Flipflops

  Component	Verilog
	<code>dff1(q,qn,d,set,reset,clk)</code>
	<code>srff1(q,qn,S,R,set,reset,clk)</code>