

Counters

© Carmi Merimovich

January 29, 2025

(Carmi) BALAGAN Lecture 17 begins here

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

Binary Counters

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

Binary Counter

1. Naive with D-FF
2. Naive with SR-FF
3. Naive 1-hot D-FF
4. Better states code DFF
5. No nonsense D-FF

Binay Counter

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

FSM

Gray Code


2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

State Diagram

 

State Table

state	next state
<i>A</i>	<i>B</i>
<i>B</i>	<i>C</i>
<i>C</i>	<i>D</i>
<i>D</i>	<i>E</i>
<i>E</i>	<i>A</i>

Binary Counter v1, State Codes

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

State	Code		
	Q_2	Q_1	Q_0
<i>A</i>	0	0	0
<i>B</i>	0	0	1
<i>C</i>	0	1	0
<i>D</i>	0	1	1
<i>E</i>	1	0	0

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

State Table

state			next state			Output		
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	X_2	X_1	X_0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	0
0	1	0	0	1	1	0	1	1
0	1	1	1	0	0	1	0	0
1	0	0	0	0	0	1	0	1

Binary Counter v1 (Equations)

D-FF input equations

$$D_2 = Q_1 Q_0$$

$$D_1 = Q_1 \oplus Q_0$$

$$D_0 = \bar{Q}_2 \bar{Q}_0$$

Output equations

$$X_2 = Q_2 + Q_1 Q_0$$

$$X_1 = Q_1 \oplus Q_0$$

$$X_0 = \bar{Q}_0$$

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

Listing 1: demo/01_counter/counter.v

```
'timescale 1ns/1ns

module counter(
    output x2,x1,x0,
    input  init,
    input  clk
);
    wire q2,q2n,q1,q1n,q0,q0n;
    wire d2,d1,d0;

    dff0 dff0(q2,q2n,d2,1'b0,init,clk);
    dff1 dff1(q1,q1n,d1,1'b0,init,clk);
    dff2 dff2(q0,q0n,d0,1'b0,init,clk);
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

```
andGate cd2(d2,q1 ,q0 );  
xorGate cd1(d1,q1 ,q0 );  
andGate cd0(d0,q2n,q0n);
```

```
orGate cx2(x2,q2,d2);  
assign x1=d1;  
assign x0=q0n;
```

```
endmodule
```

Listing 2: demo/01_counter/counter_tb.v

```
'timescale 1ns/1ns

module counter_tb;

    wire clk;
    clock #(100) c(clk);

    logic init;
    wire x2, x1, x0;
    counter c5(x2, x1, x0, init, clk);

    initial begin
```

```
$dumpfile("counter.vcd");  
$dumpvars;  
  
init = 1;  
#100ns;  
init = 0;  
  
#2000ns;  
$finish;  
end  
  
endmodule
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

The Same Binary Counter Implemented with SR-FF

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

State Table

state			next state			SR-FF					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	0	0	X	1	0	0	1
0	1	0	0	1	1	0	X	X	0	1	0
0	1	1	1	0	0	1	0	0	1	0	1
1	0	0	0	0	0	0	1	0	X	0	X

SR-FF input equations

$$S_2 = Q_1 Q_0$$

$$R_2 = Q_2$$

$$S_1 = Q_1 \oplus Q_0$$

$$R_1 = Q_1 Q_0$$

$$S_0 = \bar{Q}_2 \bar{Q}_0$$

$$R_0 = \bar{Q}_2 Q_0$$

Output equations (Same as with D-FF)

$$X_2 = Q_2 + Q_1 Q_0$$

$$X_1 = Q_1 \oplus Q_0$$

$$X_0 = \bar{Q}_0$$

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

Listing 3: demo/02_counter/counter.v

```
'timescale 1ns/1ns

module counter(
    output x2,x1,x0,
    input  init,
    input  clk
);
    wire q2,q2n,q1,q1n,q0,q0n;
    wire s2,r2,s1,r1,s0,r0;

    srffi srff0(q2,q2n,s2,r2,1'b0,init,clk);
    srffi srff1(q1,q1n,s1,r1,1'b0,init,clk);
    srffi srff2(q0,q0n,s0,r0,1'b0,init,clk);
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

```
andGate cs2(s2,q1 ,q0 );
assign r2=q2;
xorGate cs1(s1,q1 ,q0 );
andGate cr1(r1,q1 ,q0 );
norGate cs0(s0,q2 ,q0 );
andGate cr0(r0,q2n,q0);
```

```
orGate cx2(x2,q2,s2);
assign x1=s1;
assign x0=q0n;
```

```
endmodule
```

Listing 4: demo/02_counter/counter_tb.v

```
'timescale 1ns/1ns

module counter_tb;

    wire clk;
    clock #(100) c(clk);

    logic init;
    wire x2, x1, x0;
    counter c5(x2, x1, x0, init, clk);

    initial begin
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

```
$dumpfile("counter.vcd");  
$dumpvars;  
  
init = 1;  
#100ns;  
init = 0;  
  
#2000ns;  
$finish;  
end  
  
endmodule
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

Same Counter, 1-Hot with D-FF

Binary Counter v3, State Codes

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

State	Code				
	Q_4	Q_3	Q_2	Q_1	Q_0
<i>A</i>	0	0	0	0	1
<i>B</i>	0	0	0	1	0
<i>C</i>	0	0	1	0	0
<i>D</i>	0	1	0	0	0
<i>E</i>	1	0	0	0	0

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

State Table

state					next state				
Q_4	Q_3	Q_2	Q_1	Q_0	Q_4	Q_3	Q_2	Q_1	Q_0
0	0	0	0	1	0	0	0	1	0
0	0	0	1	0	0	0	1	0	0
0	0	1	0	0	0	1	0	0	0
0	1	0	0	0	1	0	0	0	0
1	0	0	0	1	0	0	0	0	1

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

Output functions

state					Output		
Q_4	Q_3	Q_2	Q_1	Q_0	X_2	X_1	X_0
0	0	0	0	1	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	1	0	0	0	1	0	0
1	0	0	0	0	1	0	1

D-FF input equations

$$D_4 = Q_3$$

$$D_3 = Q_2$$

$$D_2 = Q_1$$

$$D_1 = Q_0$$

$$D_0 = Q_4$$

Output equations

$$X_2 = Q_3 + Q_4$$

$$X_1 = Q_1 + Q_2$$

$$X_0 = Q_0 + Q_2 + Q_4$$

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

Listing 5: demo/03_counter/counter.v

```
'timescale 1ns/1ns

module counter(
    output x2,x1,x0,
    input  init,
    input  clk
);
    wire  q4,q4n,q3,q3n,q2,q2n,q1,q1n,q0,q0n;
    wire  d4,d3,d2,d1,d0;

    dfffi dff4(q4,q4n,d4,1'b0,init,clk);
    dfffi dff3(q3,q3n,d3,1'b0,init,clk);
    dfffi dff2(q2,q2n,d2,1'b0,init,clk);
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

```
dff1 dff1(q1,q1n,d1,1'b0,init,clk);  
dff0 dff0(q0,q0n,d0,init,1'b0,clk);
```

```
assign d4=q3;  
assign d3=q2;  
assign d2=q1;  
assign d1=q0;  
assign d0=q4;
```

```
orGate   cx2(x2,q3,q4);  
orGate   cx1(x1,q1,q2);  
or3Gate  cx0(x0,q0,q2,q4);
```

```
endmodule
```

Listing 6: demo/03_counter/counter_tb.v

```
'timescale 1ns/1ns

module counter_tb;

    wire clk;
    clock #(100) c(clk);

    logic init;
    wire x2, x1, x0;
    counter c5(x2, x1, x0, init, clk);

    initial begin
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

```
$dumpfile("counter.vcd");  
$dumpvars;  
  
init = 1;  
#100ns;  
init = 0;  
  
#2000ns;  
$finish;  
end  
  
endmodule
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

Same Counter with D-FF, Better Code

Binary Counter v4, States Codes

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

State	Code		
	Q_2	Q_1	Q_0
<i>A</i>	0	0	1
<i>B</i>	0	1	0
<i>C</i>	0	1	1
<i>D</i>	1	0	0
<i>E</i>	1	0	1

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

State Table

state			next state			Output		
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	X_2	X_1	X_0
0	0	1	0	1	0	0	0	1
0	1	0	0	1	1	0	1	0
0	1	1	1	0	0	0	1	1
1	0	0	1	0	1	1	0	0
1	0	1	0	0	1	1	0	1

Next State and Output are Equal

D-FF input equations

$$D_2 = \overline{Q_1 \oplus Q_0}$$

$$D_1 = Q_2 \downarrow Q_1 + Q_2 \downarrow Q_0$$

$$D_0 = Q_2 + Q_2 \downarrow Q_0$$

Output equations

$$X_2 = Q_2$$

$$X_1 = Q_1$$

$$X_0 = Q_0$$

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

Listing 7: demo/04_counter/counter.v

```
'timescale 1ns/1ns

module counter(
    output x2,x1,x0,
    input  init,
    input  clk
);
    wire q2,q2n,q1,q1n,q0,q0n;
    wire d2,d1,d0;

    dff1 dff2(q2,q2n,d2,1'b0,init,clk);
    dff1 dff1(q1,q1n,d1,1'b0,init,clk);
    dff1 dff0(q0,q0n,d0,init,1'b0,clk);
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

```
xnorGate cd2(d2,q1 ,q0 );

wire q2norq1,q2norq0;
norGate cq2q1(q2norq1,q2,q1);
norGate cq2q0(q2norq0,q2,q0);
orGate cd1(d1,q2norq1,q2norq0);

orGate cd0(d0,q2,q2norq0);

assign x2=q2;
assign x1=q1;
assign x0=q0;

endmodule
```



FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

Listing 8: demo/04_counter/counter_tb.v

```
'timescale 1ns/1ns

module counter_tb;

    wire clk;
    clock #(100) c(clk);

    logic init;
    wire x2, x1, x0;
    counter c5(x2, x1, x0, init, clk);

    initial begin
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

```
$dumpfile("counter.vcd");  
$dumpvars;  
  
init = 1;  
#100ns;  
init = 0;  
  
#2000ns;  
$finish;  
end  
  
endmodule
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

Same Counter, binaryAdder and Comparator

Listing 9: demo/05_counter/counter.v

```
'timescale 1ns/1ns

module counter(
    output x2,x1,x0,
    input  init,
    input  clk
);
    wire [2:0] q;
    wire [2:0] d;

    dfffi dff2(q[2],,d[2],1'b0,init,clk);
    dfffi dff1(q[1],,d[1],1'b0,init,clk);
    dfffi dff0(q[0],,d[0],init,1'b0,clk);
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

```
wire [2:0] e[2];
assign e[1] = 3'b001;
binaryAdder #(3) ba(,,e[0],q,3'b001,1'b0);

wire eq;
comparator #(3) com(,eq,,q,3'b101);

muxMulti #(1,3) mm(d,e,eq);

assign x2=q[2];
assign x1=q[1];
assign x0=q[0];
```

```
endmodule
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

Listing 10: demo/05_counter/counter_tb.v

```
'timescale 1ns/1ns

module counter_tb;

    wire clk;
    clock #(100) c(clk);

    logic init;
    wire x2, x1, x0;
    counter c5(x2, x1, x0, init, clk);

    initial begin
```

```
$dumpfile("counter.vcd");  
$dumpvars;  
  
init = 1;  
#100ns;  
init = 0;  
  
#2000ns;  
$finish;  
end  
  
endmodule
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

(Carmi) BALAGAN Lecture 17 reached here

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

Gray Counters

1-Bit difference between successive lines

1-bit

0

1

2-bits 3-bits

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

1-Bit difference between successive lines

1-bit	2-bits	3-bits
0	0	
1	1	

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

1-Bit difference between successive lines

1-bit	2-bits	3-bits
0	0	
1	1	
	1	
	0	

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

1-Bit difference between successive lines

1-bit	2-bits	3-bits
0	00	
1	01	
	1	
	0	

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

1-Bit difference between successive lines

1-bit	2-bits	3-bits
0	00	
1	01	
	11	
	10	

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

1-Bit difference between successive lines

1-bit	2-bits	3-bits
0	00	00
1	01	01
	11	11
	10	10

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

1-Bit difference between successive lines

1-bit	2-bits	3-bits
0	00	00
1	01	01
	11	11
	10	10
		10
		11
		01
		00

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

1-Bit difference between successive lines

1-bit	2-bits	3-bits
0	00	000
1	01	001
	11	011
	10	010
		10
		11
		01
		00

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

1-Bit difference between successive lines

1-bit	2-bits	3-bits
0	00	000
1	01	001
	11	011
	10	010
		110
		111
		101
		100

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF


3b Gray Counter SRFF

3b Gray Counter 1-hot

2-Bit Gray Counter

2-Bit Gray Counter

 - No input
- 2-Bits output (the state code)



FSM

Gray Code

2b Gray Counter


3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

2-Bit Gray Counter

State Diagram

 

State Table

state	next state
<i>A</i>	<i>B</i>
<i>B</i>	<i>C</i>
<i>C</i>	<i>D</i>
<i>D</i>	<i>A</i>

In this case, we use the output for state code

State	Code
<i>A</i>	00
<i>B</i>	01
<i>C</i>	11
<i>D</i>	10

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

State		Next State	
Q_1	Q_0	Q_1	Q_0
0	0	0	1
0	1	1	1
1	1	1	0
1	0	0	0


FF input equations

$$D_1 = Q_0$$

$$D_0 = \bar{Q}_1$$

2-Bit Gray Counter

Circuit

 

Initial state?

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

2-Bit Gray Counter with Initialization

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

If not told otherwise

- The FFs can be with or without sets or resets
- Both pins can be either active low or active high

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

Listing 11: demo/065_gray2/gray2.v

```
'timescale 1ns/1ns

module gray2(
    output x1,x0,
    input  init,
    input  clk
);

    wire  q0,q0n,q1,q1n;

    dff#1 d1(q1,q1n,q0,1'b0,init,clk);
    dff#1 d0(q0,q0n,q1n,1'b0,init,clk);
```

2-Bits Gray Counter II

```
    assign x1 = q1;  
    assign x0 = q0;  
  
endmodule
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

Listing 12: demo/06_gray2/gray2_tb.v

```
'timescale 1ns/1ns

module gray2_tb;
    logic d;
    wire q, qn;

    wire clk;

    clock #(100) c(clk);

    logic init;
    wire x1, x0;
    gray2 g(x1, x0, init, clk);
```

```
initial begin

    $dumpfile("gray2.vcd");
    $dumpvars;

    init = 1;
    #100ns;
    init = 0;

    #2000ns;
    $finish;
end

endmodule
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

2-Bits Gray Counter III



FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter DFF

(using D-FFs)

3-Bit Gray Counter

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter

FSM

Gray Code


2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

State Diagram

 

State Table

state	next state
<i>A</i>	<i>B</i>
<i>B</i>	<i>C</i>
<i>C</i>	<i>D</i>
<i>D</i>	<i>E</i>
<i>E</i>	<i>F</i>
<i>F</i>	<i>G</i>
<i>G</i>	<i>H</i>

Once again, the output is the state code

State	Code		
	Q_2	Q_1	Q_0
<i>A</i>	0	0	0
<i>B</i>	0	0	1
<i>C</i>	0	1	0
<i>D</i>	0	1	1
<i>E</i>	1	0	0
<i>F</i>	1	0	1
<i>G</i>	1	1	0
<i>H</i>	1	1	1

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

State Table

state			next state		
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	1	1	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	1	0	0
1	1	0	1	1	1
1	1	1	1	0	1

3-Bit Gray Counter (D -FF Input Equations)

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

$$D_2 = Q_1\bar{Q}_0 + Q_2Q_0 + Q_2Q_1$$

$$D_1 = \bar{Q}_2Q_0 + \bar{Q}_2Q_1 + Q_1\bar{Q}_0$$

$$D_0 = \bar{Q}_2\bar{Q}_1 + Q_2Q_1$$

3-Bit Gray Counter (D -FF Circuits)

FSM




Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

   

3-Bit Gray Counter (D -FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter (D -FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter (D -FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter (D -FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter (D -FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter (D -FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter (D -FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

$$D_2 = Q_1 \bar{Q}_0 + Q_2 Q_0 + Q_2 Q_1$$

3-Bit Gray Counter (D -FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

$$D_2 = Q_1 \bar{Q}_0 + Q_2 Q_0 + Q_2 Q_1$$

3-Bit Gray Counter (D -FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

$$D_2 = Q_1 \bar{Q}_0 + Q_2 Q_0 + Q_2 Q_1$$

3-Bit Gray Counter (D -FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

$$D_2 = Q_1 \bar{Q}_0 + Q_2 Q_0 + Q_2 Q_1$$

3-Bit Gray Counter (*D*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

$$D_2 = Q_1 \bar{Q}_0 + Q_2 Q_0 + Q_2 Q_1$$

3-Bit Gray Counter (D -FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

$$D_1 = \bar{Q}_2 Q_0 + \bar{Q}_2 Q_1 + Q_1 \bar{Q}_0$$

3-Bit Gray Counter (*D*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

$$D_1 = \bar{Q}_2 Q_0 + \bar{Q}_2 Q_1 + Q_1 \bar{Q}_0$$

3-Bit Gray Counter (*D*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

$$D_1 = \bar{Q}_2 Q_0 + \bar{Q}_2 Q_1 + Q_1 \bar{Q}_0$$

3-Bit Gray Counter (*D*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

$$D_1 = \bar{Q}_2 Q_0 + \bar{Q}_2 Q_1 + Q_1 \bar{Q}_0$$

3-Bit Gray Counter (*D*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

$$D_1 = \bar{Q}_2 Q_0 + \bar{Q}_2 Q_1 + Q_1 \bar{Q}_0$$

3-Bit Gray Counter (*D*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter (*D*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter (*D*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter (*D*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter (D -FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

Listing 13: demo/07_gray3d/gray3.v

```
'timescale 1ns/1ns

module gray3(
    output x2,x1,x0,
    input  init,
    input  clk
);
    wire q2,q2n,q1,q1n,q0,q0n;
    wire d2,d1,d0;

    wire a20,a21,a22;
    andGate and20(a20,q1,q0n);
    andGate and21(a21,q2,q0);
```

3-Bits Gray Counter II

```
andGate and22(a22,q2,q1);  
or3Gate o2(d2,a20,a21,a22);
```

```
wire a10,a11,a12;  
andGate and10(a10,q2n,q0);  
andGate and11(a11,q2n,q1);  
andGate and12(a12,q1,q0n);  
or3Gate o1(d1,a10,a11,a12);
```

```
xnorGate o0(d0,q1,q2);
```

```
dffi dff0(q2,q2n,d2,1'b0,init,clk);  
dffi dff1(q1,q1n,d1,1'b0,init,clk);  
dffi dff2(q0,q0n,d0,1'b0,init,clk);
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bits Gray Counter III

```
    assign x2 = q2;  
    assign x1 = q1;  
    assign x0 = q0;  
  
endmodule
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

Listing 14: demo/07_gray3d/gray3_tb.v

```
'timescale 1ns/1ns

module gray3_tb;

    wire clk;
    clock #(100) c(clk);

    logic init;
    wire x2, x1, x0;
    gray3 g(x2, x1, x0, init, clk);

    initial begin
```

3-Bits Gray Counter II

```
$dumpfile("gray3.vcd");
$dumpvars;

init = 1;
#100ns;
init = 0;

#2000ns;
$finish;
end

endmodule
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter

(using SR-FF)

- If we want the Q of D -FF to have some value
 - ▶ We set the D to this value
- If we want the Q of SR -FF to have some value
 - ▶ We need to use the **excitation table**

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

SR-FF Tables

Characteristic		
S	R	$Q(t+1)$
0	0	Q
0	1	0
1	0	1
1	1	X

Excitation			
Q	$Q(t+1)$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1						
0	0	1	0	1	1						
0	1	0	1	1	0						
0	1	1	0	1	0						
1	0	0	0	0	0						
1	0	1	1	0	0						
1	1	0	1	1	1						
1	1	1	1	0	1						

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X				
0	0	1	0	1	1						
0	1	0	1	1	0						
0	1	1	0	1	0						
1	0	0	0	0	0						
1	0	1	1	0	0						
1	1	0	1	1	1						
1	1	1	1	0	1						

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X		
0	0	1	0	1	1						
0	1	0	1	1	0						
0	1	1	0	1	0						
1	0	0	0	0	0						
1	0	1	1	0	0						
1	1	0	1	1	1						
1	1	1	1	0	1						

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1						
0	1	0	1	1	0						
0	1	1	0	1	0						
1	0	0	0	0	0						
1	0	1	1	0	0						
1	1	0	1	1	1						
1	1	1	1	0	1						

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1	0	X				
0	1	0	1	1	0						
0	1	1	0	1	0						
1	0	0	0	0	0						
1	0	1	1	0	0						
1	1	0	1	1	1						
1	1	1	1	0	1						

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1	0	X	1	0		
0	1	0	1	1	0						
0	1	1	0	1	0						
1	0	0	0	0	0						
1	0	1	1	0	0						
1	1	0	1	1	1						
1	1	1	1	0	1						

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1	0	X	1	0	X	0
0	1	0	1	1	0						
0	1	1	0	1	0						
1	0	0	0	0	0						
1	0	1	1	0	0						
1	1	0	1	1	1						
1	1	1	1	0	1						

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1	0	X	1	0	X	0
0	1	0	1	1	0	1	0				
0	1	1	0	1	0						
1	0	0	0	0	0						
1	0	1	1	0	0						
1	1	0	1	1	1						
1	1	1	1	0	1						

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1	0	X	1	0	X	0
0	1	0	1	1	0	1	0	X	0		
0	1	1	0	1	0						
1	0	0	0	0	0						
1	0	1	1	0	0						
1	1	0	1	1	1						
1	1	1	1	0	1						

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1	0	X	1	0	X	0
0	1	0	1	1	0	1	0	X	0	0	X
0	1	1	0	1	0						
1	0	0	0	0	0						
1	0	1	1	0	0						
1	1	0	1	1	1						
1	1	1	1	0	1						

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1	0	X	1	0	X	0
0	1	0	1	1	0	1	0	X	0	0	X
0	1	1	0	1	0	0	X				
1	0	0	0	0	0						
1	0	1	1	0	0						
1	1	0	1	1	1						
1	1	1	1	0	1						

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1	0	X	1	0	X	0
0	1	0	1	1	0	1	0	X	0	0	X
0	1	1	0	1	0	0	X	X	0		
1	0	0	0	0	0						
1	0	1	1	0	0						
1	1	0	1	1	1						
1	1	1	1	0	1						

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1	0	X	1	0	X	0
0	1	0	1	1	0	1	0	X	0	0	X
0	1	1	0	1	0	0	X	X	0	0	1
1	0	0	0	0	0						
1	0	1	1	0	0						
1	1	0	1	1	1						
1	1	1	1	0	1						

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1	0	X	1	0	X	0
0	1	0	1	1	0	1	0	X	0	0	X
0	1	1	0	1	0	0	X	X	0	0	1
1	0	0	0	0	0	0	1				
1	0	1	1	0	0						
1	1	0	1	1	1						
1	1	1	1	0	1						

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1	0	X	1	0	X	0
0	1	0	1	1	0	1	0	X	0	0	X
0	1	1	0	1	0	0	X	X	0	0	1
1	0	0	0	0	0	0	1	0	X		
1	0	1	1	0	0						
1	1	0	1	1	1						
1	1	1	1	0	1						

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1	0	X	1	0	X	0
0	1	0	1	1	0	1	0	X	0	0	X
0	1	1	0	1	0	0	X	X	0	0	1
1	0	0	0	0	0	0	1	0	X	0	X
1	0	1	1	0	0						
1	1	0	1	1	1						
1	1	1	1	0	1						

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1	0	X	1	0	X	0
0	1	0	1	1	0	1	0	X	0	0	X
0	1	1	0	1	0	0	X	X	0	0	1
1	0	0	0	0	0	0	1	0	X	0	X
1	0	1	1	0	0	X	0				
1	1	0	1	1	1						
1	1	1	1	0	1						

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1	0	X	1	0	X	0
0	1	0	1	1	0	1	0	X	0	0	X
0	1	1	0	1	0	0	X	X	0	0	1
1	0	0	0	0	0	0	1	0	X	0	X
1	0	1	1	0	0	X	0	0	X		
1	1	0	1	1	1						
1	1	1	1	0	1						

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1	0	X	1	0	X	0
0	1	0	1	1	0	1	0	X	0	0	X
0	1	1	0	1	0	0	X	X	0	0	1
1	0	0	0	0	0	0	1	0	X	0	X
1	0	1	1	0	0	X	0	0	X	0	1
1	1	0	1	1	1						
1	1	1	1	0	1						

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1	0	X	1	0	X	0
0	1	0	1	1	0	1	0	X	0	0	X
0	1	1	0	1	0	0	X	X	0	0	1
1	0	0	0	0	0	0	1	0	X	0	X
1	0	1	1	0	0	X	0	0	X	0	1
1	1	0	1	1	1	X	0				
1	1	1	1	0	1						

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1	0	X	1	0	X	0
0	1	0	1	1	0	1	0	X	0	0	X
0	1	1	0	1	0	0	X	X	0	0	1
1	0	0	0	0	0	0	1	0	X	0	X
1	0	1	1	0	0	X	0	0	X	0	1
1	1	0	1	1	1	X	0	X	0		
1	1	1	1	0	1						

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1	0	X	1	0	X	0
0	1	0	1	1	0	1	0	X	0	0	X
0	1	1	0	1	0	0	X	X	0	0	1
1	0	0	0	0	0	0	1	0	X	0	X
1	0	1	1	0	0	X	0	0	X	0	1
1	1	0	1	1	1	X	0	X	0	1	0
1	1	1	1	0	1						

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1	0	X	1	0	X	0
0	1	0	1	1	0	1	0	X	0	0	X
0	1	1	0	1	0	0	X	X	0	0	1
1	0	0	0	0	0	0	1	0	X	0	X
1	0	1	1	0	0	X	0	0	X	0	1
1	1	0	1	1	1	X	0	X	0	1	0
1	1	1	1	0	1	X	0				

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1	0	X	1	0	X	0
0	1	0	1	1	0	1	0	X	0	0	X
0	1	1	0	1	0	0	X	X	0	0	1
1	0	0	0	0	0	0	1	0	X	0	X
1	0	1	1	0	0	X	0	0	X	0	1
1	1	0	1	1	1	X	0	X	0	1	0
1	1	1	1	0	1	X	0	0	1		

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1	0	X	1	0	X	0
0	1	0	1	1	0	1	0	X	0	0	X
0	1	1	0	1	0	0	X	X	0	0	1
1	0	0	0	0	0	0	1	0	X	0	X
1	0	1	1	0	0	X	0	0	X	0	1
1	1	0	1	1	1	X	0	X	0	1	0
1	1	1	1	0	1	X	0	0	1	X	0

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF)

State and FF inputs

state			next state			FF inputs					
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	S_2	R_2	S_1	R_1	S_0	R_0
0	0	0	0	0	1	0	X	0	X	1	0
0	0	1	0	1	1	0	X	1	0	X	0
0	1	0	1	1	0	1	0	X	0	0	X
0	1	1	0	1	0	0	X	X	0	0	1
1	0	0	0	0	0	0	1	0	X	0	X
1	0	1	1	0	0	X	0	0	X	0	1
1	1	0	1	1	1	X	0	X	0	1	0
1	1	1	1	0	1	X	0	0	1	X	0

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter (SR-FF Input Equations)

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

state			
Q_2	Q_1	Q_0	
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

3-Bit Gray Counter (SR-FF Input Equations)

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

state			
Q_2	Q_1	Q_0	S_2
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	X
1	1	0	X
1	1	1	X

$$S_2 = Q_1 \bar{Q}_0$$

3-Bit Gray Counter (SR-FF Input Equations)

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

state			
Q_2	Q_1	Q_0	R_2
0	0	0	X
0	0	1	X
0	1	0	0
0	1	1	X
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

$$S_2 = Q_1 \bar{Q}_0$$

$$R_2 = \bar{Q}_1 \bar{Q}_0$$

3-Bit Gray Counter (SR-FF Input Equations)

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

state			
Q_2	Q_1	Q_0	S_1
0	0	0	0
0	0	1	1
0	1	0	X
0	1	1	X
1	0	0	0
1	0	1	0
1	1	0	X
1	1	1	0

$$S_2 = Q_1 \bar{Q}_0$$

$$R_2 = \bar{Q}_1 \bar{Q}_0$$

$$S_1 = \bar{Q}_2 Q_0$$

3-Bit Gray Counter (SR-FF Input Equations)

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

state			
Q_2	Q_1	Q_0	R_1
0	0	0	X
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	X
1	0	1	X
1	1	0	0
1	1	1	1

$$S_2 = Q_1 \bar{Q}_0$$

$$R_2 = \bar{Q}_1 \bar{Q}_0$$

$$S_1 = \bar{Q}_2 Q_0$$

$$R_1 = Q_2 Q_0$$

3-Bit Gray Counter (SR-FF Input Equations)

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

state			
Q_2	Q_1	Q_0	S_0
0	0	0	1
0	0	1	X
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	X

$$S_2 = Q_1 \bar{Q}_0$$

$$R_2 = \bar{Q}_1 \bar{Q}_0$$

$$S_1 = \bar{Q}_2 Q_0$$

$$R_1 = Q_2 Q_0$$

$$S_0 = Q_2 Q_1 + \bar{Q}_2 \bar{Q}_1$$

3-Bit Gray Counter (SR-FF Input Equations)

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

state			
Q_2	Q_1	Q_0	R_0
0	0	0	0
0	0	1	0
0	1	0	X
0	1	1	1
1	0	0	X
1	0	1	1
1	1	0	0
1	1	1	0

$$S_2 = Q_1 \bar{Q}_0$$

$$R_2 = \bar{Q}_1 \bar{Q}_0$$

$$S_1 = \bar{Q}_2 Q_0$$

$$R_1 = Q_2 Q_0$$

$$S_0 = Q_2 Q_1 + \bar{Q}_2 \bar{Q}_1$$

$$R_0 = \bar{Q}_2 Q_1 + Q_2 \bar{Q}_1$$

3-Bit Gray Counter (SR-FF Input Equations)

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

state			
Q_2	Q_1	Q_0	
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

$$S_2 = Q_1 \bar{Q}_0$$

$$R_2 = \bar{Q}_1 \bar{Q}_0$$

$$S_1 = \bar{Q}_2 Q_0$$

$$R_1 = Q_2 Q_0$$

$$S_0 = Q_2 Q_1 + \bar{Q}_2 \bar{Q}_1$$

$$R_0 = \bar{Q}_2 Q_1 + Q_2 \bar{Q}_1$$

3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter (SR -FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter (SR -FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter (SR -FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

©

3b Gray Counter 1-hot

$$S_2 = Q_1 \bar{Q}_0$$

©



3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

$$S_2 = Q_1 \bar{Q}_0$$

3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

$$R_2 = \bar{Q}_1 \bar{Q}_0$$

3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

$$R_2 = \bar{Q}_1 \bar{Q}_0$$

3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

$$R_2 = \bar{Q}_1 \bar{Q}_0$$

3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

$$S_1 = \bar{Q}_2 Q_0$$

3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

$$S_1 = \bar{Q}_2 Q_0$$

3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

$$S_1 = \overline{Q}_2 Q_0$$

3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

$$R_1 = Q_2 Q_0$$

3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

$$R_1 = Q_2 Q_0$$

3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

$$R_1 = Q_2 Q_0$$

3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

$$S_0 = \bar{Q}_2 \bar{Q}_1 + Q_2 Q_1$$

3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

$$S_0 = \bar{Q}_2\bar{Q}_1 + Q_2Q_1$$

3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bit Gray Counter (*SR*-FF Circuits)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

Listing 15: demo/08_gray3sr/gray3.v

```
'timescale 1ns/1ns

module gray3(
    output x2,x1,x0,
    input  init,
    input  clk
);
    wire q2,q2n,q1,q1n,q0,q0n;
    wire s2,r2,s1,r1,s0,r0;

    andGate as2(s2,q1,q0n);
    andGate ar2(r2,q1n,q0n);
```

3-Bits Gray Counter, SR-FF II

```
andGate  as1(s1,q2n,q0);
andGate  ar1(r1,q2,q0);

xnorGate as0(s0,q2,q1);
xorGate  ar0(r0,q2,q1);

srffi  srff0(q2,q2n,s2,r2,1'b0,init,clk);
srffi  srff1(q1,q1n,s1,r1,1'b0,init,clk);
srffi  srff2(q0,q0n,s0,r0,1'b0,init,clk);

assign x2 = q2;
assign x1 = q1;
assign x0 = q0;

endmodule
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bits Gray Counter, SR-FF III



FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

Listing 16: demo/08_gray3sr/gray3_tb.v

```
'timescale 1ns/1ns

module gray3_tb;

    wire clk;
    clock #(100) c(clk);

    logic init;
    wire x2, x1, x0;
    gray3 g(x2, x1, x0, init, clk);

    initial begin
```

3-Bits Gray Counter, SR-FF II

```
$dumpfile("gray3.vcd");  
$dumpvars;  
  
init = 1;  
#100ns;  
init = 0;  
  
#2000ns;  
$finish;  
end  
  
endmodule
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

(Carmi) Lecture 16 reached here

- We need to repeat the gray 3 bits variants

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF


3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter with Up/Down Controls

(1-hot D -FFs)

3-Bit Gray Counter with Up/Down (1-hot)

 

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

The control lines are up and down

up	down	Behavior
1	X	go up
0	1	go down
0	0	stay

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bit Gray Counter with Up/Down (1-hot)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

State	Q_7	Q_6	Q_5	Q_4	Q_3	Q_2	Q_1	Q_0
<i>A</i>	0	0	0	0	0	0	0	1
<i>B</i>	0	0	0	0	0	0	1	0
<i>C</i>	0	0	0	0	1	0	0	0
<i>D</i>	0	0	0	0	0	1	0	0
<i>E</i>	0	1	0	0	0	0	0	0
<i>F</i>	1	0	0	0	0	0	0	0
<i>G</i>	0	0	1	0	0	0	0	0
<i>H</i>	0	0	0	1	0	0	0	0

Recall for D-FF, $Q(t+1) = D$

3-Bits Gray Counter, Equations (1-hot)

Rather trivial

$$D_0 = \overline{\text{up}} \cdot \overline{\text{down}} \cdot Q_0 + \text{up} \cdot Q_4 + \overline{\text{up}} \cdot \text{down} \cdot Q_1$$

$$D_1 = \overline{\text{up}} \cdot \overline{\text{down}} \cdot Q_1 + \text{up} \cdot Q_0 + \overline{\text{up}} \cdot \text{down} \cdot Q_3$$

$$D_3 = \overline{\text{up}} \cdot \overline{\text{down}} \cdot Q_3 + \text{up} \cdot Q_1 + \overline{\text{up}} \cdot \text{down} \cdot Q_2$$

$$D_2 = \overline{\text{up}} \cdot \overline{\text{down}} \cdot Q_2 + \text{up} \cdot Q_3 + \overline{\text{up}} \cdot \text{down} \cdot Q_6$$

$$D_6 = \overline{\text{up}} \cdot \overline{\text{down}} \cdot Q_6 + \text{up} \cdot Q_2 + \overline{\text{up}} \cdot \text{down} \cdot Q_7$$

$$D_7 = \overline{\text{up}} \cdot \overline{\text{down}} \cdot Q_7 + \text{up} \cdot Q_6 + \overline{\text{up}} \cdot \text{down} \cdot Q_5$$

$$D_5 = \overline{\text{up}} \cdot \overline{\text{down}} \cdot Q_5 + \text{up} \cdot Q_7 + \overline{\text{up}} \cdot \text{down} \cdot Q_4$$

$$D_4 = \overline{\text{up}} \cdot \overline{\text{down}} \cdot Q_4 + \text{up} \cdot Q_0 + \overline{\text{up}} \cdot \text{down} \cdot Q_5$$

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bits Gray Counter, Circuit (1-hot)

Counters



FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bits Gray Counter, Circuit (1-hot)

Counters



FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot



3-Bits Gray Counter, Circuit (1-hot)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bits Gray Counter, Circuit (1-hot)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bits Gray Counter, Circuit (1-hot)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bits Gray Counter, Circuit (1-hot)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bits Gray Counter, Circuit (1-hot)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bits Gray Counter, Circuit (1-hot)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

©



3-Bits Gray Counter, Circuit (1-hot)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

3-Bits Gray Counter, Circuit (1-hot)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

©



3-Bits Gray Counter, Circuit (1-hot)

FSM


Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

 

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

Listing 17: demo/09_gray3hot/gray3.v

```
'timescale 1ns/1ns

module calc(
    output goto,
    input  up,
    input  down,
    input  prev,
    input  curr,
    input  next
);
    wire upn,downn;
    notGate n1(upn,up);
    notGate n2(downn,down);
```

3-Bits Gray Counter, Module (1-hot) II

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

```
wire stay,goDown,goUp;
and3Gate aStay(stay,upn,downn,curr);
and3Gate aDown(goDown,upn,down,next);
andGate aUp(goUp,up,prev);

or3Gate o(goto,stay,goDown,goUp);
endmodule

module gray3(
    output [2:0] x,
    input up,down,
    input init,
    input clk
);
```

3-Bits Gray Counter, Module (1-hot) III

```
wire [7:0] d,q;

dff1 dff(q[0],,d[0],init,1'b0,clk);
for (genvar i = 1; i < 8; i++)
    dff1 dff(q[i],,d[i],1'b0,init,clk);

calc c0(d[0],up,down,q[4],q[0],q[1]);
calc c1(d[1],up,down,q[0],q[1],q[3]);
calc c3(d[3],up,down,q[1],q[3],q[2]);
calc c2(d[2],up,down,q[3],q[2],q[6]);
calc c6(d[6],up,down,q[2],q[6],q[7]);
calc c7(d[7],up,down,q[6],q[7],q[5]);
calc c5(d[5],up,down,q[7],q[5],q[4]);
calc c4(d[4],up,down,q[5],q[4],q[0]);
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

3-Bits Gray Counter, Module (1-hot) IV

```
encoder #(3) e(x,q);  
  
endmodule
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

Listing 18: demo/09_gray3hot/gray3_tb.v

```
'timescale 1ns/1ns

module gray3_tb;

    wire clk;
    clock #(100) c(clk);

    logic init;
    logic up, down;
    wire [2:0] x;
    gray3 g(x, up,down, init, clk);

    initial begin
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot

```
$dumpfile("gray3.vcd");
$dumpvars;

init = 1;
up = 1;
down = 0;
#70ns;
init = 0;

#2000ns;
$finish;
end

always @(posedge clk) begin
```

3-Bits Gray Counter, Testbench (1-hot) III

```
    up = $urandom_range(0,1);  
    down = $urandom_range(0,1);  
end  
  
endmodule
```

FSM

Gray Code

2b Gray Counter

3b Gray Counter DFF

3b Gray Counter SRFF

3b Gray Counter 1-hot