

Serial Input

© Carmi Merimovich

January 29, 2025

Mod 3

disjoint 11011

overlap 11011

Modulo 3 of Serial Input

Modulo 3 of Serial Input Example

Mod 3

disjoint 11011

overlap 11011

Input	Number	Output
		00
01	01	01
10	0110	00
11	011011	00
⋮	⋮	⋮

It **looks** as if infinite states are needed

Mod 3

disjoint 11011

overlap 11011

$$3n \times 4 = 12n$$

$$3n \times 4 + 1 = 12n + 1$$

$$3n \times 4 + 2 = 12n + 2$$

$$3n \times 4 + 3 = 12n + 3$$

$$(3n + 1) \times 4 = 12n + 3 + 1$$

$$(3n + 1) \times 4 + 1 = 12n + 3 + 2$$

$$(3n + 1) \times 4 + 2 = 12n + 6$$

$$(3n + 1) \times 4 + 3 = 12n + 6 + 1$$

$$(3n + 2) \times 4 = 12n + 6 + 2$$

$$(3n + 2) \times 4 + 1 = 12n + 9$$

$$(3n + 2) \times 4 + 2 = 12n + 9 + 1$$

Modulo 3 State Diagram


Serial Input

©

Mod 3

disjoint 11011

overlap 11011

 

The output is the state code

Modulo 3 State Table

Serial Input

©

Mod 3

disjoint 11011

overlap 11011

Q_1	Q_0	X_1	X_0	$Q_1(t+1)$	$Q_0(t+1)$	D_1	D_0
0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	1
0	0	1	0	1	0	1	0
0	0	1	1	0	0	0	0
0	1	0	0	0	1	0	1
0	1	0	1	1	0	1	0
0	1	1	0	0	0	0	0
0	1	1	1	0	1	0	1
1	0	0	0	1	0	1	0
1	0	0	1	0	0	0	0
1	0	1	0	0	1	0	1
1	0	1	1	1	0	1	0

Modulo 3 State Equations

Serial Input



Mod 3

disjoint 11011

overlap 11011

$$D_1 = \bar{Q}_1\bar{Q}_0X_1\bar{X}_0 + \bar{Q}_1Q_0\bar{X}_1X_0 + Q_1\bar{Q}_0\bar{X}_1\bar{X}_0 + Q_1\bar{Q}_0X_1X_0$$

$$D_0 = \bar{Q}_1\bar{Q}_0\bar{X}_1X_0 + \bar{Q}_1Q_0\bar{X}_1\bar{X}_0 + \bar{Q}_1Q_0X_1X_0 + Q_1\bar{Q}_0X_1\bar{X}_0$$

Listing 1: demo/10_mod3/mod3.v

```
'timescale 1ns/1ns

module mod3(
    output m1,m0,
    input  x1,x0,
    input  init,
    input  clk
);
    wire x1n, x0n;
    notGate n1(x1n,x1);
    notGate n0(x0n,x0);

    wire q1, q1n, q0, q0n;
```

Mod 3

disjoint 11011

overlap 11011

```
wire a1, a2, a4, a5, a7, a8, aA, aB;
```

```
and4Gate ag1(a1,q1n,q0n,x1n,x0 );
```

```
and4Gate ag2(a2,q1n,q0n,x1 ,x0n);
```

```
and4Gate ag4(a4,q1n,q0 ,x1n,x0n);
```

```
and4Gate ag5(a5,q1n,q0 ,x1n,x0 );
```

```
and4Gate ag7(a7,q1n,q0 ,x1 ,x0 );
```

```
and4Gate ag8(a8,q1 ,q0n,x1n,x0n);
```

```
and4Gate agA(aA,q1 ,q0n,x1 ,x0n);
```

```
and4Gate agB(aB,q1 ,q0n,x1 ,x0 );
```

```
wire d1,d0;
```

```
or4Gate o1(d1,a2,a5,a8,aB);
```

```
or4Gate o2(d0,a1,a4,a7,aA);
```

```
dffi dff1(q1,q1n,d1,1'0b,init,clk);  
dffi dff0(q0,q0n,d0,1'0b,init,clk);  
  
assign m1 = q1;  
assign m0 = q0;  
  
endmodule
```

Listing 2: demo/10_mod3/mod3_tb.v

```
'timescale 1ns/1ns

module mod3_tb;

    wire clk;
    clock #(100) c(clk);

    logic init;
    logic x1, x0;
    wire m1, m0;

    mod3 g(m1, m0, x1, x0, init, clk);
```

Mod 3

disjoint 11011

overlap 11011

```
initial begin

    $dumpfile("mod3.vcd");
    $dumpvars;

    x1 = 1;
    x0 = 0;

    init = 1;
    #100ns;
    init = 0;

    #2000ns;
    $finish;
end
```

```
always @(posedge clk) begin
    $display(m1,m0);
end
endmodule
```

Mod 3

disjoint 11011

overlap 11011

Mod 3

disjoint 11011

overlap 11011

Identifying disjoint “11011”

disjoint “11011” Serial Input Example

Mod 3

disjoint 11011

overlap 11011

Input	Number	Output
		0
1	1	0
1	11	0
0	110	0
1	1101	0
1	11011	1
0	110110	0
⋮	⋮	⋮

disjoint 11011 State Diagram


Serial Input

©

Mod 3

disjoint 11011

overlap 11011

 

State Codes

Name	Q_5	Q_4	Q_3	Q_2	Q_1	Q_0
	0	0	0	0	0	1
1	0	0	0	0	1	0
11	0	0	0	1	0	0
110	0	0	1	0	0	0
1101	0	1	0	0	0	0
11011	1	0	0	0	0	0

disjoint “11011” State Table

Serial Input

©

Mod 3

disjoint 11011

overlap 11011

Q_5	Q_4	Q_3	Q_2	Q_1	Q_0	X	Q_5	Q_4	Q_3	Q_2	Q_1	Q_0
0	0	0	0	0	1	0	0	0	0	0	0	1
0	0	0	0	0	1	1	0	0	0	0	1	0
0	0	0	0	1	0	0	0	0	0	0	0	1
0	0	0	0	1	0	1	0	0	0	1	0	0
0	0	0	1	0	0	0	0	0	1	0	0	0
0	0	0	1	0	0	1	0	0	0	1	0	0
0	0	1	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	1	0	1	0	0	0	0
0	1	0	0	0	0	0	0	0	0	0	0	1
0	1	0	0	0	0	1	1	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	0	1
1	0	0	0	0	0	1	0	0	0	0	1	0

disjoint “11011” FF Equations

Serial Input

©

Mod 3

disjoint 11011

overlap 11011

$$D_5 = Q_4 X$$

$$D_4 = Q_3 X$$

$$D_3 = Q_2 \bar{X}$$

$$D_2 = Q_1 X + Q_2 X$$

$$D_1 = Q_0 X + Q_5 X$$

$$D_0 = Q_0 \bar{X} + Q_1 \bar{X} + Q_3 \bar{X} + Q_4 \bar{X} + Q_5 \bar{X}$$

Output Equation

$$Z = Q_5$$

Listing 3: demo/20_disjoint/disjoint11011.v

```
'timescale 1ns/1ns

module disjoint11011(
    output z,
    input  x,
    input  init,
    input  clk
);

    wire q5,q5n,q4,q4n,q3,q3n,q2,q2n,q1,q1n,q0,q0n;
    wire d5,d4,d3,d2,d1,d0;
    dfffi dff5(q5,q5n,d5,1'b0,init,clk);
    dfffi dff4(q4,q4n,d4,1'b0,init,clk);
```

Mod 3

disjoint 11011

overlap 11011

```
dfffi dff3(q3,q3n,d3,1'b0,init,clk);  
dfffi dff2(q2,q2n,d2,1'b0,init,clk);  
dfffi dff1(q1,q1n,d1,1'b0,init,clk);  
dfffi dff0(q0,q0n,d0,init,1'b0,clk);
```

```
assign z = q5;
```

```
wire xn;  
notGate n(xn,x);
```

```
andGate cd5(d5,q4,x);  
andGate cd4(d4,q3,x);  
andGate cd3(d3,q2,xn);
```

```
wire q1x,q2x;
```

Mod 3

disjoint 11011

overlap 11011

```
andGate cq1x(q1x,q1,x);
andGate cq2x(q2x,q2,x);
orGate cd2(d2,q1x,q2x);

wire q0x,q5x;
andGate cq0x(q0x,q0,x);
andGate cq5x(q5x,q5,x);
orGate cd1(d1,q0x,q5x);

andGate cd0(d0,q2n,xn);

endmodule
```

Listing 4: demo/02_disjoint11011/disjoint11011_tb.v

```
'timescale 1ns/1ns

module disjoint11011_tb;

    wire clk;
    clock #(100) c(clk);

    logic init;
    logic x;
    wire z;

    disjoint11011 g(z, x, init, clk);
```

```
initial begin
```

```
    $dumpfile("disjoint11011.vcd");  
    $dumpvars;
```

```
    init = 1;  
    #100ns;  
    init = 0;  
    x = 1;
```

```
    #2000ns;  
    $finish;
```

```
end
```

```
always @(posedge clk) begin
```

Mod 3

disjoint 11011

overlap 11011

Disjoint 11011 Testbench III

```
    if ($urandom_range(0,5) == 0)
        x = 0;
    else
        x = 1;
    end
endmodule
```

Mod 3

disjoint 11011

overlap 11011

Mod 3

disjoint 11011

overlap 11011

Identifying overlap “11011”

overlap “11011” Serial Input Example

Serial Input

©

Mod 3

disjoint 11011

overlap 11011

Input	Number	Output
		0
1	1	0
1	11	0
0	110	0
1	1101	0
1	11011	1
0	110110	0
1	1101101	0
1	11011011	1
⋮	⋮	⋮

overlap 11011 State Diagram


Serial Input

©

Mod 3

disjoint 11011

overlap 11011

 

State Codes

Name	Q_5	Q_4	Q_3	Q_2	Q_1	Q_0
	0	0	0	0	0	1
1	0	0	0	0	1	0
11	0	0	0	1	0	0
110	0	0	1	0	0	0
1101	0	1	0	0	0	0
11011	1	0	0	0	0	0

overlap "11011" State Table

Serial Input

©

Mod 3

disjoint 11011

overlap 11011

Q_5	Q_4	Q_3	Q_2	Q_1	Q_0	X	Q_5	Q_4	Q_3	Q_2	Q_1	Q_0
0	0	0	0	0	1	0	0	0	0	0	0	1
0	0	0	0	0	1	1	0	0	0	0	1	0
0	0	0	0	1	0	0	0	0	0	0	0	1
0	0	0	0	1	0	1	0	0	0	1	0	0
0	0	0	1	0	0	0	0	0	1	0	0	0
0	0	0	1	0	0	1	0	0	0	1	0	0
0	0	1	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	1	0	1	0	0	0	0
0	1	0	0	0	0	0	0	0	0	0	0	1
0	1	0	0	0	0	1	1	0	0	0	0	0
1	0	0	0	0	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	1	0	0

overlap “11011” FF Equations

Serial Input

©

Mod 3

disjoint 11011

overlap 11011

$$D_5 = Q_4 X$$

$$D_4 = Q_3 X$$

$$D_3 = Q_2 \bar{X} + Q_5 \bar{X}$$

$$D_2 = Q_1 X + Q_2 X + Q_5 X$$

$$D_1 = Q_0 X$$

$$D_0 = Q_0 \bar{X} + Q_1 \bar{X} + Q_3 \bar{X} + Q_4 \bar{X}$$

Output Equation

$$Z = Q_5$$

Listing 5: demo/03_overlap11011/overlap11011.v

```
'timescale 1ns/1ns

module overlap11011(
    output z,
    input  x,
    input  init,
    input  clk
);

    wire q5,q5n,q4,q4n,q3,q3n,q2,q2n,q1,q1n,q0,q0n;
    wire d5,d4,d3,d2,d1,d0;
    dfffi dff5(q5,q5n,d5,1'b0,init,clk);
    dfffi dff4(q4,q4n,d4,1'b0,init,clk);
```

Mod 3

disjoint 11011

overlap 11011

```
dfffi dff3(q3,q3n,d3,1'b0,init,clk);  
dfffi dff2(q2,q2n,d2,1'b0,init,clk);  
dfffi dff1(q1,q1n,d1,1'b0,init,clk);  
dfffi dff0(q0,q0n,d0,init,1'b0,clk);
```

```
assign z = q5;
```

```
wire xn;  
notGate n(xn,x);
```

```
wire q0x,q1x,q2x,q3x,q4x,q5x;  
andGate cq0x(q0x,q0,x);  
andGate cq1x(q1x,q1,x);  
andGate cq2x(q2x,q2,x);  
andGate cq3x(q3x,q3,x);
```

Mod 3

disjoint 11011

overlap 11011

```
andGate cq4x(q4x,q4,x);
andGate cq5x(q5x,q5,x);

wire q0xn,q1xn,q2xn,q3xn,q4xn,q5xn;
andGate cq0xn(q0xn,q0,xn);
andGate cq1xn(q1xn,q1,xn);
andGate cq2xn(q2xn,q2,xn);
andGate cq3xn(q3xn,q3,xn);
andGate cq4xn(q4xn,q4,xn);
andGate cq5xn(q5xn,q5,xn);

assign d5=q4x;
assign d4=q3x;
orGate cd3(d3,q2xn,q5xn);
```

Mod 3

disjoint 11011

overlap 11011

```
or3Gate cd2(d2,q1x,q2x,q5x);

assign d1=q0x;

or4Gate cd0(d0,q0xn,q1xn,q3xn,q4xn);

endmodule
```

Listing 6: demo/03_overlap11011/overlap11011_tb.v

```
'timescale 1ns/1ns

module overlap11011_tb;

    wire clk;
    clock #(100) c(clk);

    logic init;
    logic x;
    wire z;

    overlap11011 g(z, x, init, clk);
```

```
initial begin
```

```
    $dumpfile("overlap11011.vcd");  
    $dumpvars;
```

```
    init = 1;  
    #100ns;  
    init = 0;  
    x = 1;
```

```
    #2000ns;  
    $finish;
```

```
end
```

```
always @(posedge clk) begin
```

Mod 3

disjoint 11011

overlap 11011

overlap 11011 Testbench III

Serial Input



```
if ($urandom_range(0,5) == 0)
    x = 0;
else
    x = 1;
end
endmodule
```

Mod 3

disjoint 11011

overlap 11011

Mod 3

disjoint 11011

overlap 11011

Example: SR-FF from D-FF

Thus: D-FF is equivalent to SR-FF

State Diagram and Table


Serial Input

©

Mod 3

disjoint 11011

overlap 11011

 

State	S	R	Next State
A	0	0	A
A	0	1	A
A	1	0	B
A	1	1	X
B	0	0	B
B	0	1	A
B	1	0	B
B	1	1	X

State Code/Table/Equation

Serial Input

©

Mod 3

disjoint 11011

overlap 11011

State	Code
A	0
B	1

Q	S	R	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	X
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	X

$$Q(t+1) = S + \bar{R}Q$$

SR-FF from D-FF, FF Input Equation and Circuit

Serial Input


©

Mod 3

disjoint 11011

overlap 11011

$$D = S + \bar{R}Q$$

 

Circuit output is the state

(Carmi) Lecture 19(?!) reached here