

Registers

© Carmi Merimovich

January 29, 2025

Registers

1-Bit Register

v1

v2

 n -Bit Register

v1

v2

v3

The n -bit register, step by step

Registers

1-Bit Register

v1

v2

n -Bit Register

v1

v2

v3

- Registers are what software types call variables
- From hardware point of view these are **fast** variables
- Registers can be viewed as D-FFs with longer memory
- (and some other abilities)

1-Bit Register (v1)

Registers

1-Bit Register

v1


v2

n-Bit Register

v1

v2


v3

 

$$\text{out}(t + 1) = \begin{cases} \text{out} & \text{if load} = 0, \\ \text{in} & \text{if load} = 1. \end{cases}$$

(Kind of a strange SR-FF)

 1-Bit Register (v1), Possible Realization (circuit)



Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

Make a good realization with SR-FF

Listing 1: reg1bit.v

```
'timescale 1ns/1ns

module  reg1bit(
    output out,
    input  in,
    input  load,
    clk
);
    wire [1:0] options;
    wire q;

    assign options[0] = q;
    assign options[1] = in;
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

1-Bit Register (v1) (module) II

```
wire d;  
mux #(1) m(d, options, load);  
  
dff1 dff(q,,d,1'b0,1'b0,clk);  
  
assign out = q;  
  
endmodule
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

Listing 2: reg1bit_tb.v

```
'timescale 1ns/1ns

module reg1bit_tb;

    wire clk;
    clock #(80ns) c(clk);

    logic load, in;
    wire out;
    reg1bit r(out, in, load, clk);

    initial begin
        $dumpfile("reg1bit.vcd");
    end
endmodule
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

1-Bit Register (v1) (testbench) II

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

```
$dumpvars;

load = 0;
in = 0;

repeat (100) begin
    #220ns;
    if ($urandom_range(0,2) == 0)
        load = load + 1;
    if ($urandom_range(0,2) == 0)
        in = in + 1;
end
$finish;
end
endmodule;
```

1-Bit Register (v1) (testbench) III

Registers

1-Bit Register

v1

v2


n -Bit Register

v1

v2

v3

1-Bit Register (v2) (block)

 

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

$$\text{out}(t + 1) = \begin{cases} \text{in} & \text{if load} = 1, \\ 0 & \text{if reset} = 1, \\ \text{out} & \text{otherwise.} \end{cases}$$

- **Do not** set both load and reset at the same time
- Specific implementation behaves differently when both controls are set

1-Bit Register (v2) (circuit)

Registers

1-Bit Register

v1


v2

n-Bit Register

v1

v2

v3

 

- Realize the above with the `dff1` component
- Realize the above using the `v1` register

Listing 3: reg1bit.v

```
'timescale 1ns/1ns

module reg1bit(
    output out,
    input in,
    input load,
    input reset,
    clk
);
    wire d, q;
    wire [3:0] options;
    wire [1:0] s;
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

1-Bit Register v2 (module) II

```
assign s[1] = reset;  
assign s[0] = load;  
  
assign options[0] = q;  
assign options[1] = in;  
assign options[2] = 0;  
assign options[3] = 0;  
  
assign out = q;  
  
mux #(2) m(d, options, s);  
dff dff(q,,d,1'b0,1'b0,clk);  
  
endmodule
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

Listing 4: reg1bit_tb.v

```
'timescale 1ns/1ns

module reg1bit_tb;
    wire clk;
    clock #(80ns) c(clk);

    logic load, in, reset;
    wire out;
    reg1bit r(out, in, load, reset, clk);

    initial begin
        $dumpfile("reg1bit.vcd");
        $dumpvars;
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

1-Bit Register v2 (testbench) II

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

```
load = 0;
in = 0;
reset = 1;

repeat (100) begin
    #80ns;
    if (reset == 0) begin
        if ($urandom_range(0,5) == 0)
            reset++;
    end else begin
        if ($urandom_range(0,1) == 0)
            reset++;
    end
    if ($urandom_range(0,1) == 0)
```

1-Bit Register v2 (testbench) III

```
        load++;  
        if ($urandom_range(0,2) == 0)  
            in++;  
    end  
    $finish;  
end  
endmodule
```

Registers

1-Bit Register

v1

v2


n-Bit Register

v1

v2

v3

n -Bit Register v1 (block diagram)

 

Registers

1-Bit Register

v1

v2

n -Bit Register

v1

v2

v3

$$\text{out}(t+1) = \begin{cases} \text{in} & \text{if load} = 1, \\ 0 & \text{if reset} = 1, \\ \text{out} & \text{otherwise.} \end{cases}$$

- Do not set load and reset at the same time
- When both controls are set, unexpected behavior

n -Bit Register v1 (circuit)

Registers

1-Bit Register

v1


v2

n -Bit Register

v1

v2

v3

 

Registers

1-Bit Register

v1

v2

 n -Bit Register

v1

v2

v3

Listing 5: regNbit.v

```
'timescale 1ns/1ns

module regNbit #(parameter WIDTH=1) (
    output [WIDTH-1:0] out,
    input  [WIDTH-1:0] in,    // value to store
    input  load,              // true for load
    input  reset,             // true for reset
    input  clk
);
    for (genvar i = 0; i < WIDTH; i++)
        reg1bit r(out[i],in[i],load,reset,clk);
endmodule
```

Listing 6: regNbit.v

```
'timescale 1ns/1ns

module regNbit_tb;

    parameter WIDTH=8;

    wire clk;
    clock    #(80) c(clk);

    logic load, reset;
    logic [WIDTH-1:0] in;
    wire  [WIDTH-1:0] out;
```

Registers

1-Bit Register

v1

v2

 n -Bit Register

v1

v2

v3

n -Bit Register v1 (testbench) II

```
regNbit #(WIDTH) r(out,in,load,
                    reset,clk);

initial begin
    $dumpfile("regNbit.vcd");
    $dumpvars;

    load = 0;
    in = 0;
    reset = 1;

    repeat (100) begin
        #80ns;
        if (reset == 0) begin
            if ($urandom_range(0,5) == 0)
```

Registers

1-Bit Register

v1

v2

 n -Bit Register

v1

v2

v3

n-Bit Register v1 (testbench) III

```
        reset++;
    end else begin
        if ($urandom_range(0,1) == 0)
            reset++;
        end
        if ($urandom_range(0,1) == 0)
            load++;
            if ($urandom_range(0,2) == 0)
                in = $urandom_range(0,2**WIDTH-1);
            end
        $finish;
    end
end

endmodule
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

n -Bit Register v2 (block diagram)

Registers

1-Bit Register

v1


v2

 n -Bit Register

v1

v2

v3

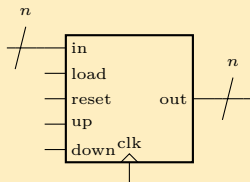

$$\text{out}(t+1) = \begin{cases} \text{in} & \text{if load} = 1, \\ \text{out} + 1 & \text{if up} = 1, \quad (+ \text{ is addition}) \\ \text{out} - 1 & \text{if down} = 1, \\ 0 & \text{if reset} = 1, \\ \text{out} & \text{otherwise.} \end{cases}$$

- Set **only one** of load, reset, up and down at a time

Listing 7: register.v

```
'timescale 1ns/1ns

module  register #(parameter WIDTH=1) (
    output [WIDTH-1:0] out,
    input  [WIDTH-1:0] in,    // value to store
    input  down,
    input  up,
    input  load,              // true for load
    input  reset,             // true for reset
    input  clk
);

    wire [2:0] sel;
```

Registers

1-Bit Register

v1

v2

 n -Bit Register

v1

v2

v3

n-bit register v2 (module) II

```
assign sel[2] = load;
assign sel[1] = up;
assign sel[0] = down;

wire [WIDTH-1:0] options[7:0];
for (genvar i=4; i < 8; i++)
    assign options[i] = in;
for (genvar i=2; i < 4; i++)
    assign options[i] = oneMore;
assign options[1] = oneLess;
assign options[0] = d;

wire [WIDTH-1:0] oneMore,d;
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

n -bit register v2 (module) III

```
binaryAdder #(WIDTH) a(, , oneMore, d,
    {{WIDTH-1{1'b0}},1'b1},1'b0);

wire [WIDTH-1:0] oneLess;
binaryAdder #(WIDTH) s(, , oneLess, d,
    {{WIDTH{1'b1}}},1'b0);

wire [WIDTH-1:0] in;
muxMulti #(3,WIDTH) m(in, options, sel);

regNbit #(WIDTH) r(d, in, load, reset, clk);

endmodule
```

Registers

1-Bit Register

v1

v2

 n -Bit Register

v1

v2

v3

n -bit register v2 (module) IV

Registers



Registers

1-Bit Register

v1

v2

n -Bit Register

v1

v2

v3

Listing 8: register_tb.v

```
'timescale 1ns/1ns

module register_tb;

    parameter WIDTH=8;

    wire clk;
    clock    #(80) c(clk);

    logic load, reset, up, down;
    logic [WIDTH-1:0] in;
    wire [WIDTH-1:0] out;
```

Registers

1-Bit Register

v1

v2

 n -Bit Register

v1

v2

v3

n -bit register v2 (Testbench) II

```
register #(WIDTH) r(out,in,down,up,load,reset,clk);

initial begin
    $dumpfile("register.vcd");
    $dumpvars;

    load = 0;
    in = 0;
    reset = 1;

    repeat (100) begin
        #80ns;
        if (reset == 0) begin
            if ($urandom_range(0,5) == 0)
                reset++;
        end
    end
end
```

Register

1-Bit Register

v1

v2

 n -Bit Register

v1

v2

v3

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

```
        end else begin
            if ($urandom_range(0,1) == 0)
                reset++;
            end
            if ($urandom_range(0,1) == 0)
                load++;
            if ($urandom_range(0,2) == 0)
                in = $urandom_range(0,2**WIDTH-1);
            end
            $finish;
        end
    end

endmodule
```

n -Bit Register v3 (block diagram)

Registers

1-Bit Register

v1


v2

 n -Bit Register

v1

v2

v3

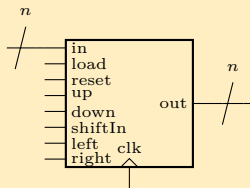

$$\text{out}(t+1) = \begin{cases} \text{in} & \text{if load} = 1, \\ \text{out} + 1 & \text{if up} = 1, \quad (+ \text{ is addition}) \\ \text{out} - 1 & \text{if down} = 1, \\ \text{out} \ll 1 + \text{shiftIn} & \text{if left} = 1, \\ \text{out} \gg 1 + \text{shiftIn} \times 2^{n-1} & \text{if right} = 1, \\ 0 & \text{if reset} = 1, \\ \text{out} & \text{otherwise.} \end{cases}$$

Registers

1-Bit Register

v1

v2

 n -Bit Register

v1

v2

v3

Listing 9: register.v

```
'timescale 1ns/1ns

module  register #(parameter WIDTH=1) (
    output [WIDTH-1:0] out,
    input  [WIDTH-1:0] in,    // value to store
    input  shiftIn,
    input  right,
    input  left,
    input  down,
    input  up,
    input  load,              // true for load
    input  reset,            // true for reset
    input  clk
```

```
);
```

```
wire [4:0] sel;  
wire [WIDTH-1:0] oneMore,d;  
wire [WIDTH-1:0] oneLess;  
wire [WIDTH-1:0] shiftLeft;  
wire [WIDTH-1:0] shiftRight;  
wire [WIDTH-1:0] in;  
  
assign sel[4] = load;  
assign sel[3] = up;  
assign sel[2] = down;  
assign sel[1] = left;  
assign sel[0] = right;
```

Registers

1-Bit Register

v1

v2

 n -Bit Register

v1

v2

v3

n-bit register v3 (module) III

```
wire [WIDTH-1:0] options[31:0];
for (genvar i=16; i < 32; i++)
    assign options[i] = in;
for (genvar i=8; i < 16; i++)
    assign options[i] = oneMore;
for (genvar i=4; i < 8; i++)
    assign options[i] = oneLess;
for (genvar i=2; i < 4; i++)
    assign options[i] = shiftLeft;
assign options[1] = shiftRight;
assign options[0] = d;

binaryAdder #(WIDTH) a(, , oneMore, d,
    {{WIDTH-1{1'b0}}}, 1'b1, 1'b0);
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

n-bit register v3 (module) IV

```
binaryAdder #(WIDTH) s(, oneLess, d,  
    {{WIDTH{1'b1}}}, 1'b0);
```

```
assign shiftLeft[0] = shiftIn;  
for (genvar i = 0; i < WIDTH-1; i++)  
    assign shiftLeft[i+1] = d[i];
```

```
assign shiftRight[WIDTH-1] = shiftIn;  
for (genvar i = 0; i < WIDTH-1; i++)  
begin: sr  
    assign shiftRight[i] = d[i+1];  
end
```

```
wire [WIDTH-1:0] value;
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

n -bit register v3 (module) V

```
muxMulti #(5,WIDTH) m(value, options, sel);

wire realLoad;
or5Gate o(realLoad,load,up,down,right,left);

regNbit #(WIDTH) rN(d, value, realLoad, reset, clk);

assign out=d;

endmodule
```

Registers

1-Bit Register

v1

v2

 n -Bit Register

v1

v2

v3

Listing 10: register_tb.v

```
'timescale 1ns/1ns

module register_tb;

    parameter WIDTH=8;

    wire clk;
    clock #(80) c(clk);

    logic load, reset, up, down, right, left;
    logic shiftIn;
    logic [WIDTH-1:0] in;
    wire [WIDTH-1:0] out;
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

Register v3 (Testbench) II

```
register #(WIDTH) r(out,in,shiftIn,
                    right,left,down,
                    up,load,reset,clk);

initial begin
    $dumpfile("register.vcd");
    $dumpvars;

    load = 0;
    in = 0;
    reset = 1;

    repeat (100) begin
        #80ns;
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

Register v3 (Testbench) III

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

```
    if (reset == 0) begin
        if ($urandom_range(0,5) == 0)
            reset++;
    end else begin
        if ($urandom_range(0,1) == 0)
            reset++;
    end
    if ($urandom_range(0,1) == 0)
        load++;
    if ($urandom_range(0,2) == 0)
        in = $urandom_range(0,2**WIDTH-1);
    end
    $finish;
end
```

Register v3 (Testbench) IV

```
endmodule
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

```
reg1bit(output out, input in,load,reset,clk)
regNbit #(N) (output [N-1:0]out,input [N-1:0]in,
              input load,reset,clk)
register #(N) (output [N-1:0]out,input [N-1:0]in,
              input shiftIn,right,left,down,up,
              load,reset,clk)
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

(Carmi) Lecture 20 reached here



Registers

1-Bit Register

v1

v2

 n -Bit Register

v1

v2

v3

Listing 11: register.v

```
'timescale 1ns/1ns

module seq (
    output found,
    input  in,
    input  clk
);

    wire [4:0]d;
    logic reset,up;
    register #(5) r(d, 5'b0,in,1'b1,1'b0,
                                1'b0,1'b0,1'b0,
                                1'b0, clk);
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

Overlapping Sequence (module) II

```
    comparator #(5) c(,found,,d,5'b01100);  
endmodule
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

Listing 12: register_tb.v

```
'timescale 1ns/1ns

module seq_tb;

    wire clk;
    clock #(500) c(clk);

    wire found;
    logic in;
    seq s(found,in,clk);

    initial begin
        $dumpfile("seq.vcd");
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

Overlapping Sequence (Testbench) II

```
$dumpvars;

in = 0;
#20000ns;

$finish;
end

always @(posedge(clk)) begin
    #5ns;
    in <= $urandom_range(0,1);
end

endmodule
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

Overlapping Sequence (Testbench) III

Registers

1-Bit Register

v1

v2

n -Bit Register

v1

v2

v3

Listing 13: register.v

```
'timescale 1ns/1ns

module seq (
    output found,
    input in,
    input reset,
    input clk
);

    wire [4:0]d;
    register #(5) r(d, 5'b0, in, 1'b1, 1'b0,
                    1'b0, 1'b0, 1'b0,
                    1'b0, clk);
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

Overlapping Sequence Fix (module) II

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

```
wire eq;
comparator #(5) cmp(,eq,,d,5'b01100);

wire [2:0]step;
wire work,up;

notGate n(up,work);
register #(3) cnt(step,3'b0,1'b0,1'b0,1'b0,
                1'b0,up,1'b0,reset,clk);
comparator #(3) cmp5(,work,,step,3'b101);

andGate mask(found,eq,work);
endmodule
```

Listing 14: register_tb.v

```
'timescale 1ns/1ns

module seq_tb;

    wire clk;
    clock #(500) c(clk);

    wire found;
    logic in;
    logic reset;

    seq s(found,in,reset,clk);
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

Overlapping Sequence Fix (Testbench) II

```
initial begin
    $dumpfile("seq.vcd");
    $dumpvars;

    in = 0;
    reset=1;
    #350ns;
    reset=0;

    #20000ns;

    $finish;
end

always @(posedge(clk)) begin
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

Overlapping Sequence Fix (Testbench) III

```
#5ns;  
in <= $urandom_range(0,1);  
end
```

```
endmodule
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

Listing 15: register.v

```
'timescale 1ns/1ns

module seq (
    output found,
    input  in,
    input  reset,
    input  clk
);

    wire [4:0]d;
    register #(5) r(d, 5'b0,in,1'b1,1'b0,
                    1'b0,1'b0,1'b0,
                    reset, clk);
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

```
wire eq;
comparator #(5) cmp(,eq,,d,5'b01100);

wire [2:0]step;
wire work,up;

orGate o(realReset,reset,work);

register #(3) cnt(step,3'b0,1'b0,1'b0,1'b0,
                1'b0,1'b1,1'b0,realReset,clk);
comparator #(3) cmp5(,work,,step,3'b100);

andGate mask(found,eq,work);
endmodule
```

Registers

1-Bit Register

v1

v2

n -Bit Register

v1

v2

v3

Listing 16: register_tb.v

```
'timescale 1ns/1ns

module seq_tb;

    wire clk;
    clock #(500) c(clk);

    wire found;
    logic in;
    logic reset;

    seq s(found,in,reset,clk);
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

Disjoint Sequence (Testbench) II

```
initial begin
    $dumpfile("seq.vcd");
    $dumpvars;

    in = 0;
    reset=1;
    #350ns;
    reset=0;

    #20000ns;

    $finish;
end

always @(posedge(clk)) begin
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

Disjoint Sequence (Testbench) III

```
#5ns;  
in <= $urandom_range(0,1);  
end
```

```
endmodule
```

Registers

1-Bit Register

v1

v2

n-Bit Register

v1

v2

v3

(Carmi) Lecture 21 reached here

1. The above took way longer than expected
2. The RTL attempt was disaster
3. We will redo next time