

Register Transfer Level (RTL)

© Carmi Merimovich

February 4, 2025

$$\sum_{i=0}^n i \text{ comb.}$$

$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples


$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

Discussion: $\sum_{i=0}^n i$

 $\sum_{i=0}^n i$ combinational circuit (block)



RTL

©C.M.

$\sum_{i=0}^n i$ comb.

$\sum_{i=0}^n i$ program
Method 1

Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

$\sum_{i=0}^5 i$ combinational circuit

RTL

©C.M.


$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
 Method 1
 Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

 

Listing 1: sum.v

```
'timescale 1ns/1ns

module sum #(parameter W=5,parameter N=5) (
    output [W-1:0] out
);
    wire [W-1:0] s[N+1];

    assign s[0] = 0;
    for (genvar i = 1; i <= N; i++) begin
        wire [W-1:0] t,ss;
        assign t = i;
        assign ss=s[i]; //for GTKwave
        binaryAdder #(W) a(,,s[i],s[i-1],
```

$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1
Method 2

RTL examples

($\sum_{i=0}^n i$ rtl
InvokeSum
Fibonacci

$\sum_{i=0}^n i$ combinational (verilog) II

```
                                t,1'b0);  
  
    end  
  
    assign out = s[N];  
endmodule
```

RTL

©C.M.

$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1
Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

Listing 2: sum_tb.v

```
'timescale 1ns/1ns

module sum_tb;

    parameter W = 24;
    parameter N = 1000;

    wire [W-1:0] out;

    sum #(W,N) s(out);

    initial begin
```

$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1
Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

$\sum_{i=0}^n i$ combinational (testbench) II

RTL

©C.M.

```
$dumpfile("sum.vcd");
```

```
$dumpvars;
```

```
#10000ns;
```

```
$display(out);
```

```
$finish();
```

```
end
```

```
endmodule;
```

$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1
Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

$\sum_{i=0}^n i$ combinational: So?

- Probably the fastest
- Lots of hardware
- It really is kind of insane
- What do we do if we need several N s?
- **Obviously we need a program**

RTL

©C.M.

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

$$\sum_{i=0}^n i \text{ comb.}$$

$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

$$\sum_{i=0}^n i$$

Program

$\sum_{i=0}^n i$ Program

```
sum = 0;
for (i = 0; i <= n; i++)
    sum = sum + i;
```

- We need to **build** the program
- Some concept of order should be introduced: States

RTL

©C.M.

$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1
Method 2


RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

 $\sum_{i=0}^n i$ State Diagram Approximation



We **Split** the design

1. Data path: **What** needs to be done
2. Control: **When** what needs to be done should be done

RTL

©C.M.

$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1
Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

$\sum_{i=0}^n i$ What needs to be Done

```
i ← 0
sum ← 0
i ← i + 1
sum ← sum + i
i ≤ n
```

RTL

©C.M.

$\sum_{i=0}^n i$ comb.

$\sum_{i=0}^n i$ program
Method 1

Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

$$\sum_{i=0}^n i \text{ comb.}$$

$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

Method 1: Control Controls the Controls

$\sum_{i=0}^n i$ Data Path (What **can** be done)

RTL

©C.M.

$$\sum_{i=0}^n i \text{ comb.}$$

$$\sum_{i=0}^n i \text{ program}$$

Method 1


Method 2

RTL examples

$$\sum_{i=0}^n i \cdot \text{rtl}$$

InvokeSum


Fibonacci

 

$\sum_{i=0}^n i$ Data Path (What **can** be done)

RTL

©C.M.

 

$$\sum_{i=0}^n i \text{ comb.}$$

$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum


Fibonacci

$$i \leftarrow 0$$

$\sum_{i=0}^n i$ Data Path (What **can** be done)

RTL

©C.M.

 

$$\sum_{i=0}^n i \text{ comb.}$$

$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

$$i \leftarrow i + 1$$

$\sum_{i=0}^n i$ Data Path (What **can** be done)

RTL

©C.M.

$$\sum_{i=0}^n i \text{ comb.}$$

$$\sum_{i=0}^n i \text{ program}$$

Method 1


Method 2

RTL examples

$$\sum_{i=0}^n i \cdot \text{rtl}$$

InvokeSum

Fibonacci

 


$$\text{sum} \leftarrow 0$$

$\sum_{i=0}^n i$ Data Path (What **can** be done)

RTL

©C.M.

 

$$\sum_{i=0}^n i \text{ comb.}$$

$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum


Fibonacci

$$\text{sum} \leftarrow \text{sum} + i$$

$\sum_{i=0}^n i$ Data Path (What **can** be done)

RTL

©C.M.

 

$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
 Method 1
 Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

Listing 3: demo/02_sum/sumDP.v

```
'timescale 1ns/1ns

module sumDP #(parameter W=1) (
    output [W-1:0] out ,
    output iLEn ,
    input iClear ,
    input iInc ,
    input sumClear ,
    input sumAdd ,
    input [W-1:0] n ,
    input clk
);
```

 $\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1

Method 2

RTL examples

 $\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

```
wire [W-1:0] sumOut;
wire [W-1:0] sumPi;
register #(W) sum(sumOut, sumPi, 1'b0,
                  1'b0, 1'b0,
                  1'b0, 1'b0,
                  sumAdd, sumClear,
                  clk);

assign out = sumOut;

wire [W-1:0] iOut;
register #(W) i(iOut, W'(0), 1'b0,
                1'b0, 1'b0,
                1'b0, iInc,
                iClear, 1'b0,
                clk);
```

 $\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1

Method 2

RTL examples

 $\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

```
binaryAdder #(W) ba(,,sumPi,sumOut,  
                    i0out,1'b0);
```

```
comparator #(W) com(lt,eq,,i0out,n);  
orGate o(iLEn,eq,lt);
```

```
endmodule
```

$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1

Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

$\sum_{i=0}^n i$ State Diagram

RTL

©C.M.


$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1
Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

 

name/iClear ilnc sumClear sumAdd

This is a **Mealy** machine

State Codes (1-hot)

Name	Code
init	001
loop	010
done	100

RTL

©C.M.

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

State Table and State Equations

RTL

©C.M.

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$
Method 1
Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

$T_2 T_1 T_0$ iLEn	Next $T_2 T_1 T_0$	iClear	iInc	sumClear	sumAdd
0 0 1 X	0 1 0	1	0	1	0
0 1 0 0	1 0 0	0	0	0	0
0 1 0 1	0 1 0	0	1	0	1
1 0 0 X	1 0 0	0	0	0	0

D-FFs so columns D_2, D_1, D_0 are not shown above

$$D_0 = 0$$

$$D_1 = T_0 + T_1 \text{iLEn}$$

$$D_2 = T_2 + T_1 \overline{\text{iLEn}}$$

$$\text{iClear} = T_0$$

$$\text{sumClear} = T_0$$

$$\text{iInc} = T_1 \text{iLTn}$$

$$\text{sumAdd} = T_1 \text{iLTn}$$

Control (circuit)

RTL

©C.M.


$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1
Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

 

Listing 4: 02_sumCTL.v

```
'timescale 1ns/1ns

module sumCTL (
    output iClear,
    output iInc,
    output sumClear,
    output sumAdd,
    input  iLEn,
    input  reset,
    input  clk
);

    wire t0,t1,t2,d0,d1,d2;
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
dff0 dff0(t0,,d0,reset,1'b0,clk);  
dff1 dff1(t1,,d1,1'b0,reset,clk);  
dff2 dff2(t2,,d2,1'b0,reset,clk);
```

```
assign d0=0;
```

```
wire iLEnn,t1LE,t1LEn;  
notGate ciLEnn(iLEnn,iLEn);  
andGate ct1LE(t1LE,t1,iLEn);  
andGate ct1LEn(t1LEn,t1,iLEnn);
```

```
orGate cd1(d1,t0,t1LE);  
orGate cd2(d2,t2,t1LEn);
```

```
assign iClear = t0;
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
assign sumClear = t0;  
  
assign iInc = t1LE;  
assign sumAdd = t1LE;  
endmodule
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2


RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

$\sum_{i=0}^n i$ Circuit

 

RTL

©C.M.

$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
 Method 1

Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

Listing 5: sum.v

```
'timescale 1ns/1ns

module sum #(parameter W=1) (
    output [W-1:0] out,
    input  [W-1:0] n,
    input  reset,
    input  clk
);

    wire sumClear, sumAdd, iClear, iInc;
    wire iLEn;

    sumCTL    ctl(iClear, iInc, sumClear, sumAdd,
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
        iLEn,reset,clk);  
sumDP #(W) dp(out,iLEn,iClear,iInc,  
        sumClear,sumAdd,n,  
        clk);  
  
endmodule
```

$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1

Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

Listing 6: sum_tb.v

```
'timescale 1ns/1ns

module sum_tb;
    parameter W = 24;
    parameter N = 1000;

    clock #(200) cclk(clk);

    logic reset;
    wire [W-1:0] value;
    wire iLTn;

    sum #(W) sum(value,W'(N),reset,clk);
```

 $\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1

Method 2

RTL examples

 $\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

```
initial begin
    $dumpfile("sum.vcd");
    $dumpvars;

    reset=1;
    #300ns;
    reset=0;

    #1000000ns;

    $display(value);
    $finish();
end
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

$\sum_{i=0}^n i$ Testbench III

```
endmodule;
```

RTL

©C.M.

$\sum_{i=0}^n i$ comb.

$\sum_{i=0}^n i$ program

Method 1

Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

$$\sum_{i=0}^n i \text{ comb.}$$

$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

Method 2: Control controls the States

$\sum_{i=0}^n i$ Data Path (What **can** be done)

RTL

©C.M.

$$\sum_{i=0}^n i \text{ comb.}$$

$$\sum_{i=0}^n \text{Method 1}$$


Method 2

RTL examples

$$\sum_{i=0}^n i \cdot \text{rtl}$$

InvokeSum

Fibonacci

 

Listing 7: demo/03_sum/sumDP.v

```
'timescale 1ns/1ns

module sumDP #(parameter W=1) (
    output [W-1:0] out,
    output iLEn,
    input  t2,
    input  t1,
    input  t0,
    input  [W-1:0] n,
    input  clk
);

    wire [W-1:0] sumOut;
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
wire [W-1:0] sumPi;  
register #(W) sum(sumOut, sumPi, 1'b0,  
                 1'b0, 1'b0,  
                 1'b0, 1'b0,  
                 tmp, t0,  
                 clk);  
  
assign out = sumOut;  
  
wire [W-1:0] iOut;  
register #(W) i(iOut, W'(0), 1'b0,  
               1'b0, 1'b0,  
               1'b0, tmp,  
               t0, 1'b0,  
               clk);
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
binaryAdder #(W) ba(, ,sumPi,sumOut,  
                    iOut,1'b0);
```

```
comparator #(W) com(lt,eq,,iOut,n);  
orGate o(iLEn,eq,lt);
```

```
wire tmp;  
andGate incAdd(tmp,t1,iLEn);  
assign iInc = tmp;  
assign sumAdd = tmp;  
endmodule
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

$\sum_{i=0}^n i$ State Diagram

RTL

©C.M.

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1


Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

 

This is a **Moore** machine

Control (circuit)

RTL

©C.M.

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1


Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

 

Listing 8: demo/03_sum/ctl.v

```
'timescale 1ns/1ns

module sumCTL (
    output t2,
    output t1,
    output t0,
    input  iLEn,
    input  reset,
    input  clk
);

    wire d0,d1,d2;
    dffi dff0(t0,,d0,reset,1'b0,clk);
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
dff1 dff1(t1,,d1,1'b0,reset,clk);  
dff1 dff2(t2,,d2,1'b0,reset,clk);
```

```
assign d0=0;
```

```
wire iLEnn,t1LE,t1LEn;  
notGate ciLEnn(iLEnn,iLEn);  
andGate ct1LE(t1LE,t1,iLEn);  
andGate ct1LEn(t1LEn,t1,iLEnn);
```

```
orGate cd1(d1,t0,t1LE);  
orGate cd2(d2,t2,t1LEn);
```

```
endmodule
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$


InvokeSum

Fibonacci

$\sum_{i=0}^n i$ Circuit

RTL

©C.M.

 

$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1

Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

Listing 9: sum.v

```
'timescale 1ns/1ns

module sum #(parameter W=1) (
    output [W-1:0] out,
    input  [W-1:0] n,
    input  reset,
    input  clk
);

    wire iLEn;
    wire t2,t1,t0;

    sumCTL    ctl(t2,t1,t0,iLEn,reset,clk);
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
sumDP #(W) dp(out,iLEn,t2,t1,t0,n,clk);  
endmodule
```

$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1

Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

Listing 10: sum_tb.v

```
'timescale 1ns/1ns

module sum_tb;
    parameter W = 24;
    parameter N = 1000;

    clock #(200) cclk(clk);

    logic reset;
    wire [W-1:0] value;
    wire iLTn;

    sum #(W) sum(value,W'(N),reset,clk);
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
initial begin
    $dumpfile("sum.vcd");
    $dumpvars;

    reset=1;
    #300ns;
    reset=0;

    #1000000ns;

    $display(value);
    $finish();
end
endmodule;
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

$\sum_{i=0}^n i$ Testbench III

RTL

©C.M.

$\sum_{i=0}^n i$ comb.

$\sum_{i=0}^n i$ program
Method 1

Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

$$\sum_{i=0}^n i \text{ comb.}$$

$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

A Higher Level Notation

- Up until now we used Verilog at the Gate Level
- There are higher levels of description, e.g., RTL
- Verilog can be used also for RTL
- However, it is too abstract for the course needs
- So we will use an easy variation

Several examples will do

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

Example 1

RTL

©C.M.

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$


InvokeSum

Fibonacci

rtl

P: $A \leftarrow 0$

Drawing

 

Verilog

```
register #(N) A(,,1'b0,  
                1'b0,1'b0,  
                1'b0,1'b0,  
                1'b0,P,);
```

Example 2

RTL

©C.M.

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$


InvokeSum

Fibonacci

rtl

```
Q: A ← A + 1
```

Drawing

 

Verilog

```
register #(N) A(,,1'b0,  
                1'b0,1'b0,  
                1'b0,Q,  
                1'b0,1'b0,);
```

Example 3

RTL

©C.M.

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$


InvokeSum

Fibonacci

rtl

```
R: A ← A - 1
```

Drawing

 

Verilog

```
register #(N) A(,{N{1'b0}},1'b0 ,  
                1'b0 ,1'b0 ,  
                R,1'b0 ,  
                1'b0 ,1'b0 ,);
```

Example 4

RTL

©C.M.

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$


InvokeSum

Fibonacci

rtl

```
S: A ← A << 1
```

Drawing

 

Verilog

```
register #(N) A(,N'(0),1'b0,
                1'b0,S,
                1'b0,1'b0,
                1'b0,1'b0,);
```

Example 5

RTL

©C.M.

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$


InvokeSum

Fibonacci

rtl

```
T: A ← A >> 1
```

Drawing

 

Verilog

```
register #(N) A(,{N{1'b0}},1'b0,  
               T,1'b0,  
               1'b0,1'b0,  
               1'b0,1'b0,);
```

Example 6

RTL

©C.M.

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$


InvokeSum

Fibonacci

rtl

```
P: A ← 0
Q: A ← A + 1
R: A ← A - 1
S: A ← A << 1
T: A ← A >> 1
```

Drawing

 

Verilog

```
register #(N) A(,N'(0),1'b0,
                T,S,
                R,Q,
                1'b0,P,);
```

Example 7

RTL

©C.M.

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$


InvokeSum

Fibonacci

rtl

P: $A \leftarrow 5$

Drawing

 

Verilog

```
register #(N) A(,N'(5),1'b0,
                1'b0,1'b0,
                1'b0,1'b0,
                P,1'b0,);
```

Example 8 rtl, drawing

RTL

©C.M.

$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1
Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum


Fibonacci

rtl

P: A $\leftarrow$ 5

Q: A $\leftarrow$ 7

Drawing

 

Example 8 verilog

RTL

©C.M.

Verilog

```
assign options[0] = N'(d7);
assign options[1] = N'(d5);
muxMulti #(1,N) m(d,options,P);
orGate o(PoQ,P,Q);
register #(N) A(,d,1'b0,
                1'b0,1'b0,
                1'b0,1'b0,
                PoQ,1'b0,);
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

Example 9 rtl, drawing

RTL

©C.M.

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$


InvokeSum

Fibonacci

rtl

R: $A \leftarrow B$

Drawing

 

Example 9 verilog

RTL

©C.M.

Verilog

```
register #(N) A(,d,1'b0,
                1'b0,1'b0,
                1'b0,1'b0,
                R,1'b0,);
register #(N) B(d,,1'b0,
                1'b0,1'b0,
                1'b0,1'b0,
                1'b0,1'b0,);
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

Example 10 rtl, drawing

RTL

©C.M.

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

rtl


R: $A \leftarrow B, B \leftarrow A$

rtl

R: $A \leftarrow B$

R: $B \leftarrow A$

Drawing

 

Example 10 verilog

Verilog

```
register #(N) A(e,d,1'b0,
                1'b0,1'b0,
                1'b0,1'b0,
                R,1'b0,);

register #(N) B(d,e,1'b0,
                1'b0,1'b0,
                1'b0,1'b0,
                R,1'b0,);
```

RTL

©C.M.

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

When	What
reset :	$T_0 \leftarrow 1, T_1 \leftarrow 0, T_2 \leftarrow 0$
$T_0 :$	$\text{sum} \leftarrow 0, \text{seq} \leftarrow 1$
$T_0 :$	$i \leftarrow 0$
$T_1(i \leq n) :$	$i++ , \text{sum} \leftarrow \text{sum} + i, \text{seq} \leftarrow 1$
$T_1(i > n) :$	$\text{seq} \leftarrow 2$
$T_2 :$	$\text{seq} \leftarrow 2$

When	What
$T_2 :$	$\text{seq} \leftarrow 2$
$T_1(i \leq n) :$	$i++ , \text{sum} \leftarrow \text{sum} + i, \text{seq} \leftarrow 1$
$T_0 :$	$\text{sum} \leftarrow 0, \text{seq} \leftarrow 1$
$T_1(i > n) :$	$\text{seq} \leftarrow 2$
$T_0 :$	$i \leftarrow 0$
reset :	$T_0 \leftarrow 1, T_1 \leftarrow 0, T_2 \leftarrow 0$

So?

- We need to count cycles?
- How else the initiator knows when the sum is correct?
- A protocol is called for

RTL

©C.M.

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

(Carmi) Lecture 22 reached here

```
reset :      seq  $\leftarrow$  0
T0 :      sum  $\leftarrow$  0, i  $\leftarrow$  0, done  $\leftarrow$  0
T0 $\overline{\text{go}}$  :  seq  $\leftarrow$  0
T0go :     seq  $\leftarrow$  1
T1(i  $\leq$  n) : i ++, sum  $\leftarrow$  sum + i, seq  $\leftarrow$  1
T1(i > n) : done  $\leftarrow$  1, seq  $\leftarrow$  2
T2go :     seq  $\leftarrow$  2
T2 $\overline{\text{go}}$  :   done  $\leftarrow$  0, seq  $\leftarrow$  0
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

$\sum_{i=0}^n i$ State Diagram

RTL

©C.M.


$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1
Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

 

This is a **Moore** machine

- Method 1 data path is used
- Another method is used for the control: Sequence

Listing 11: demo/04_sum/sumCTL.v

```
'timescale 1ns/1ns

module sumCTL (
    output done,
    output iClear,
    output iInc,
    output sumClear,
    output sumAdd,
    input  iLEn,
    input  go,
    input  reset,
    input  clk
);
```

$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1
Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

```
wire [1:0]seqReg,seqIn;
wire seqUp,seqLoad,seqReset;
register #(2) seq(seqReg,seqIn,1'b0,
                1'b0,1'b0,
                1'b0,seqUp,
                seqLoad,seqReset,
                clk);

assign seqLoad=0;
or3Gate cseqReset(seqReset,reset,t0gon,t2gon);
orGate cseqUp(seqUp,t0go,t1GT);

wire [3:0]t;
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$
Method 1
Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

$\sum_{i=0}^n i$ Control III

RTL

©C.M.

```
decoder #(2) timing(t,seqReg);

wire gon;
notGate cgon(gon,go);

wire t0go,t0gon;
andGate ct0go(t0go,t[0],go);
andGate ct0gon(t0gon,t[0],gon);

wire t2go,t2gon;
andGate ct2go(t2go,t[2],go);
andGate ct2gon(t2gon,t[2],gon);

wire iGTn,t1LE,t1GT;
notGate ciLEnn(iGTn,iLEn);
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
andGate ct1LE(t1LE,t[1],iLEn);  
andGate ct1LEn(t1GT,t[1],iGTn);
```

```
assign iClear = t[0];  
assign sumClear = t[0];  
orGate cdone(done,t1GT,t2go);
```

```
assign iInc = t1LE;  
assign sumAdd = t1LE;  
endmodule
```

$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1
Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

Listing 12: sum.v

```
'timescale 1ns/1ns

module sum #(parameter W=1) (
    output done,
    output [W-1:0] out,
    input [W-1:0] n,
    input go,
    input reset,
    input clk
);

    wire sumClear, sumAdd, iClear, iInc;
    wire iLEn;
```

$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1
Method 2

RTL examples

 $\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

```
sumCTL    ctl(done,iClear,iInc,sumClear,sumAdd,
            iLEn,go,reset,clk);
sumDP    #(W) dp(out,iLEn,iClear,iInc,
               sumClear,sumAdd,n,
               clk);

endmodule
```

$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1
Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

Listing 13: sum_tb.v

```
'timescale 1ns/1ns

module sum_tb;
    parameter W = 24;
    parameter N = 1000;

    clock #(200) cclk(clk);

    logic reset,go;
    wire [W-1:0]value;

    sum #(W) sum(done,value,W'(N),go,reset,clk);
```

$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1
Method 2

RTL examples

 $\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

```
initial begin
    $dumpfile("sum.vcd");
    $dumpvars;

    reset=1;
    #150ns;
    reset=0;
    go=1;

    #10000000ns;

    $display(value);
    $finish();
end
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

$\sum_{i=0}^n i$ Testbench III

RTL

©C.M.

```
always @(posedge clk) begin
    if (done == 1)
        go = 0;
end

endmodule;
```

$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1
Method 2

RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

$$\sum_{i=0}^n i \text{ comb.}$$

$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

Invoking sum

Invoking sum rtl

RTL

©C.M.

```
reset :      seq ← 0
T0 :      sumMux ← 0
T1 :      sumGo ← 1
T2sumDone : seq ← 2
T3 :      sumGo ← 0, sumMux ← 1
T4 :      sumGo ← 1
T5sumDone : seq ← 5
T6 :      sumGo ← 0, sumMux ← 2
T7 :      sumGo ← 1
T8sumDone : seq ← 8
T9 :      sumGo ← 0, seq ← 9
```

- Default behavior of seq: seq ++
- Output hold until explicit change

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2


RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

Invoke State Diagram (not really needed)

 

RTL

©C.M.

$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1
Method 2



RTL examples

$\sum_{i=0}^n i$ rtl

InvokeSum

Fibonacci

InvokeSum Outputs (not really needed)

  

RTL

©C.M.

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

Listing 14: invokeSumDP.v

```
'timescale 1ns/1ns

module invokeSumDP #(parameter W=1) (
    output sumDone,
    input  [1:0] sumMux,
    input  sumGo,
    input  reset,
    input  clk
);

    wire [W-1:0] options[4];
    assign options[0] = 10;
    assign options[1] = 20;
```

$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
 Method 1
 Method 2

RTL examples

$\sum_{i=0}^n i$ rtl
 InvokeSum

Fibonacci

```
assign options[2] = 30;
assign options[3] = 40;

wire [W-1:0]n;
muxMulti #(2,W) mux(n,options,sumMux);

wire [W-1:0] sumAnswer;
sum #(W) sum(sumDone,sumAnswer,n,sumGo,
             reset,clk);

endmodule
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

Listing 15: demo/05_invokeSum/invokeSumCTL.v

```
'timescale 1ns/1ns

module invokeSumCTL #(parameter W=1) (
    output [1:0] sumMux,
    output sumGo,
    input  sumDone,
    input  reset,
    input  clk
);
    wire [3:0] seqReg;
    wire seqUp;
    register #(4) seq(seqReg,,
                      1'b0,1'b0,
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
1'b0, seqUp,
1'b0, reset, clk);

wire sumNDone;
notGate csumNDone(sumNDone, sumDone);
wire t2sumNDone, t5sumNDone, t8sumNDone;
andGate ct2sumNDone(t2sumNDone, t[2],
                    sumNDone);
andGate ct5sumNDone(t5sumNDone, t[5],
                    sumNDone);
andGate ct8sumNDone(t8sumNDone, t[8],
                    sumNDone);
nor4Gate cseqNUp(seqUp, t2sumNDone,
                 t5sumNDone, t8sumNDone, t[9]);
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
wire [15:0]t;
decoder #(4) timing(t,seqReg);

wire sumGo;
nor4Gate csumGo(sumGo,t[0],t[3],t[6],
                t[9]);

wire sumMuxUp;
register #(2) csumMux(sumMux,,,
                    1'b0,1'b0,
                    1'b0,sumMuxUp,
                    1'b0,t[0],clk);
    orGate csumMuxUp(sumMuxUp,t[3],t[6]);
endmodule
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

$$\sum_{i=0}^n i \text{ comb.}$$

$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

Listing 16: invokeSum.v

```
'timescale 1ns/1ns

module invokeSum #(parameter W=1) (
    input  reset,
    input  clk
);

    wire [1:0] sumMux;

    invokeSumCTL #(W) invokeSumCTL(
        sumMux,
        sumGo,
        sumDone,
        reset,
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
        clk);  
  
    invokeSumDP #(W) invokeSumDP (  
        sumDone ,  
        sumMux ,  
        sumGo ,  
        reset ,  
        clk);  
  
endmodule
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

Listing 17: invokeSum_tb.v

```
'timescale 1ns/1ns

module invokeSum_tb;
    parameter W = 24;

    logic reset;
    wire clk;

    clock #(400) cclk(clk);

    invokeSum #(W) invokeSum(reset,clk);

    initial begin
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
$dumpfile("invokeSum.vcd");  
$dumpvars;
```

```
reset=1;  
#250ns;  
reset=0;
```

```
#1000000ns;
```

```
$finish();
```

```
end
```

```
endmodule;
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

$$\sum_{i=0}^n i \text{ comb.}$$

$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

Fibbonaci Sequence

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
reset :      seq  $\leftarrow$  0
T0 :      done  $\leftarrow$  0, b  $\leftarrow$  0, c  $\leftarrow$  1, i  $\leftarrow$  0
T1 $\overline{\text{go}}$  :  seq  $\leftarrow$  1
T1go :     seq  $\leftarrow$  2
T2(i < n) :  i ++, b  $\leftarrow$  c, c  $\leftarrow$  b + c, seq  $\leftarrow$  2
T2(i  $\geq$  n) : done  $\leftarrow$  1, seq  $\leftarrow$  3
T3go :     seq  $\leftarrow$  3
T3 $\overline{\text{go}}$  :   b  $\leftarrow$  0, c  $\leftarrow$  1, i  $\leftarrow$  0, done  $\leftarrow$  0, seq  $\leftarrow$  1
```

- done - wire
- b,c,i: Registers

Listing 18: demo/06_fibo/fiboDP.v

```
'timescale 1ns/1ns

module fiboDP #(parameter W=1) (
    output [W-1:0] out ,
    output iLTn ,
    input [W-1:0] n ,
    input iUp ,
    input iReset ,
    input cMux ,
    input cLoad ,
    input bLoad ,
    input bReset ,
    input clk
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
);  
wire [W-1:0] bReg;  
register #(W) b(bReg, regC, 1'b0,  
               1'b0, 1'b0,  
               1'b0, 1'b0,  
               bLoad, bReset,  
               clk);  
  
wire [W-1:0] optC [2], inC;  
assign optC[0] = W'(1);  
assign optC[1] = sumBC;  
muxMulti #(1,W) muxC(inC, optC, cMux);  
  
wire [W-1:0] regC;  
register #(W) c(regC, inC, 1'b0,
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
1'b0,1'b0,
1'b0,1'b0,
cLoad,1'b0,
clk);

wire [W-1:0] iReg;
register #(W) i(iReg,W'(0),1'b0,
               1'b0,1'b0,
               1'b0,iUp,
               1'b0,iReset,
               clk);

wire [W-1:0] sumBC;
binaryAdder #(W) ba(,,sumBC,bReg,
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
regC,1'b0);  
  
comparator #(W) com(iLTn,,,iReg,n);  
  
assign out=bReg;  
  
endmodule
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

Listing 19: demo/06_fibo/fiboCTL.v

```
'timescale 1ns/1ns

module fiboCTL (
    output    iUp,
    output    iReset,
    output    cMux,
    output    cLoad,
    output    bLoad,
    output    bReset,
    output    done,
    input     iLTn,
    input     go,
    input     reset,
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
input  clk
);

wire [1:0]seqReg, seqIn;
wire seqUp, seqLoad;
register #(2) seq(seqReg,2'(1),1'b0,
                  1'b0,1'b0,
                  1'b0,seqUp,
                  seqLoad,reset,
                  clk);

comparator #(2) cmp(,eq,,seqReg,2'(3));
andGate cseqLoad(seqLoad,eq,t3gon);

or3Gate cseqUp(seqUp,t[0],t1go,t2LTn);
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
wire [3:0]t;  
decoder #(2) timing(t,seqReg);  
  
andGate cdone(done,t[2],iLTnn);  
  
orGate cbRreset(bReset,t[0],t3gon);  
andGate cbLoad(bLoad,t[2],iLTn);  
  
or3Gate ccLoad(cLoad,t[0],t2LT,t3gon);  
assign cMux = t2LT;  
  
orGate ciReset(iReset,t[0],t3gon);  
  
andGate ciUp(iUp,t[2],iLTn);
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
wire gon;  
notGate cgon(gon,go);  
  
wire t1gon,t3gon;  
andGate ct1gon(t1gon,t[1],gon);  
  
wire t1go;  
andGate c1go(t1go,t[1],go);  
  
wire iLTnn,t1LT,t1LTn;  
notGate ciLTnn(iLTnn,iLTn);  
andGate ct1LT(t2LT,t[2],iLTn);  
andGate ct1LTn(t2LTn,t[2],iLTnn);
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
wire t3go;  
andGate ct3go(t3go,t[3],go);  
andGate ct3gon(t3gon,t[3],gon);
```

```
endmodule
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

Listing 20: demo/06_fibo/fibo.v

```
'timescale 1ns/1ns

module fibo #(parameter W=1) (
    output [W-1:0] out,
    output done,
    input [W-1:0] n,
    input go,
    input reset,
    input clk
);

    wire iLTn;
    wire t2,t1,t0;
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
fibonacci ctl(iUp,iReset,cMux,cLoad,bUp,bReset,
             done,iLTn,go,reset,clk);
fibonacci #(W) dp(out,iLTn,n,
                 iUp,iReset,cMux,cLoad,bUp,bReset,
                 clk);

endmodule
```

$\sum_{i=0}^n i$ comb.
 $\sum_{i=0}^n i$ program
Method 1
Method 2

RTL examples

$\sum_{i=0}^n i$ rtl
InvokeSum

Fibonacci

Listing 21: demo/06_fibo/fibo_tb.v

```
'timescale 1ns/1ns

module fibo_tb;
    parameter W = 24;
    parameter N = 10;

    clock #(200) cclk(clk);

    logic reset,go;
    wire [W-1:0]value;
    wire iLTn;

    wire done;
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
fibo #(W) fibo(value,done,W'(N),go,reset,clk);

initial begin
    $dumpfile("fibo.vcd");
    $dumpvars;

    reset=1;
    go = 0;
    #150ns;
    reset=0;
    go = 1;

    #1000000ns;
```

$$\sum_{i=0}^n i \text{ comb.}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci

```
                                $finish();  
end  
  
always @(posedge clk) begin  
    if (done == 1)  
        go = 0;  
end  
  
endmodule;
```

$$\sum_{i=0}^n i \text{ comb.}$$
$$\sum_{i=0}^n i \text{ program}$$

Method 1

Method 2

RTL examples

$$\sum_{i=0}^n i \text{ rtl}$$

InvokeSum

Fibonacci