

The Carmion

© Carmi Merimovich

February 3, 2025

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

 $r[n]$


ALU

 $r[n]$ $\sum_{i=0}^n i \text{ program}$

The Carmion-1

A subset of RISC-V64 was planned, but this will do, I guess

Classical Computer System

 

- This is how computer systems **used** to look
- **We** can still think they look like this

Carmion-1

```
rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
r[n]
ALU
r[n]

$$\sum_{i=0}^n i \text{ program}$$

```

Processor loop

carmion

©C.M.

The **processor** is a **program** in an infinite loop

1. Instruction fetch
2. Instruction decode
3. Instruction execute

The processor consumes **machine instructions**

Carmion-1

rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
r[n]
ALU
r[n]
 $\sum_{i=0}^n i \text{ program}$

Carmion's Main Characteristics

carmion

©C.M.

- Von Neumann architecture
- Word size is 32 bits
- Main memory size is 1024 words
- The memory is word addressable
- Two registers are available for programming

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

$\sum_{i=0}^n i \text{ program}$

Internal Registers

Name	Full name	Width
seq	Sequencer	6
pc	Program Counter	10
ir	Instruction Register	32
ar	Address Register	10
dr	Data Register	32
haltReg	Halt Register	1
ilglReg	Illegal Instruction Register	1

Programmer Accessible

Name	Full name	Width
r0		32
r1		32

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]


ALU

r[n]

 $\sum_{i=0}^n i \text{ program}$

Memory (RAM/ROM)

 - Memory access nowadays is not exactly trivial
- We will use a simplified memory model
 - ▶ Memory responds fast
 - ▶ Only word access



Recall: Von Neumann architecture

- Machine instructions are in memory
- The processor needs to bring the instructions in

Carmion-1

```
rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
r[n]
ALU
r[n]

$$\sum_{i=0}^n i \text{ program}$$

```


Carmion's Instructions Format

carmion

©C.M.

Carmion-1

 rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
 $r[n]$
ALU
 $r[n]$
 $\sum_{i=0}^n i \text{ program}$



field	meaning
-------	---------

Operation Code: Identifies the instruction

n : The number of the 'left' register

m : The number of the 'right' register

Address : Memory address of operand

Carmion's Machine Instructions

carmion

©C.M.

halt

00000000000000000001	xx	xxxxxxxxxxxx
----------------------	----	--------------

lw rn,addr

00000000000000000010	xn	addr
----------------------	----	------

sw rn,addr

00000000000000000011	xn	addr
----------------------	----	------

add rn,rm

00000000000000000100	mn	xxxxxxxxxxxx
----------------------	----	--------------

bgeu rn,rm

00000000000000000101	mn	distance
----------------------	----	----------

Carmion-1

rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
r[n]
ALU
r[n]
 $\sum_{i=0}^n i \text{ program}$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU


r[n]

 $\sum_{i=0}^n i \text{ program}$

The Processor RTL

State Machine Conventions

 - Each state has a unique number
- The active state number is in the register seq
- No explicit mention of seq on an edge means $\text{seq}++$
- For simplification the value of seq goes into a decoder
- (A peculiar 1-hot method, I guess)



Carmion-1

rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
r[n]
ALU
r[n]
 $\sum_{i=0}^n i \text{ program}$

Processor initialization

```
reset :  seq  $\leftarrow$  0, r0  $\leftarrow$  0, r1  $\leftarrow$  0  
 $T_0$  :    pc  $\leftarrow$  512,  
 $T_0$  :    haltReg  $\leftarrow$  0, ilglReg  $\leftarrow$  0  
 $T_0$  :    ir  $\leftarrow$  0
```

The reset on $r[0]$ and $r[1]$ is a kludge for the alu flags

Carmion-1

```
rtl  
seq  
pc  
haltR  
ilglReg  
ar  
dr  
Memory  
ir  
r[n]  
ALU  
r[n]  
 $\sum_{i=0}^n$  i program
```

$$T_1 : \text{ar} \leftarrow \text{pc}, \text{pc} \leftarrow \text{pc} + 1$$

$$T_2 : \text{dr} \leftarrow m[\text{ar}]$$

$$T_3 : \text{ir} \leftarrow \text{dr}$$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

 $r[n]$

ALU

 $r[n]$

$$\sum_{i=0}^n i \text{ program}$$

$T_4(\text{op} \neq 0)(\text{op} < 6) :$ $\text{op} = \text{ir}[31 : 12]$
 $T_5 :$ $\text{seq} \leftarrow \text{op} \ll 3$
 $T_6 :$ $\text{haltReg} \leftarrow \text{haltReg} + 1$
 $T_7 :$ $\text{ilglReg} \leftarrow \text{ilglReg} + 1$
 $T_7 :$ $\text{seq} \leftarrow 7$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

 $r[n]$

ALU

 $r[n]$ $\sum_{i=0}^n i \text{ program}$

halt (**halt**)

Processor stops

$$T_8 : \text{haltReg} \leftarrow \text{haltReg} + 1$$

$$T_9 : \text{seq} \leftarrow 9$$

Carmion-1

rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
r[n]
ALU
r[n]
 $\sum_{i=0}^n i \text{ program}$

lw rn,addr (**L**oad **w**ord)

carmion

©C.M.

$$r[n] \leftarrow [\text{addr}]$$
$$T_{16} : \text{ar} \leftarrow \text{ir}[9 : 0]$$
$$T_{17} : \text{dr} \leftarrow m[\text{ar}]$$
$$T_{18} : r[\text{ir}[10]] \leftarrow \text{dr}, \text{seq} \leftarrow 0$$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

$r[n]$

ALU

$r[n]$

$\sum_{i=0}^n i$ program

sw rn,addr (store word)

carmion

©C.M.

$[addr] \leftarrow r[n]$

$T_{24} : \text{dr} \leftarrow r[\text{ir}[10]], \text{ar} \leftarrow \text{ir}[9 : 0]$

$T_{25} : m[\text{ar}] \leftarrow \text{dr}, \text{seq} \leftarrow 0$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

$r[n]$

ALU

$r[n]$

$\sum_{i=0}^n i \text{ program}$

add rn,rm (**add**)

$$r[n] \leftarrow r[n] + r[m]$$

$$T_{32} : r[\text{ir}[10]] \leftarrow r[\text{ir}[10]] + r[\text{ir}[11]], \text{seq} \leftarrow 0$$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

 $r[n]$

ALU

 $r[n]$ $\sum_{i=0}^n i \text{ program}$

bgeu rn,rm,off (**b**branch **g**reater **e**qual) **u**nsigned

carmion

©C.M.

If $r[n] \geq_u r[m]$ then $pc \leftarrow pc + ir[9 : 0]$

$T_{40}(r[ir[10]] \geq_u r[ir[11]]) : pc \leftarrow pc + ir[9 : 0]$
 $T_{40} : seq \leftarrow 0$

Carmion-1

rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
 $r[n]$
ALU
 $r[n]$
 $\sum_{i=0}^n i$ program

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

$$\sum_{i=0}^n i \text{ program}$$

'Building' the Hardware

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

$$\sum_{i=0}^n i \text{ program}$$

The seq register

seq to the left of $\leftarrow$ (RTL)

reset : seq $\leftarrow$ 0
 $T_4(0 \neq \text{op} < 6)$: seq $\leftarrow$ op $\ll$ 3
 T_6 : seq $\leftarrow$ 6
 T_9 : seq $\leftarrow$ 9
 T_{18} : seq $\leftarrow$ 0
 T_{25} : seq $\leftarrow$ 0
 T_{32} : seq $\leftarrow$ 0
 T_{40} : seq $\leftarrow$ 0


Carmion-1

rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
r[n]
ALU
r[n]
 $\sum_{i=0}^n$ i program

seq to the left of $\leftarrow$ (data path)

carmion

©C.M.

 

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

$r[n]$

ALU

$r[n]$

$\sum_{i=0}^n i \text{ program}$

seq to the left of $\leftarrow$ (formulae)

seqClear = reset

$$t = T_{18} + T_{25} + T_{32} + T_{40}$$

$$\text{seqLoad} = T_4(\text{op} < 6)(\text{ir}[31] + \dots + \text{ir}[12]) + T_6 + T_9 + t$$

$$\text{seqLoadSel}_1 = T_6 + T_9$$

$$\text{seqLoadSel}_0 = T_4 + T_9$$

Carmion-1

rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
r[n]
ALU
r[n]
 $\sum_{i=0}^n$ i program


seq to the left of $\leftarrow$ (control)

carmion

©C.M.

Carmion-1

 rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
 $r[n]$
ALU
 $r[n]$
 $\sum_{i=0}^n i$ program



Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

$$\sum_{i=0}^n i \text{ program}$$

The pc register

pc to the left of $\leftarrow$ (RTL)

reset : $pc \leftarrow 512$
 T_1 : $pc \leftarrow pc + 1$
 $T_{40}(r[ir[10]] \geq_u r[ir[11]])$: $pc \leftarrow pc + ir[9 : 0]$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

 $r[n]$


ALU

 $r[n]$ $\sum_{i=0}^n i \text{ program}$

pc to the left of $\leftarrow$ (data path)

carmion

©C.M.

 

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

$r[n]$

ALU

$r[n]$

$\sum_{i=0}^n i$ program

pc to the left of $\leftarrow$ (formulae)

carmion

©C.M.

$$\text{pcLoad} = \text{reset} + T_{40}(r[\text{ir}[10]] \geq_u \text{ir}[11])$$

$$\text{pcLoadSel} = T_{40}$$

$$\text{pcUp} = T_1$$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

$\sum_{i=0}^n i$ program


pc to the left of $\leftarrow$ (control)

carmion

©C.M.

Carmion-1

 rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
 $r[n]$
ALU
 $r[n]$
 $\sum_{i=0}^n i$ program



Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

 $\sum_{i=0}^n i \text{ program}$

The haltReg register

haltReg to the left of $\leftarrow$ (RTL)

$T_0 : \text{haltReg} \leftarrow 0$

$T_5 : \text{haltReg} \leftarrow \text{haltReg} + 1$

$T_8 : \text{haltReg} \leftarrow \text{haltReg} + 1$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

 $r[n]$

ALU

 $r[n]$ $\sum_{i=0}^n i \text{ program}$

haltReg to the left of $\leftarrow$ (formulae)

$$\text{haltRegClear} = T_0$$

$$\text{haltRegUp} = T_5 + T_8$$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

$r[n]$

ALU


$r[n]$

$\sum_{i=0}^n i \text{ program}$

haltReg to the left of $\leftarrow$ (control)

carmion

©C.M.

 

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

$r[n]$

ALU

$r[n]$

$\sum_{i=0}^n i$ program

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

$$\sum_{i=0}^n i \text{ program}$$

The ilglReg register

ilglReg to the left of $\leftarrow$ (RTL)

carmion

©C.M.

$$T_0 : \text{ilglReg} \leftarrow 0$$

$$T_5 : \text{ilglReg} \leftarrow \text{ilglReg} + 1$$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

$\sum_{i=0}^n i$ program

ilglReg to the left of $\leftarrow$ (formulae)

carmion

©C.M.

$$\text{ilglRegClear} = T_0$$

$$\text{ilglRegUp} = T_5$$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

$r[n]$

ALU


$r[n]$

$\sum_{i=0}^n i \text{ program}$

ilglReg to the left of $\leftarrow$ (control)

carmion

©C.M.

 

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

$r[n]$

ALU

$r[n]$

$\sum_{i=0}^n i$ program

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

 $\sum_{i=0}^n i \text{ program}$

The ar register

ar to the left of $\leftarrow$ (RTL)

$$\begin{aligned}T_1 : \quad & \text{ar} \leftarrow \text{pc} \\T_{16} : \quad & \text{ar} \leftarrow \text{ir}[9 : 0] \\T_{24} : \quad & \text{ar} \leftarrow \text{ir}[9 : 0]\end{aligned}$$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

 $\sum_{i=0}^n i \text{ program}$

ar to the left of $\leftarrow$ (data path)

carmion

©C.M.

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory


ir

r[n]

ALU

r[n]

$\sum_{i=0}^n i \text{ program}$

 

ar to the left of $\leftarrow$ (formulae)

carmion

©C.M.

$$\text{arLoad} = T_1 + T_{16} + T_{24}$$

$$\text{arLoadSel} = T_0$$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

$r[n]$

ALU


$r[n]$

$\sum_{i=0}^n i \text{ program}$

ar to the left of $\leftarrow$ (circuit)

carmion

©C.M.

 

Carmion-1

rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
 $r[n]$
ALU
 $r[n]$
 $\sum_{i=0}^n i \text{ program}$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

 $\sum_{i=0}^n i \text{ program}$

The dr register

dr to the left of $\leftarrow$ (RTL)

$$\begin{aligned}T_2 : & \quad \text{dr} \leftarrow m[\text{ar}] \\T_{17} : & \quad \text{dr} \leftarrow m[\text{ar}] \\T_{24} : & \quad \text{dr} \leftarrow r[\text{ir}[10]]\end{aligned}$$

Carmion-1

rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
 $r[n]$
ALU
 $r[n]$
 $\sum_{i=0}^n i$ program


dr to the left of $\leftarrow$ (data)

carmion

©C.M.

Carmion-1

 rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
 $r[n]$
ALU
 $r[n]$
 $\sum_{i=0}^n i$ program



dr to the left of $\leftarrow$ (formulae)

carmion

©C.M.

$$\text{drLoad} = T_2 + T_{17} + T_{24}$$

$$\text{drLoadSel}_1 = T_{24}$$

$$\text{drLoadSel}_0 = \text{ir}[10]$$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

$r[n]$

ALU

$r[n]$

$\sum_{i=0}^n i \text{ program}$


dr to the left of $\leftarrow$ (control)

carmion

©C.M.

Carmion-1

 rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
 $r[n]$
ALU
 $r[n]$
 $\sum_{i=0}^n i$ program



Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

 $r[n]$

ALU

 $r[n]$ $\sum_{i=0}^n i \text{ program}$

Memory Access

Memory Access (RTL)

$$T_2 : \quad \text{dr} \leftarrow m[\text{ar}]$$

$$T_{17} : \quad \text{dr} \leftarrow m[\text{ar}]$$

$$T_{25} : \quad m[\text{ar}] \leftarrow \text{dr}$$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU


r[n]

 $\sum_{i=0}^n i \text{ program}$

Memory Access (data path)

carmion

©C.M.

 

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

$\sum_{i=0}^n i \text{ program}$

Memory access (formulae)

carmion

©C.M.

$$\text{memRead} = T_2 + T_{17}$$

$$\text{memWrite} = T_{25}$$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

$r[n]$

ALU


$r[n]$

$\sum_{i=0}^n i \text{ program}$

Memory Access (control)

carmion

©C.M.

 

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

$r[n]$

ALU

$r[n]$

$\sum_{i=0}^n i \text{ program}$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

 $\sum_{i=0}^n i \text{ program}$

The ir register

ir to the left of $\leftarrow$ (RTL)

carmion

©C.M.

$$T_3 : \text{ir} \leftarrow \text{dr}$$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

$r[n]$

ALU

$r[n]$

$\sum_{i=0}^n i \text{ program}$


ir to the left of $\leftarrow$ (control)

carmion

©C.M.

Carmion-1

 rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
 $r[n]$
ALU
 $r[n]$
 $\sum_{i=0}^n i \text{ program}$



ir to the left of $\leftarrow$ (formulae)

carmion

©C.M.

irClear = reset

irLoad = T_3

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

$r[n]$

ALU


$r[n]$

$\sum_{i=0}^n i$ program

ir to the left of $\leftarrow$ (control)

carmion

©C.M.

 

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

$r[n]$

ALU

$r[n]$

$\sum_{i=0}^n i \text{ program}$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

 $\sum_{i=0}^n i \text{ program}$

$r[n]$ to the left of $\leftarrow$

$r[n]$ to the left of $\leftarrow$ (RTL)

reset : $r[0] \leftarrow 0, r[1] \leftarrow 0$

T_{18} : $r[\text{ir}[10]] \leftarrow \text{dr}$

T_{32} : $r[\text{ir}[10]] \leftarrow r[\text{ir}[10]] + r[\text{ir}[11]]$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

 $r[n]$


ALU

 $r[n]$ $\sum_{i=0}^n i \text{ program}$

ALU (data path)

carmion

©C.M.

 

Carmion-1

rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
 $r[n]$
ALU
 $r[n]$
 $\sum_{i=0}^n i$ program


$r[n]$ to the left of $\leftarrow$ (data path)

carmion

©C.M.

Carmion-1

 rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
 $r[n]$
ALU
 $r[n]$
 $\sum_{i=0}^n i \text{ program}$



$r[n]$ to the left of $\leftarrow$ (formulae)

Carmion-1

rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
 $r[n]$
ALU
 $r[n]$
 $\sum_{i=0}^n$ i program

$$r0Reset = reset$$

$$r0Load = T_{18} \overline{ir[10]} + T_{32} \overline{ir[10]}$$

$$r1Reset = reset$$

$$r1Load = T_{18} ir[10] + T_{32} ir[10]$$

$$aluSel_0 = ir[10]$$


$$aluSel_1 = ir[11]$$

$$aluOp = T_{24}$$

ALU (control)

carmion

©C.M.

 

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

$\sum_{i=0}^n i \text{ program}$


$r[n]$ to the left of $\leftarrow$ (control)

carmion

©C.M.

Carmion-1

rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
 $r[n]$
ALU
 $r[n]$
 $\sum_{i=0}^n i$ program

 

Listing 1: demo/01_carmion1/dp.v

```
'timescale 1ns/1ns

module dp(
    output aluEq, aluGeu, aluGtu, aluLeu, aluLtui,
    output [9:0] arOut,
    output [31:0] drOut,
    output [31:0] irOut,
    input aluOp,
    input arLoad, arLoadSel,
    input [31:0] drInOpt,
    input drLoad,
    input [1:0] drLoadSel,
    input irClear, irLoad,
```

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

 $r[n]$

ALU

 $r[n]$
 $\sum_{i=0}^n i \text{ program}$

```
    input  pcLoad, pcLoadSel, pcUp,
    input  r0Load,
    input  r1Load,
    input  reset,
    input  clk

);

//
// pc
//
wire [9:0] pcOut, pcIn;
register #(10) pc(
    pcOut, pcIn, ,
    1'b0, 1'b0,
    1'b0,
    pcUp, pcLoad, 1'b0,
```

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

 $\sum_{i=0}^n i \text{ program}$

```

        clk
    );

    wire [9:0] pcOptions [2];
    wire [9:0] pcAdd;
    assign pcOptions [0] = 10'(512);
    assign pcOptions [1] = pcAdd;
    binaryAdder #(10) c_pcadd(, , pcAdd, pcOut, r[n], r[n]);
    muxMulti #(1, 10) cpcIn(pcIn, pcOptions, pcLoadSel, r[n]);

    //
    // ar
    //
    wire [9:0] arIn;
    register #(10) ar(

```

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

$$\sum_{i=0}^n r[i]$$

```

        arOut, arIn, ,
        1'b0, 1'b0,
        1'b0, 1'b0,
        arLoad, 1'b0,
        clk
    );
    wire [9:0] arOptions[2];
    assign arOptions[0] = irOut[9:0];
    assign arOptions[1] = pcOut;
    muxMulti #(1,10) c_arIn(arIn, arOptions, arLoad

//
// dr
//

```

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

$$\sum_{i=0}^n i \text{ program}$$

```
wire [31:0] drIn;
wire drLoad;
register #(32) dr(
    drOut, drIn, ,
    1'b0, 1'b0,
    1'b0, 1'b0,
    drLoad, 1'b0,
    clk
);
wire [31:0] drOptions[4];
assign drOptions[0] = drInOpt;
assign drOptions[1] = drInOpt;
assign drOptions[2] = r0Out;
assign drOptions[3] = r1Out;
muxMulti #(2,32) c_drIn(drIn, drOptions, drLoad
```

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

 $\sum_{i=0}^n i \text{ program}$

```
//  
// ir  
//  
register #(32) ir(  
    irOut,drOut,,  
    1'b0, 1'b0,  
    1'b0, 1'b0,  
    irLoad, irClear,  
    clk  
);  
  
//  
// alu
```

Carmion-1

rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
r[n]
ALU
r[n]
 $\sum_{i=0}^n i \text{ program}$

```
//  
  
wire [31:0] r10Out,r00Out;  
register #(32) r0(  
    r00Out,aluOut,,  
    1'b0, 1'b0,  
    1'b0, 1'b0,  
    r0Load, reset,  
    clk  
);  
register #(32) r1(  
    r10Out,aluOut,,  
    1'b0, 1'b0,  
    1'b0, 1'b0,  
    r1Load, reset,
```

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

 $\sum_{i=0}^n i \text{ program}$


```

        clk
    );

    wire [31:0] aluOut;
    wire aluSel0, aluSel1;
    wire aluLtu, aluEq, aluGtu, aluLeu, aluGeu;
    alu alu(aluEq, aluGeu, aluGtu, aluLeu, aluLtu,
            aluOut,
            r0Out, r1Out, drOut,
            irOut[10], irOut[11], aluOp);

endmodule

```

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

r[n]

 $\sum_{i=0}^n$

i program

Listing 2: demo/01_carmion1/alu.v

```
'timescale 1ns/1ns

//
// op:
//    2 - dr
//
module alu(
    output eq,geu,gtu,leu,ltu,
    output [31:0] out,
    input  [31:0] in0,in1,in2,
    input  sel0, sel1,
    input  op
);
```

Carmion-1

rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
r[n]
ALU
r[n]
 $\sum_{i=0}^n i \text{ program}$

```
wire [31:0] opt0[2], opt1[2];
wire [31:0] arg0, arg1;
assign opt0[0] = in0;
assign opt0[1] = in1;
assign opt1[0] = in0;
assign opt1[1] = in1;
muxMulti #(1,32) c_arg0(arg0,opt0,sel0);
muxMulti #(1,32) c_arg1(arg1,opt1,sel1);

wire [31:0] sum;
binaryAdder #(32) ba(, ,sum,arg0,arg1,1'b0);

wire [31:0] options[2];
```

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

 $\sum_{i=0}^n i \text{ program}$

carmion1 alu (datapath) III

```
assign options[0] = sum;
assign options[1] = in2;

muxMulti #(1,32) c_out(out,options,op);

comparator #(32) cond(ltu,eq,gtu,arg0,arg1);

orGate c_aluLequ(leu,ltu,eq);
orGate c_aluGequ(geu,gtu,eq);

endmodule
```

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ic

ALU

r[n]

 $\sum_{i=0}^n i \text{ program}$

Listing 3: demo/01_carmion1/ctl.v

```
'timescale 1ns/1ns

parameter opCodeHalt = 1;
parameter opCodeLw   = 2;
parameter opCodeSw   = 3;
parameter opCodeAdd  = 4;
parameter opCodeBgeu = 5;

parameter T_SHIFT = 3;
parameter T_OP    = (2**T_SHIFT);

parameter T_FETCH = 1;
parameter T_SWITCH = 4;
```

Carmion-1

rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
r[n]
ALU
r[n]
 $\sum_{i=0}^n i \text{ program}$

```

parameter T_ilgl = 5;
parameter T_ilglDone = T_ilgl + 1;

parameter T_halt = opCodeHalt * T_OP;
parameter T_haltDone = T_halt + 1;

parameter T_lw      = opCodeLw * T_OP;
parameter T_lwDone  = T_lw + 2;

parameter T_sw      = opCodeSw * T_OP;
parameter T_swDone  = T_sw + 1;

parameter T_add      = opCodeAdd * T_OP;

```

Carmion-1

rtl
 seq
 pc
 haltR
 ilglReg
 ar
 dr
 Memory
 ir
 r[n]
 ALU
 r[n]
 $\sum_{i=0}^n i \text{ program}$

```

parameter T_addDone = T_add;

parameter T_bgeu      = opCodeBgeu * T_OP;
parameter T_bgeuDone = T_bgeu;

module ctl(
    output aluOp,
    output arLoad, arLoadSel,
    output drLoad,
    output [1:0]drLoadSel,
    output flagHalt, flagIlgl,
    output irClear, irLoad,
    output memRead, memWrite,
    output pcLoad, pcLoadSel, pcUp,
    output r0Load,

```

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

$$\sum_{i=0}^n i \text{ program}$$

```

    output  r1Load,
    input   aluEq, aluGeu, aluGtu, aluLeu, aluLtu,
    input   [31:0]ir,
    input   reset,
    input   clk

);

//
// seq
//
wire [(T_SHIFT+3)-1:0] seqOut, seqIn;
wire seqClear, seqLoad, seqUp;
register #(T_SHIFT+3) seq(
    seqOut, seqIn, ,
    1'b0, 1'b0,
    1'b0,

```

Carmion-1

rtl
 pc
 haltR
 ilglReg
 ar
 dr
 Memory
 ir
 r[n]
 ALU
 r[n]
 $\sum_{i=0}^n$ i program


```

        seqUp, seqLoad, seqClear,
        clk
    );

    wire [2*(T_SHIFT+3)-1:0] t;
    decoder #(T_SHIFT+3) timing(t, seqOut);

    wire [1:0] seqLoadSel;
    wire [T_SHIFT+3-1:0] seqOptions[4];
    assign seqOptions[0] = T_FETCH;
    assign seqOptions[1] = {ir[14:12], {(T_SHIFT)'(0)}};
    assign seqOptions[2] = T_ilglDone;
    assign seqOptions[3] = T_haltDone;
    orGate c_seqLoadSel1(seqLoadSel[1], t[T_ilglDone], t[T_haltDone]);
    orGate c_seqLoadSel0(seqLoadSel[0], t[T_SWITCH], t[T_FETCH]);

```

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

$$\sum_{i=0}^n i \text{ program}$$

```

muxMulti #(2,T_SHIFT+3) cseqIn(seqIn,seqOptions

wire opLegal;
comparator #(20) c_opLegal(opLegal,,,ir[31:12],
andGate c_seqSwitch(seqSwitch,t[T_SWITCH],opLeg

wire [5:0]allDone;
assign allDone[0]=seqSwitch;
assign allDone[1]=t[T_haltDone];
assign allDone[2]=t[T_lwDone];
assign allDone[3]=t[T_swDone];
assign allDone[4]=t[T_addDone];
assign allDone[5]=t[T_bgeuDone];

orMulti #(6) c_seqLoad(seqLoad,allDone);

```

Carmion1

r[n]

seq

pc

haltR

ilgReg

alu

r[n]

memory

ir

r[n]

ALU

r[n]

$$\sum_{i=0}^n i \text{ program}$$

```

orGate  cseqClear(seqClear,reset,reset);

norGate  cseqUp(seqUp,seqLoad,seqClear);

//
// pc
//
andGate  c_condGeu(condGeu,t[T_bgeu],aluGeu);
orGate  c_pcLoad(pcLoad,t[0],condGeu);
assign  pcLoadSel = t[T_bgeu];
assign  pcUp=t[1];

```

Carmion-1

```

rtl
seq
pc
haltR
ilglReg
ar
dr
Memory
ir
r[n]
ALU
r[n]

$$\sum_{i=0}^n i \text{ program}$$


```

```
//  
// haltReg  
//  
wire haltOut, haltUp;  
register #(1) chaltReg(  
    haltOut, , ,  
    1'b0, 1'b0,  
    1'b0, haltUp,  
    1'b0, t[0],  
    clk  
);  
orGate chaltUp(haltUp, t[T_ilgl], t[T_halt]);  
assign flagHalt=haltOut;  
  
//
```

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

 $\sum_{i=0}^n i \text{ program}$

```
// ilglReg
//
wire ilglOut,ilglUp;
register #(1) cilglReg(
    ilglOut,,,
    1'b0, 1'b0,
    1'b0,
    ilglUp, 1'b0, t[0],
    clk

);
assign ilglUp = t[T_ilgl];
assign flagIlgl = ilglOut;

//
```

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

 $\sum_{i=0}^n i \text{ program}$

```

// ar
//
or3Gate carLoad(arLoad,t[1],t[T_lw],t[T_sw]);
assign arLoadSel = t[1];

//
// dr
//
or3Gate cdrLoad(drLoad,t[2],t[T_lw+1],t[T_sw]);
assign drLoadSel={{t[T_sw]},{ir[10]}};

//
// Memory

```

Carmion-1

rtl

seq

pc

hasht

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

$$\sum_{i=0}^n i \text{ program}$$

```

//
orGate  cmemRead(memRead,t[2],t[T_lw+1]);
assign  memWrite=t[T_sw+1];

//
//  ir
//
assign  irLoad=t[3];
assign  irClear=reset;

//
//  r[n]
//

```

Carmion-1

rtl
 seq
 pc
 haltR
 ilglReg
 ar
 dr
 Memory
 ir
 r[n]
 ALU
 r[n]
 $\sum_{i=0}^n i$ program

```

assign aluOp = t[T_lw+2];

notGate  ir10n(ir10n,ir[10]);
andGate  cr0loadLw (r0LoadLw ,t[T_lw+2],ir10n);
andGate  cr0loadAdd(r0LoadAdd,t[T_add],ir10n);
orGate   c_r0Load(r0Load,r0LoadLw,r0LoadAdd);

andGate  cr1loadLw (r1LoadLw , t[T_lw+2],ir[10]);
andGate  cr1loadAdd(r1LoadAdd,t[T_add],ir[10]);
orGate   c_r1Load(r1Load,r1LoadLw,r1LoadAdd);

endmodule

```

Carmion-1

rtl

seq

pc

haltR

ilglReg

pc

dr

Memory

r[n]

ALU

r[n]

 $\sum_{i=0}^n r[i]$
 $\sum_{i=0}^n r[i]$
 $\sum_{i=0}^n r[i]$
 $\sum_{i=0}^n r[i]$
 $\sum_{i=0}^n r[i]$
 $\sum_{i=0}^n r[i]$
 $\sum_{i=0}^n r[i]$
 $\sum_{i=0}^n r[i]$

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

$$\sum_{i=0}^n i \text{ program}$$

Finally, Software

		.code
512	0100000000000000	loop: lw r0,sum
513	0100100000000001	lw r1,i
514	1001000000000000	add r0,r1
515	0110000000000000	sw r0,sum
516	0100000000000011	lw r0,one
517	1000100000000000	add r1,r0
518	0110100000000001	sw r1,i
519	0100000000000010	lw r0,n
520	101101111110111	bgeu r0,r1,loop
521	0010000000000000	halt
		.data
0	0000000000000000	sum: .word 0
1	0000000000000000	i: .word 0
2	0000000000001010	n: .word 10
3	0000000000000001	one: .word 1

Assembler Symbol Table

carmion

©C.M.

Carmion-1

rtl

seq

pc

haltR

ilglReg

ar

dr

Memory

ir

r[n]

ALU

r[n]

$$\sum_{i=0}^n i \text{ program}$$

Label	Address
i	1
n	2
loop	512
one	3
sum	0